

ON Semiconductor

Is Now

onsemi™

To learn more about onsemi™, please visit our website at
www.onsemi.com

onsemi and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.



Is Now Part of



ON Semiconductor®

To learn more about ON Semiconductor, please visit our website at

www.onsemi.com

ON Semiconductor and the ON Semiconductor logo are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

User Guide for
FEBFL6961FL6300_L08U070A

70 W LED Driver at Universal Line

Featured Fairchild Product:
FL6961 + FL6300A

***Direct questions or comments
about this evaluation board to:
“Worldwide Direct Support”***

Fairchild Semiconductor.com

Table of Contents

1. Introduction.....	3
1.1. General Description of FL6961	3
1.2. Features of FL6961	3
1.3. Block Diagram of FL6961	4
1.4. General Description of FL6300A	5
1.5. Features of FL6300A	5
1.6. Block Diagram	5
2. Evaluation Board Specifications.....	6
3. Photographs.....	7
4. Printed Circuit Board	8
5. Schematic	9
6. Bill of Materials	10
7. Transformer Design	12
8. Performance of Evaluation Board.....	14
8.1. Electrical Performances	15
8.2. Power Factor (PF)	16
8.3. Total Harmonic Distortion (THD)	17
8.4. Constant Current (CC) & Constant Voltage (CV)	19
8.5. Operating Temperature	21
8.6. Startup Time.....	22
8.7. Operation Waveforms.....	25
8.8. Short-Circuit Protection.....	28
8.9. Stress of the MOSFET & Rectifier	29
8.10. Electromagnetic Interference (EMI)	35
9. Revision History	36

This user guide supports the evaluation kit for the FL6961 & FL6300A. It should be used in conjunction with the FL6961 & FL6300A datasheets as well as Fairchild's application notes and technical support team. Please visit Fairchild's website at www.fairchildsemi.com.

1. Introduction

This document describes the proposed solution for a universal LED ballast using the FL6961 CRM PFC controller and the FL6300A QR PWM controller. The input voltage range is $90 V_{RMS} - 277 V_{RMS}$ and there is one DC output with a constant current of 2.9 A at $24 V_{MAX}$. This document contains a general description of FL6961 & FL6300A, the power supply specification, schematic, a bill of materials, and the typical operating characteristics.

1.1. General Description of FL6961

The FL6961 is an active Power Factor Correction (PFC) controller for boost PFC applications that operate in Critical Conduction Mode (CRM). It uses a voltage mode PWM that compares an internal ramp signal with the error amplifier output to generate the MOSFET turn-off signal. Because the voltage-mode CRM PFC controller does not need rectified AC line voltage information, it saves the power loss of the input voltage-sensing network required by the current-mode CRM PFC controller.

1.2. Features of FL6961

- Boundary Mode PFC Controller
- Low Input Current THD
- Controlled On-Time PWM
- Zero-Current Detection (ZCD)
- Cycle-by-Cycle Current Limiting
- Leading-Edge Blanking Instead of RC Filtering
- Low Startup Current: 10 μ A (Typical)
- Low Operating Current: 4.5 mA (Typical)
- Feedback Open-Loop Protection
- Programmable Maximum On-Time (MOT)
- Output Over-Voltage Clamping Protection
- Clamped Gate Output Voltage: 16.5 V

1.3. Block Diagram of FL6961

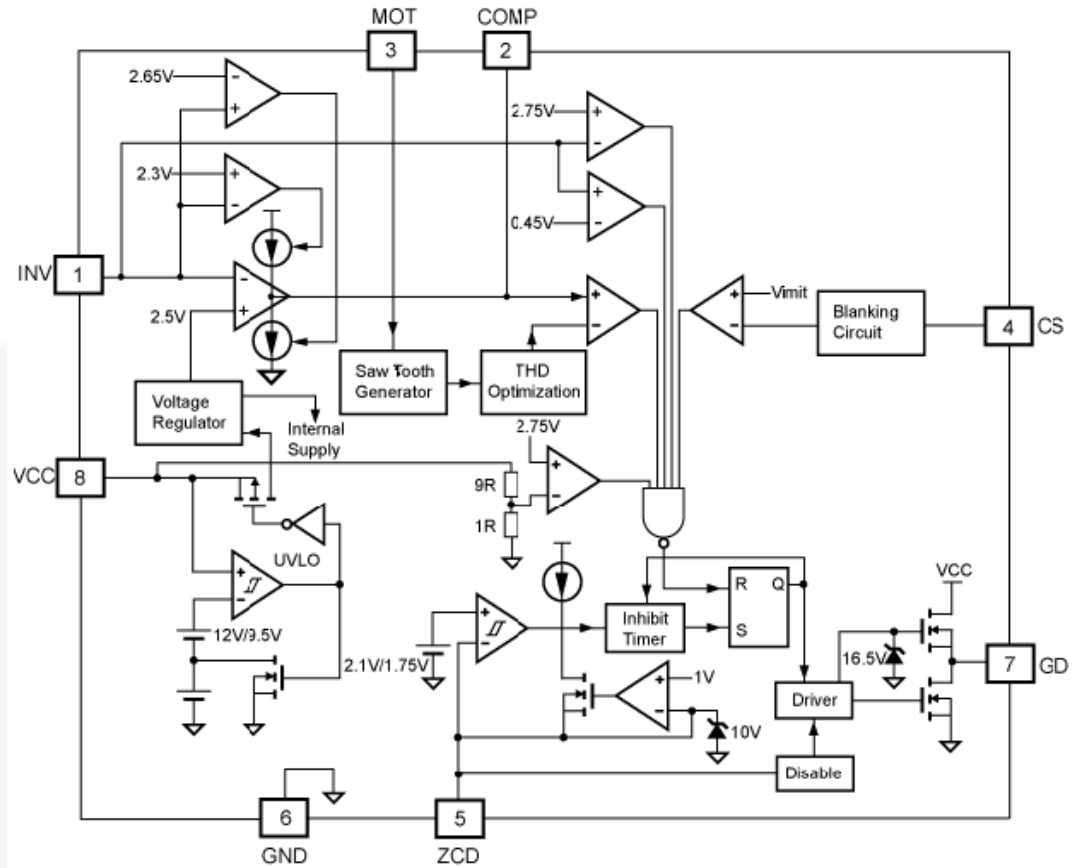


Figure 1. FL6961 Block Diagram

1.4. General Description of FL6300A

The FL6300A is a highly integrated quasi-resonant PWM controller with several features to enhance the performance of flyback converters. A built-in HV startup circuit can provide more startup current to reduce the startup time of the controller and reduce power consumption. An internal valley voltage detector ensures the power system operates at quasi-resonant operation in wide range line voltage and any load conditions and reduces switching loss to minimize switching voltage on the drain of the power MOSFET.

1.5. Features of FL6300A

- Internal High-Voltage Startup
- Quasi-Resonant Operation
- Cycle-by-Cycle Current Limiting
- Peak Current Mode Control
- Leading-Edge Blanking
- Internal Minimum t_{OFF}
- Internal 2 ms Soft-Start
- Over-Power Compensation
- Gate Output Maximum Voltage
- Auto-Recovery Short-Circuit Protection (FB Pin)
- Auto-Recovery Open-Loop Protection (FB Pin)
- VDD Pin & Output Voltage (DET Pin) Latch OVP

1.6. Block Diagram

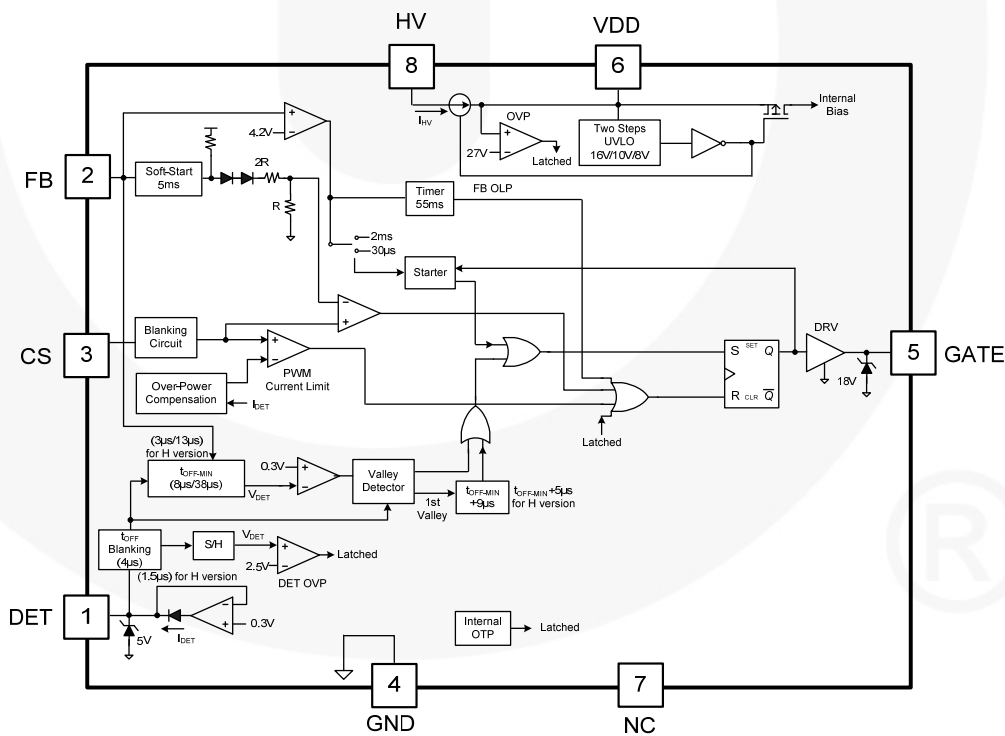


Figure 2. FL6300A Block Diagram

2. Evaluation Board Specifications

Table 1. Summary of Features for LED Lighting Bulb

Main Controller	FL6961 & FL6300A
Input Voltage Range	90 V _{AC} ~277 V _{AC}
Input Voltage Frequency	47 Hz~63 Hz
Rated Output Power	70 W
Rated Output Voltage	24 V
Rated Output Current	2.9 A
Application	LED Lighting

All data of the evaluation board was measured with the board enclosed in a case and external temperature of around 25°C.

3. Photographs

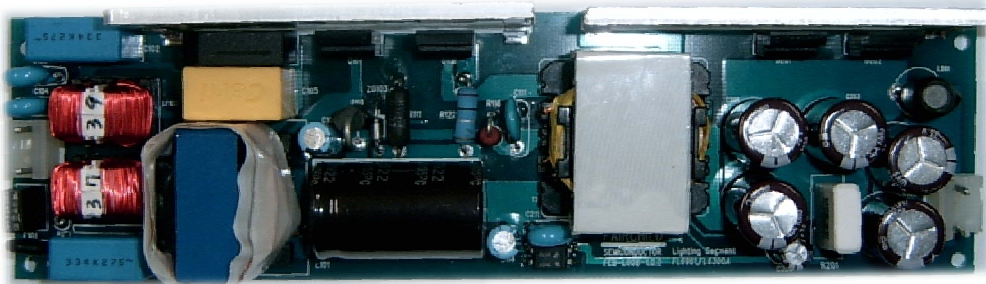


Figure 3. Photograph (183 mm (L) x 55 mm (W)) Top View

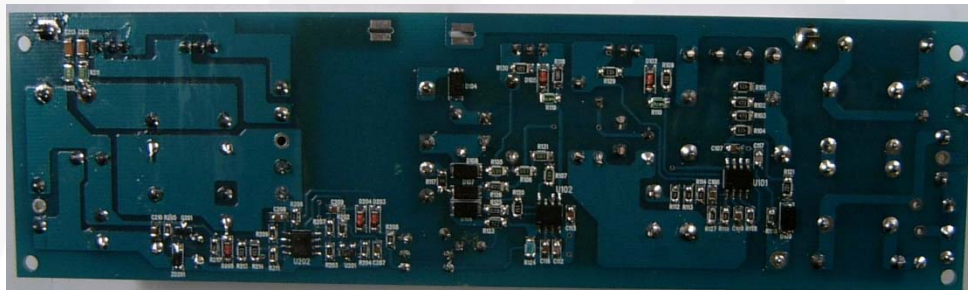


Figure 4. Photograph (183 mm (L) x 55 mm (W)) Bottom View

4. Printed Circuit Board

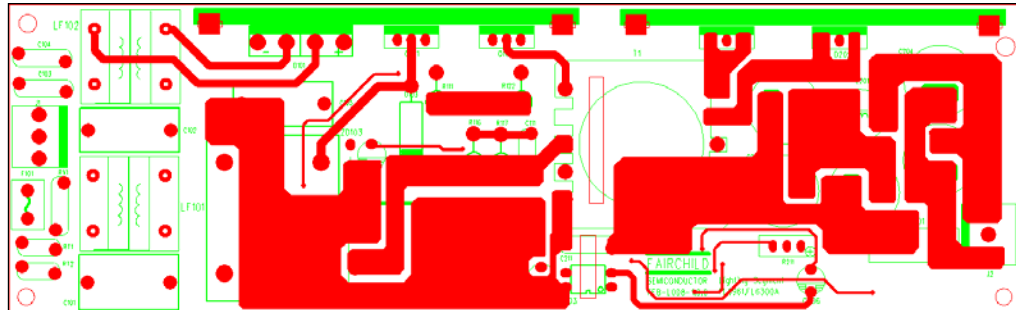


Figure 5. Printed PCB, Top Side

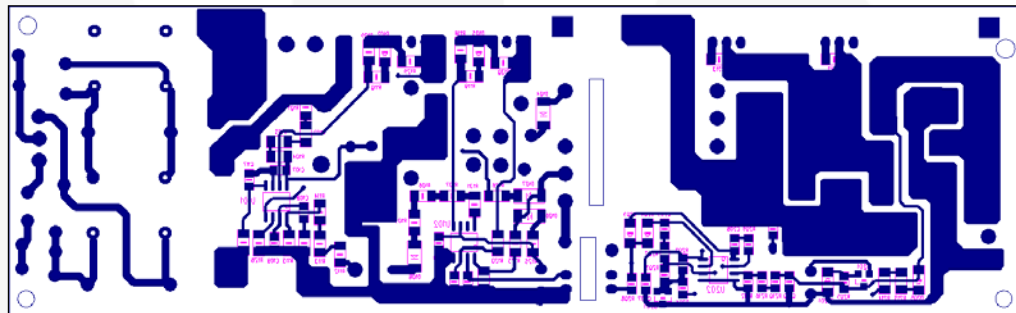


Figure 6. Printed PCB, Bottom Side

5. Schematic

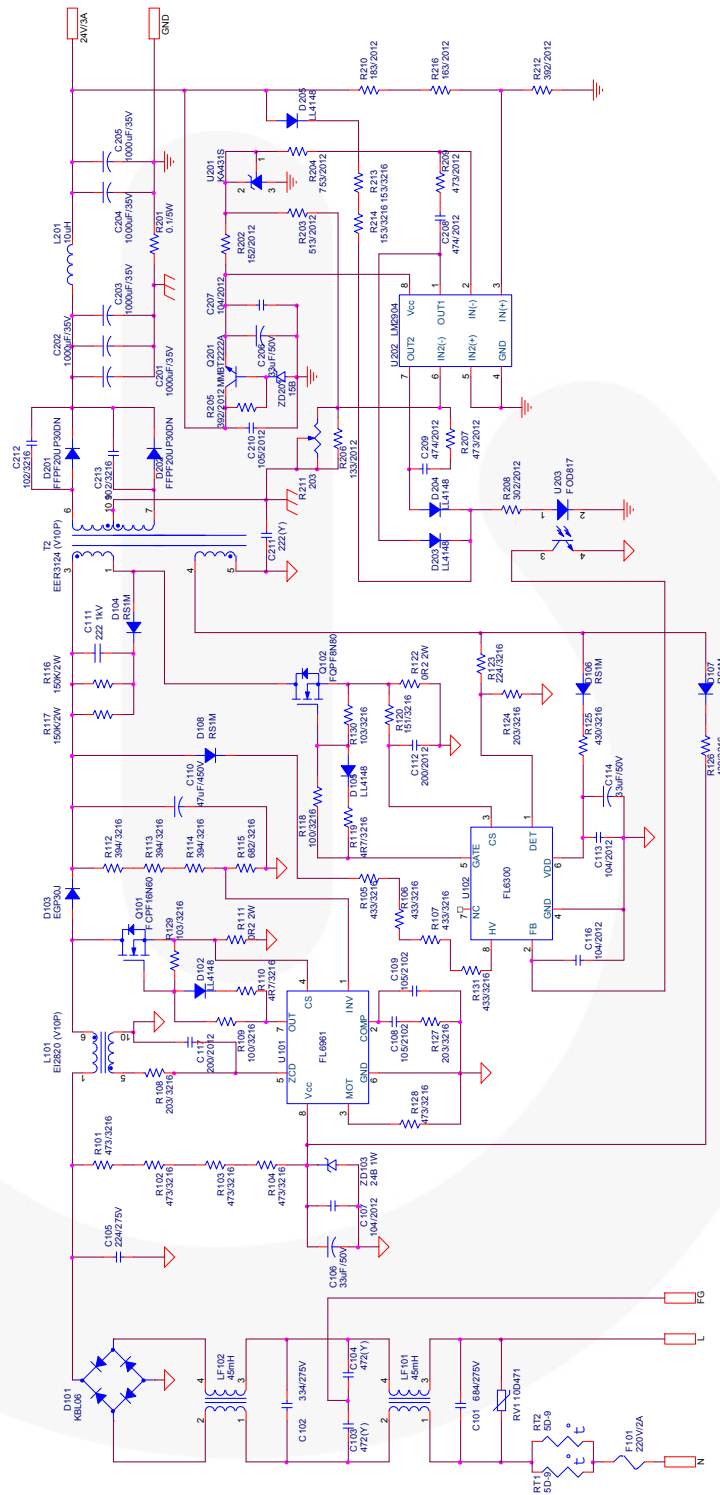


Figure 7. Evaluation Board Schematic

6. Bill of Materials

Table 2. Bill of Materials of Evaluation Board

Item No.	Part Reference	Value	Qty	Description
1	U101	FL6961	1	CRM PFC Controller, Fairchild Semiconductor
2	U102	FL6300A	1	QR PWM Controller, Fairchild Semiconductor)
3	Q101	FCPF20N60	1	600 V / 20 A MOSFET, Fairchild Semiconductor
4	Q102	FQPF8N80	1	800 V / 8 A MOSFET, Fairchild Semiconductor
5	D201, D202	FFPF20UP30DN	2	Ultra-Fast Recovery Power Rectifier, Fairchild Semiconductor
6	D103	EGP30J	1	600 V / 3 A Ultra-Fast Recovery Diode, Fairchild Semiconductor
7	D104, D106, D107, D108	RS1M	4	1000 V / 1 A Ultra-Fast Recovery Diode, Fairchild Semiconductor
8	D101	KBL06	1	Bridge Diode, Fairchild Semiconductor
9	Q201	MMBT2222A	1	General-Purpose Transistor, Fairchild Semiconductor
10	U202	LM2904	1	Dual OP AMP, Fairchild Semiconductor
11	U203	FOD817	1	Opto-Coupler, Fairchild Semiconductor
12	U201	KA431S	1	Shunt Regulator, Fairchild Semiconductor
13	ZD103	24B 1W	1	Zener Diode, Fairchild Semiconductor
14	ZD201	15B	1	Zener Diode, Fairchild Semiconductor
15	D102, D105, D203, D204, D205	LL4148	5	General-Purpose Diode, Fairchild Semiconductor
16	C101	684 / 275 V	1	0.68 μ F / 275 V _{AC} X – Capacitor
17	C102	334 / 275 V	1	0.33 μ F / 275 V _{AC} X – Capacitor
18	C105	224 / 275 V	1	0.22 μ F / 275 V _{AC} X – Capacitor
19	C103,C104	472 (Y)	2	4.7 nF / 250 V Y – Capacitor
20	C211	222 (Y)	1	2.2 nF / 250 V Y – Capacitor
21	C106, C114, C206	33 μ F / 50V	3	33 μ F / 50 V Electrolytic Capacitor, 105°C
22	C107, C113, C116, C207	104/ 2012	4	0.1 μ F SMD Capacitor 2012
23	C108, C109, C210	105 / 2102	3	1 μ F SMD Capacitor 2012
24	C110	68 μ F / 450 V	1	68 μ F / 450 V Electrolytic Capacitor, 105°C
25	C111	222 / 1 kV	1	2.2 nF Ceramic-Capacitor
26	C112, C117	200 / 2012	2	20 pF SMD Capacitor 2012
27	C201, C202, C203, C204, C205	1000 μ F / 35 V	5	1000 μ F / 35 V Electrolytic Capacitor, 105°C
28	C208, C209	474 / 2012	2	0.47 μ F SMD Capacitor 2012
29	C212, C213	102 / 3216	2	1 nF SMD Capacitor 3216
30	F101	250 V / 2 A	1	Fuse
31	L101	EI2820	1	PFC Inductor (V10P), 450 μ H, 1 kHz, 1 V
32	L201	10 μ H	1	10 μ H Stick Inductor
33	LF101, LF102	45 mH	2	45 mH Line Filter
34	R101, R102, R103, R104	104 / 3216	4	100 k Ω SMD Resistor 3216
35	R128	393 / 3216	1	39 k Ω SMD Resistor 3216
36	R105, R106, R107, R131	433 / 3216	4	43 k Ω SMD Resistor 3216

Bill of Materials (Continued)

Item No.	Part Reference	Value	Qty	Description
37	R108, R124, R127	203 / 3216	3	20 kΩ SMD Resistor 3216
38	R109, R118	100 / 3216	2	10 Ω SMD Resistor 3216
39	R110, R119	4R7 / 3216	2	4.7 Ω SMD Resistor 3216
40	R111, R122	0R2 / 2 W	2	0.2 Ω Metal Film Resistor 2 W
41	R112, R113, R114	394 / 3216	3	390 kΩ SMD Resistor 3216
42	R115	682 / 3216	1	6.8 kΩ SMD Resistor 3216
43	R213, R214	153 / 3216	2	15 kΩ SMD Resistor 3216
44	R116, R117	150 K / 2 W	2	150 kΩ Metal Film Resistor 2 W
45	R120	151 / 3216	1	150 Ω SMD Resistor 3216
46	R123	224 / 3216	1	220 kΩ SMD Resistor 3216
47	R125, R126	430 / 3216	2	43 Ω SMD Resistor 3216
48	R129, R130	103 / 3216	2	10 kΩ SMD Resistor 3216
49	R201	0.1 / 5 W	1	0.1 Ω MPR Resistor 5W
50	R202	152 / 2012	1	1.5 kΩ SMD Resistor 2012
51	R203	513 / 2012	1	51 kΩ SMD Resistor 2012
52	R204	753 / 2012	1	75 kΩ SMD Resistor 2012
53	R205	392 / 2012	1	3.9 kΩ SMD Resistor 2012
54	R206	133 / 2012	1	13 kΩ SMD Resistor 2012
55	R207, R209	473 / 2012	2	47 kΩ SMD Resistor 2012
56	R208	302 / 2012	1	3 kΩ SMD Resistor 2012
57	R212	432 / 2012	1	4.3 kΩ SMD Resistor 2012
58	R210	153 / 2012	1	15 kΩ SMD Resistor 2012
59	R216	223 / 2012	1	22 kΩ SMD Resistor 2012
60	R211	20 k	1	Variable Resistor 20 k
61	RT1, RT2	5D-9	2	NTC
62	T2	EER3124	1	QR Transformer (V10P), 500 μH, 1 kHz, 1 V
63	RV1	10D471	1	VARISTOR

7. Transformer Design

7.1. Flyback Converter Transformer (T2)

- Core: EER3124
- Bobbin: 10 pins

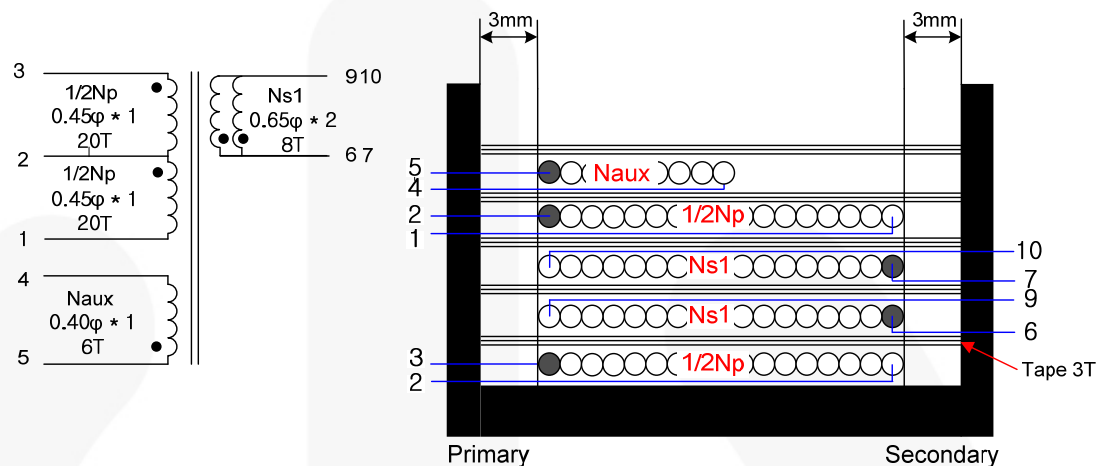


Figure 8. Transformer Specifications & Construction (EER3124)

Table 3. Winding Specifications

No.	Winding	Pin (S → F)	Wire	Turns	Winding Method
1	1/2Np	3 → 2	0.10φ×20	20 Ts	Solenoid Winding
Insulation: Polyester Tape t = 0.025 mm, 3-Layer					
2	Ns1	6 → 9	0.10φ×50	8 Ts	Solenoid Winding
Insulation: Polyester Tape t = 0.025 mm, 1-Layer					
3	Ns2	7 → 10	0.10φ×50	8 Ts	Solenoid Winding
Insulation: Polyester Tape t = 0.025 mm, 3-Layer					
4	1/2Np	2 → 1	0.10φ×20	20 Ts	Solenoid Winding
Insulation: Polyester Tape t = 0.025 mm, 2-Layer					
6	Naux	5 → 4	0.40φ×1	6 Ts	Solenoid Winding
Insulation: Polyester Tape t = 0.025 mm, 3-Layer					

Table 4. Electrical Characteristics

	Pin	Specification	Remark
Inductance	1 – 3	500 μH ±7%	1 kHz, 1 V
Leakage	1 – 3	14 μH Maximum	Short All Output Pins

7.2. Power Factor Controller Transformer (L101)

- Core : EI2820
- Bobbin : 10 pin

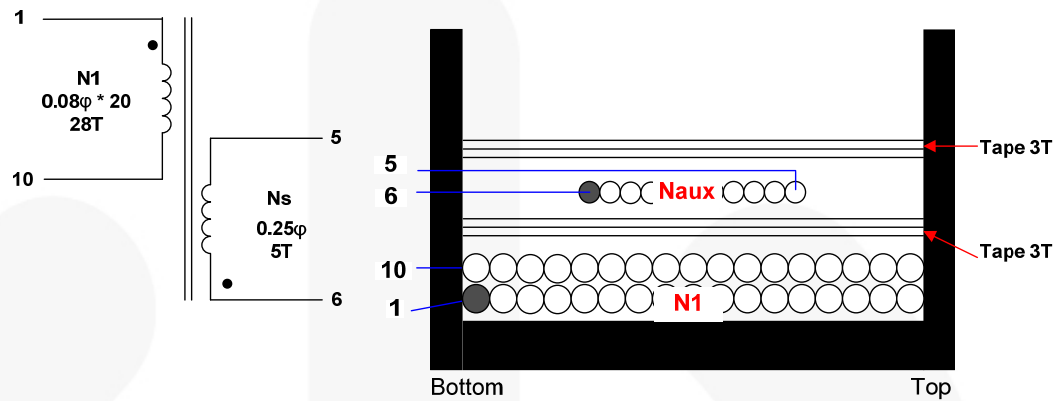


Figure 9. Inductor Specifications & Construction (EI2824)

Table 5. Winding Specifications

No	Winding	Pin (S→F)	Wire	Turns	Winding Method
1	N1	1 → 10	0.12φ×25	44 Ts	Solenoid Winding
Insulation: Polyester Tape t = 0.025 mm, 3-Layer					
2	Ns1	7 → 5	0.1φ×12	6 Ts	Space Winding
Insulation: Polyester Tape t = 0.025 mm, 3-Layer					

Table 6. Electrical Characteristics

	Pin	Specification	Remark
Inductance	1 – 10	450 μH	1 kHz, 1 V
Leakage	1 – 10	10 μH Maximum	Short All Output Pins

8. Performance of Evaluation Board

Table 7. Test Conditions & Items

Ambient Temperature	$T_A = 25^\circ\text{C}$
Test Equipment	AC Power Source: PCR500L by Kikusui Power Analyzer: PM3000 by Voltech Electronic Load: PLZ303WH by KIKUSUI Multi Meter: 2002 by KEITHLEY, 45 by FLUKE Oscilloscope: 104Xi by LeCroy Two-Line V-Network: ENV216 by ROHDE & SCHWARZ Thermometer: Thermal CAM SC640 by FLIR SYSTEMS

8.1. Electrical Performances

Figure 10 shows at least 83% system efficiency with universal input condition at the rated output load.

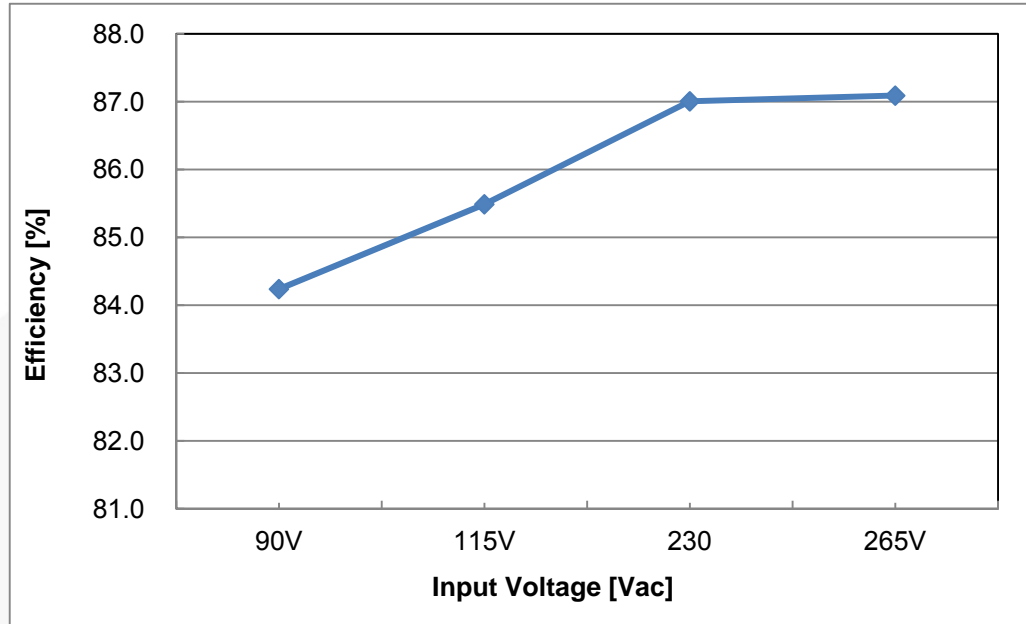


Figure 10. System Efficiency

Input Voltage	90 V _{AC}	115 V _{AC}	230 V _{AC}	277 V _{AC}
Efficiency	83.02%	84.77%	87.23%	87.33%

8.2. Power Factor (PF)

Figure 11 shows consistent results over 90% PF results with universal input condition at the rated output power.

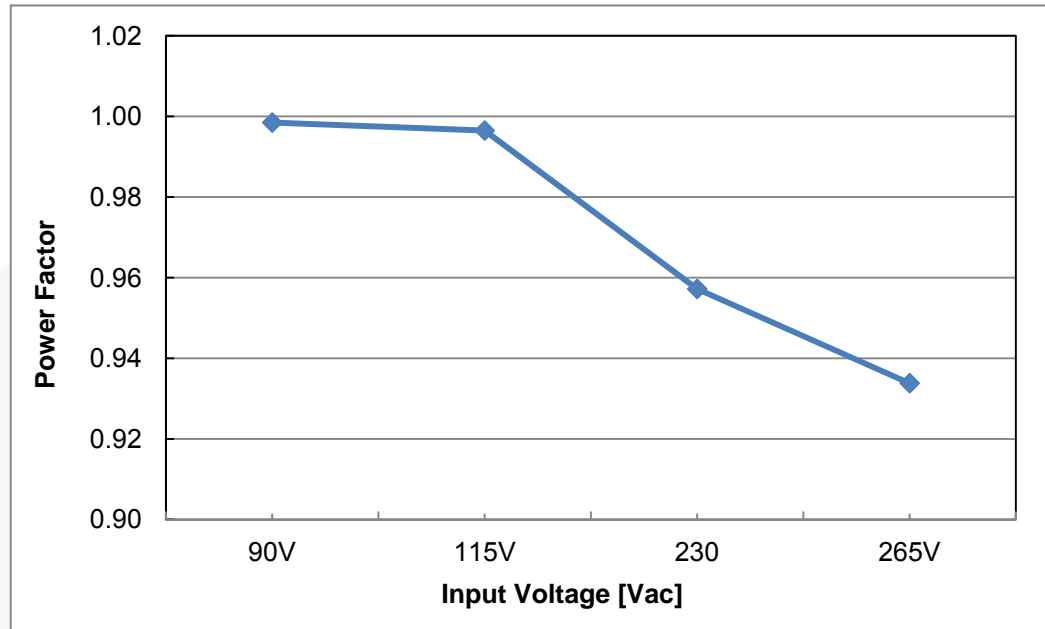


Figure 11. Power Factor

Input Voltage	90 V _{AC}	115 V _{AC}	230 V _{AC}	277 V _{AC}
PF	0.996	0.995	0.954	0.913

8.3. Total Harmonic Distortion (THD)

Figure 12 through Figure 15 show the test results of FL6961 and FL6300A evaluation board. All the results meet the international regulations.

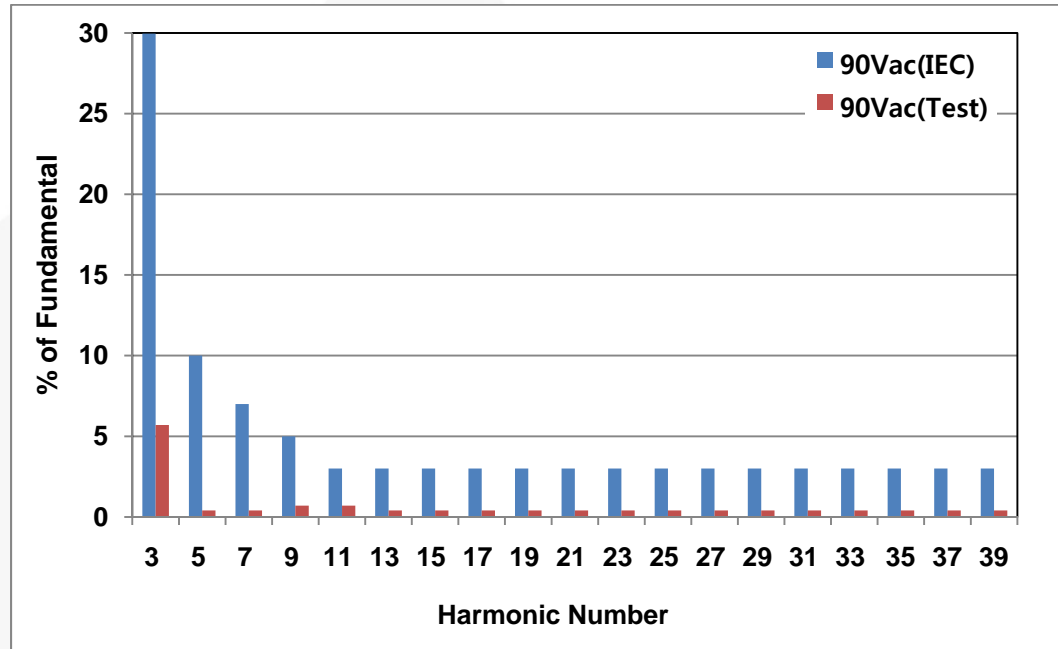


Figure 12. THD Performance Results at 90 V_{AC}

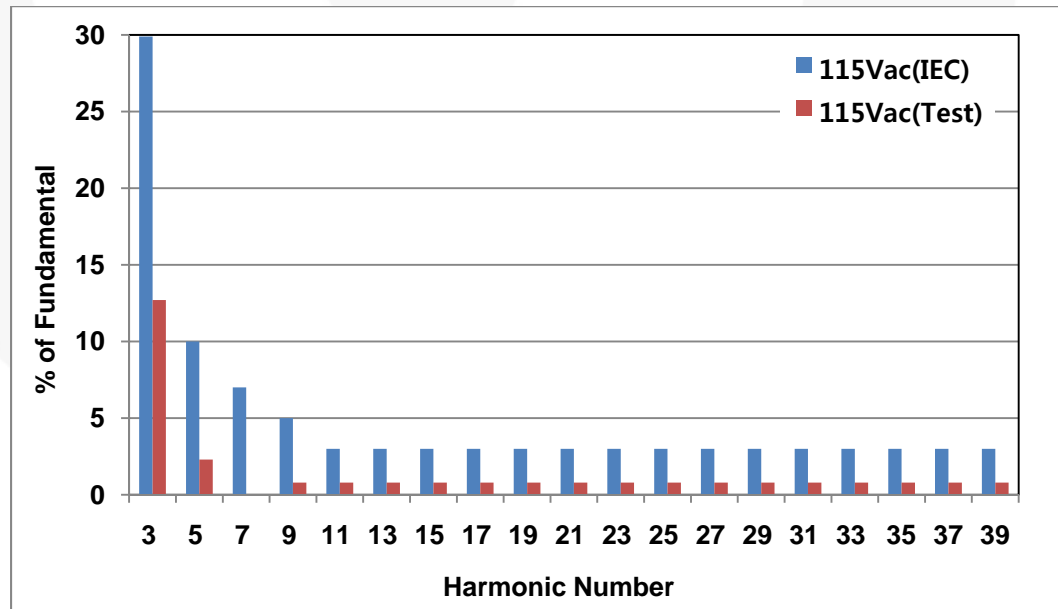


Figure 13. THD Performance Results at 115 V_{AC}

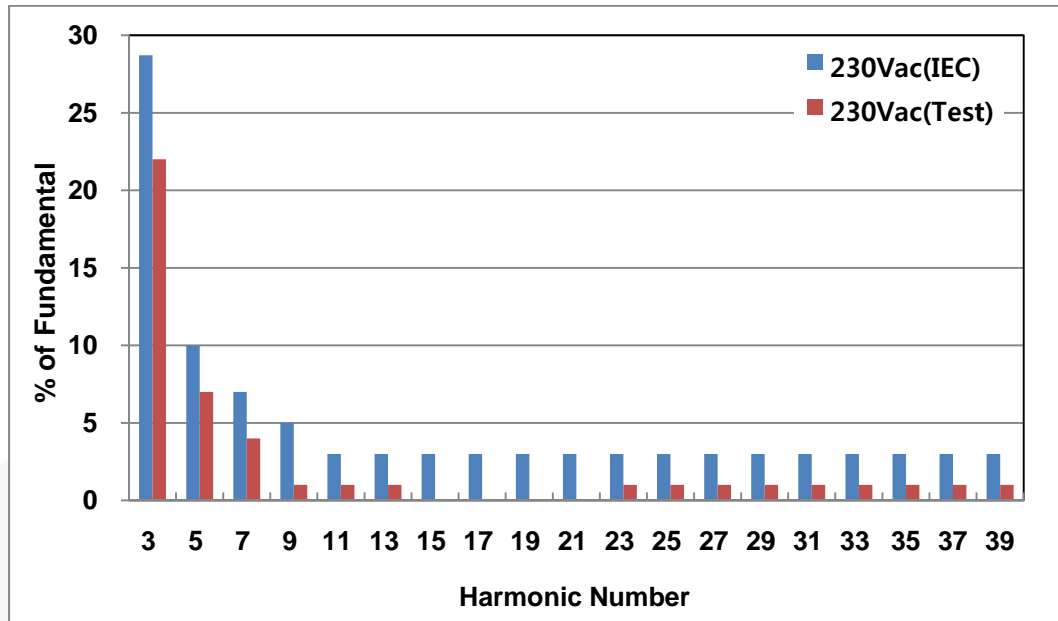


Figure 14. THD Performance Results at 230 V_{AC}

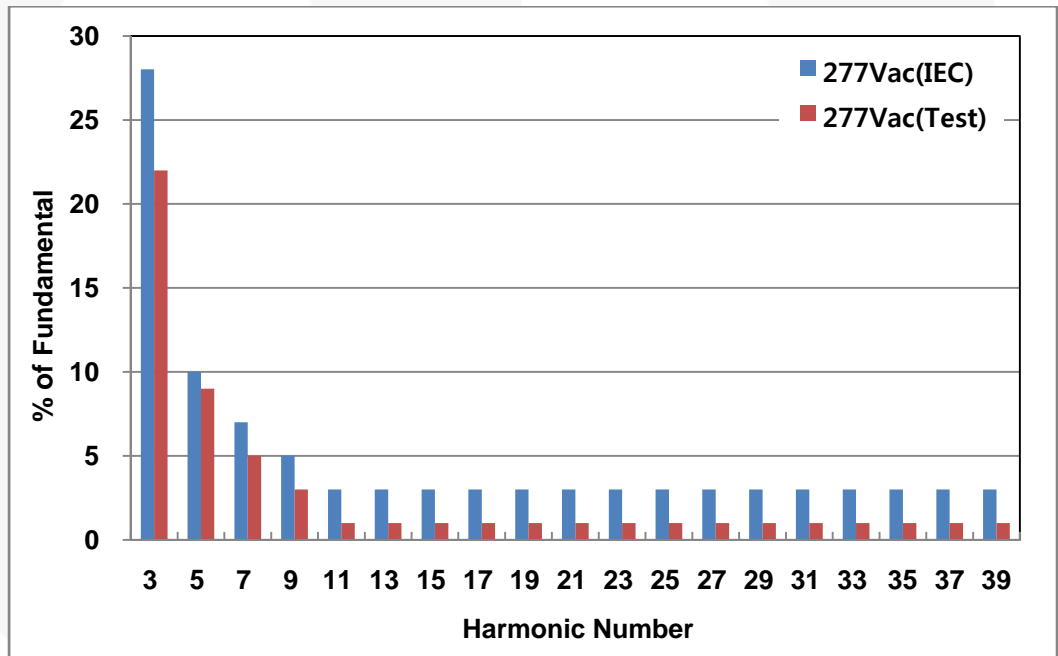


Figure 15. THD Performance Results at 277 V_{AC}

8.4. Constant Current (CC) & Constant Voltage (CV)

Figure 16 shows the typical CC/CV performance on the board, showing very stable CC performance at 90 V_{AC} ~ 277 V_{AC} input conditions.

Input Voltage	Min. Current [A]	Max. Current [A]	Tolerance	Remark
90 V _{AC} / 60 Hz	2.968	2.976	0.27%	< 10%
115 V _{AC} / 60 Hz	2.967	2.975	0.27%	
230 V _{AC} / 60 Hz	2.977	2.984	0.23%	
277 V _{AC} / 60 Hz	2.970	2.977	0.24%	
Total	2.968	2.984	0.54%	

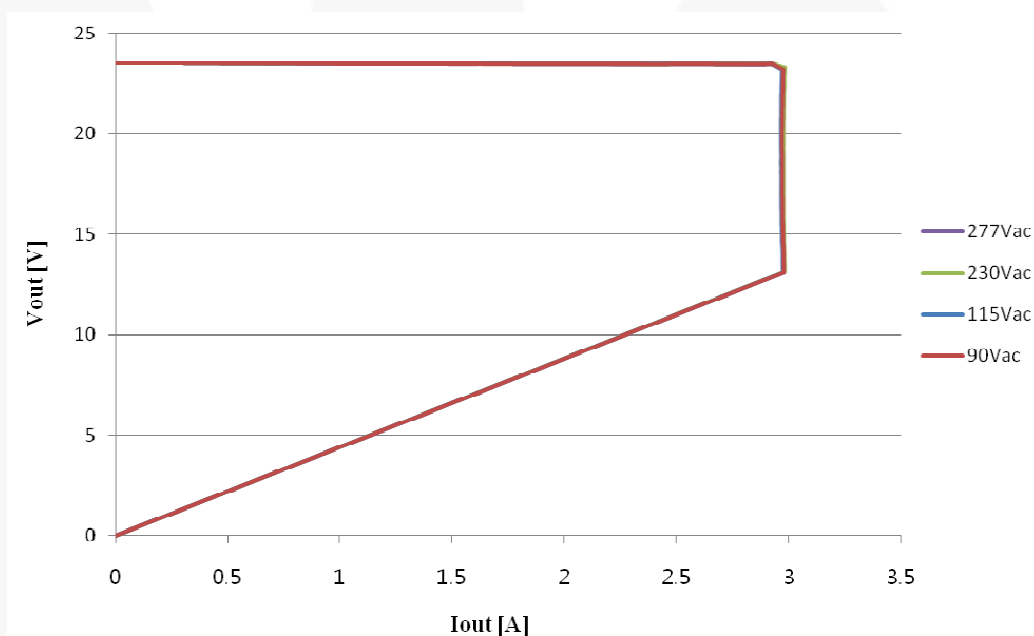


Figure 16. CC/CV Performance

Table 8. CC and CV Measured Data

90 V _{AC}		115 V _{AC}		230 V _{AC}		277 V _{AC}	
V _{OUT} [V]	I _{OUT} [A]	V _{OUT} [V]	I _{OUT} [A]	V _{OUT} [V]	I _{OUT} [A]	V _{OUT} [V]	I _{OUT} [A]
23.52	0	23.52	0	23.51	0	23.52	0
23.52	0.291	23.52	0.291	23.51	0.291	23.51	0.440
23.51	0.440	23.51	0.440	23.50	0.440	23.51	0.440
23.50	0.582	23.50	0.582	23.49	0.582	23.50	0.582
23.50	0.731	23.50	0.731	23.49	0.731	23.50	0.731
23.49	0.879	23.49	0.879	23.48	0.879	23.49	0.879
23.48	1.022	23.48	1.022	23.47	1.021	23.48	1.022
23.48	1.170	23.48	1.170	23.47	1.170	23.48	1.170
23.47	1.312	23.48	1.312	23.47	1.312	23.47	1.466
23.47	1.466	23.47	1.466	23.46	1.466	23.46	1.615
23.47	1.615	23.47	1.615	23.46	1.615	23.47	1.757
23.46	1.757	23.47	1.757	23.46	1.757	23.46	1.906
23.46	1.906	23.46	1.906	23.46	1.905	23.46	1.906
23.46	2.054	23.46	2.054	23.46	2.053	23.46	2.054
23.46	2.190	23.46	2.190	23.46	2.190	23.46	2.190
23.46	2.344	23.46	2.344	23.45	2.343	23.46	2.344
23.45	2.789	23.45	2.789	23.45	2.789	23.46	2.927
23.46	2.926	23.46	2.926	23.47	2.927	23.46	2.926
23.46	2.926	23.46	2.926	23.47	2.927	23.22	2.975
23.20	2.973	23.18	2.971	23.29	2.984	23.21	2.975
22.27	2.971	22.26	2.969	22.35	2.982	22.28	2.973
21.69	2.970	21.68	2.968	21.77	2.980	21.10	2.972
20.80	2.969	20.79	2.967	20.87	2.979	20.52	2.971
20.50	2.969	20.49	2.967	20.57	2.978	20.22	2.970
19.89	2.968	19.87	2.967	19.94	2.978	19.90	2.970
19.57	2.968	19.56	2.967	19.63	2.978	19.32	2.970
19.31	2.968	19.30	2.967	19.37	2.978	19.32	2.970
18.70	2.969	18.69	2.968	18.76	2.978	18.71	2.971
18.42	2.969	18.41	2.967	18.48	2.978	18.44	2.971
18.13	2.969	18.12	2.968	18.18	2.978	18.14	2.971
17.53	2.969	17.53	2.968	17.59	2.978	17.54	2.971
17.53	2.969	17.53	2.968	17.59	2.978	17.22	2.971
17.21	2.969	17.21	2.968	17.26	2.978	17.22	2.971
17.21	2.969	17.21	2.968	17.26	2.978	16.94	2.971
16.93	2.969	16.92	2.968	19.98	2.978	16.94	2.971
16.34	2.970	16.33	2.968	16.39	2.978	16.05	2.972
16.04	2.970	16.03	2.969	16.08	2.978	16.05	2.972
16.04	2.970	16.03	2.969	16.08	2.978	15.78	2.972
15.77	2.970	15.77	2.969	15.81	2.978	15.78	2.972
15.47	2.971	15.47	2.970	15.51	2.979	15.17	2.973
15.16	2.971	15.16	2.970	15.20	2.979	15.17	2.973
14.87	2.972	14.86	2.971	14.90	2.980	14.59	2.974
14.58	2.972	14.58	2.971	14.62	2.980	14.59	2.974
14.29	2.974	14.29	2.973	14.33	2.981	14.02	2.976
14.01	2.975	14.01	2.974	14.05	2.982	14.02	2.976
13.69	2.975	13.69	2.974	13.72	2.982	13.41	2.977
13.40	2.975	13.40	2.974	13.43	2.983	13.41	2.977
13.11	2.976	13.10	2.975	13.14	2.983	13.11	2.977

8.5. Operating Temperature

Figure 17 through Figure 20 show the temperature-checking results on the board in minimum and maximum input voltage condition.

	90 V _{AC} / 60 Hz	277 V _{AC} / 60 Hz	Remark
Bridge Diode	66.3°C	55.7°C	Top-Side Circle
FET(PFC)	63.5°C	56.8°C	Top-Side Line
FET(QR)	65.2°C	56.8°C	Top-Side Box
Rectifier	64.9°C	65.6°C	Top-Side Spot

Temperature Results

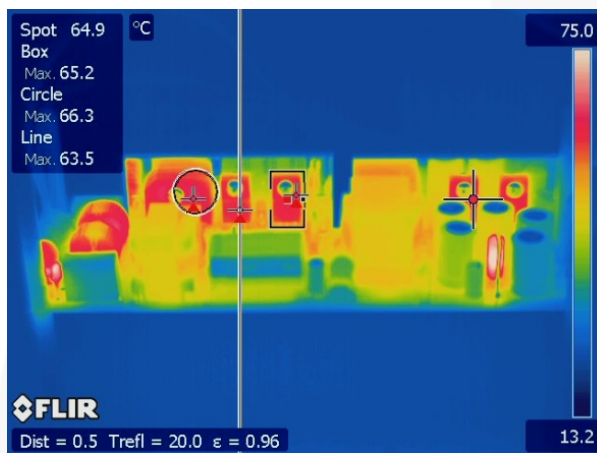


Figure 17. 90 V_{AC} / 60 Hz; Top Side

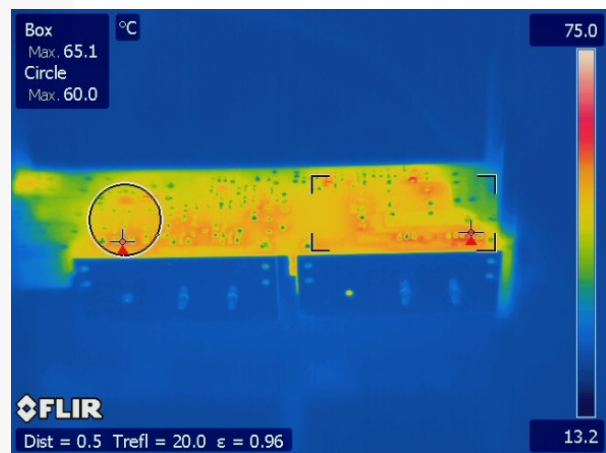


Figure 18. 90 V_{AC} / 60 Hz; Bottom Side

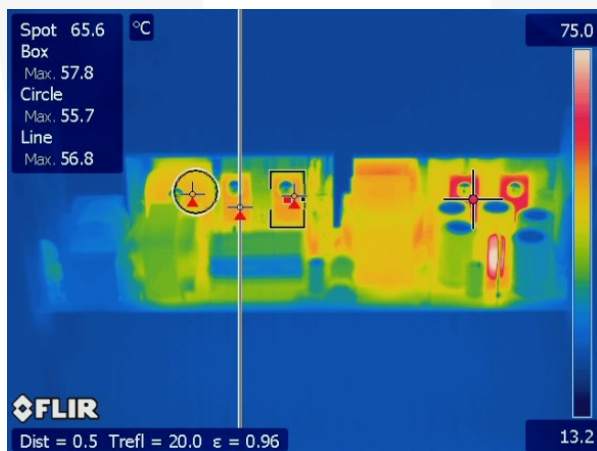


Figure 19. 277 V_{AC} / 60 Hz; Top Side

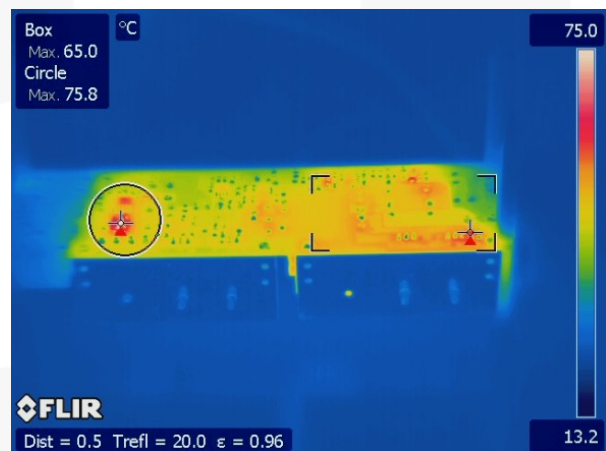


Figure 20. 277 V_{AC} / 60 Hz; Bottom Side

8.6. Startup Time

Figure 21 and Figure 22 show the typical startup performance on the board. A longer startup time to release the UVLO function can be achieved on the IC at 90 V_{AC} condition rather than 277 V_{AC} condition. This time normally depends on the starting resistor and capacitor on the board.

Input Voltage	Turn On Time	Remark
90 V _{AC} / 60 Hz	0.872 s	< 1 s
277 V _{AC} / 60 Hz	0.271 s	

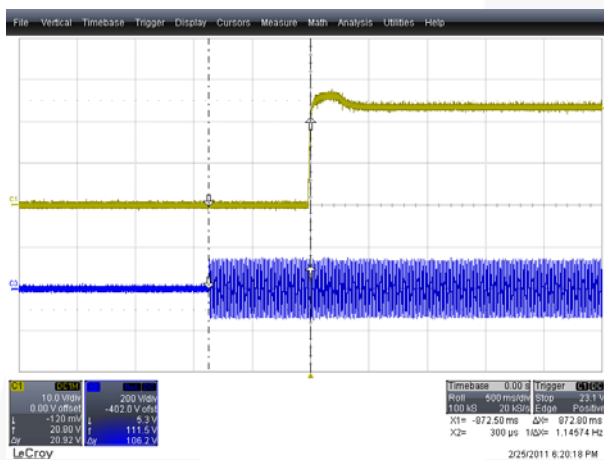


Figure 21. 90 V_{AC} / 60 Hz, CH1 (Yellow): V_{OUT}, CH3 (Blue): V_{IN}

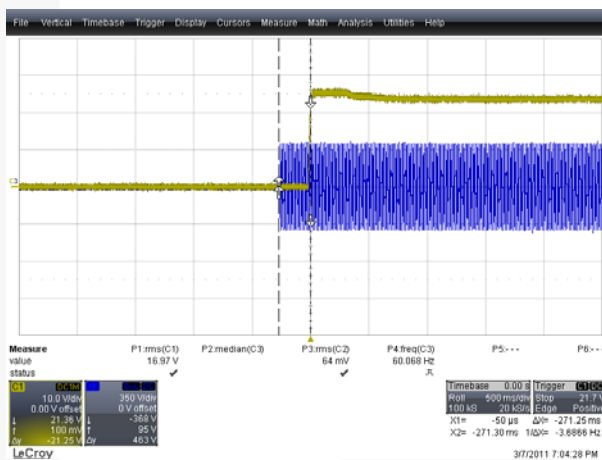


Figure 22. 277 V_{AC} / 60 Hz, CH1 (Yellow): V_{OUT}, CH3 (Blue): V_{IN}

Figure 23 through Figure 26 show the typical startup performance of PFC circuit on the board.

Input Voltage	Turn-On Time	Remark
90 V _{AC} / 60 Hz	0.584 s	< 1 s
115 V _{AC} / 60 Hz	0.535 s	
230 V _{AC} / 60 Hz	0.320 s	
277 V _{AC} / 60 Hz	0.242 s	

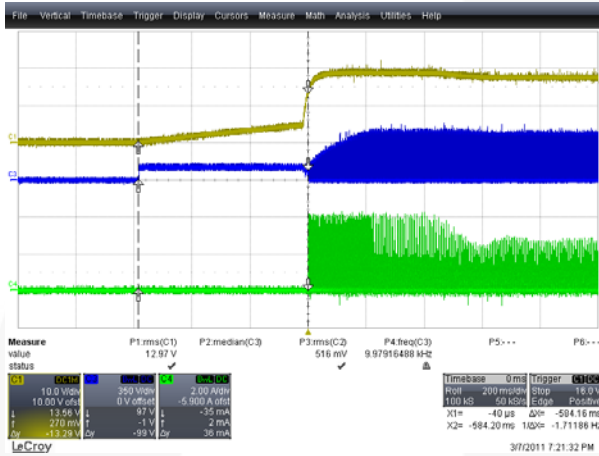


Figure 23. 90 V_{AC} / 60 Hz, CH2 (Red): V_{CC}(PFC), CH3 (Blue): V_{DS}(PFC), CH4 (Green): I_{DS}(PFC)

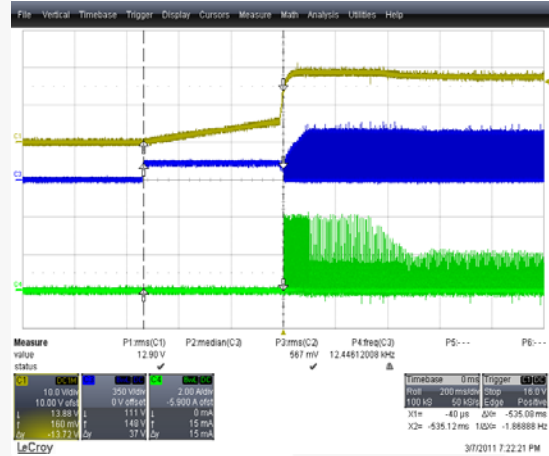


Figure 24. 115 V_{AC} / 60 Hz, CH2 (Red): V_{CC}(PFC), CH3 (Blue): V_{DS}(PFC), CH4 (Green): I_{DS}(PFC)

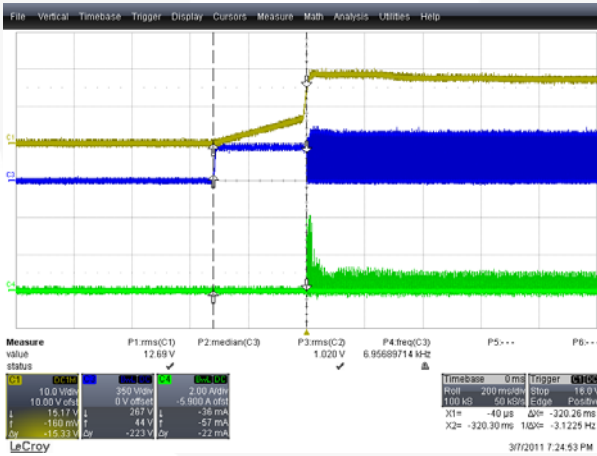


Figure 25. 230 V_{AC} / 60 Hz, CH2 (Red): V_{CC}(PFC), CH3 (Blue): V_{DS}(PFC), CH4 (Green): I_{DS}(PFC)

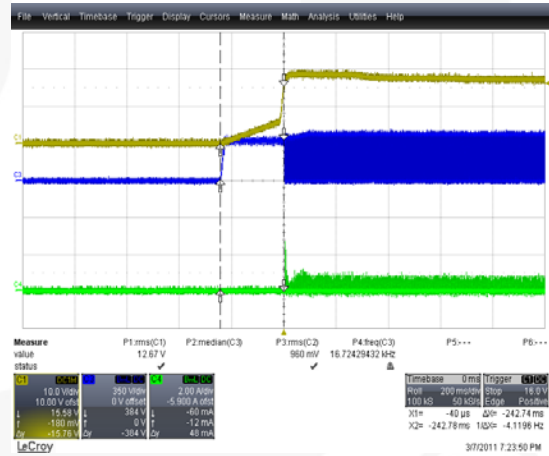


Figure 26. 277 V_{AC} / 60 Hz, CH2 (Red): V_{CC}(PFC), CH3 (Blue): V_{DS}(PFC), CH4 (Green): I_{DS}(PFC)

Figure 27 through Figure 30 show the typical startup performance of the QR flyback circuit on the board.

Input Voltage	Turn On Time	Remark
90 V _{AC} / 60 Hz	0.878 s	< 1 s
115 V _{AC} / 60 Hz	0.677 s	
230 V _{AC} / 60 Hz	0.351 s	
277 V _{AC} / 60 Hz	0.320 s	

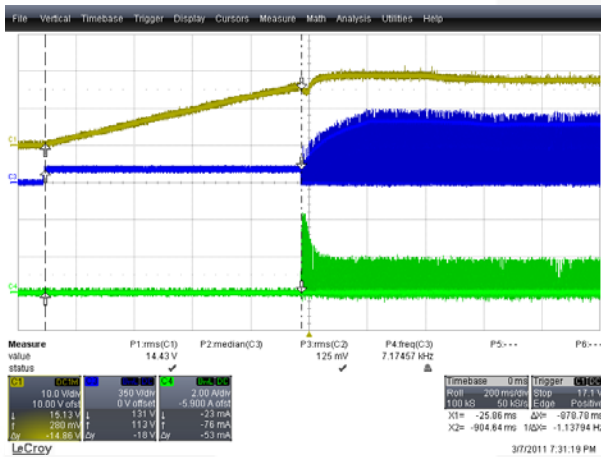


Figure 27. 90 V_{AC} / 60 Hz, CH1 (Yellow): V_{CC(QR)}, CH3 (Blue): V_{DS(QR)}, CH4 (Green): I_{DS(QR)}

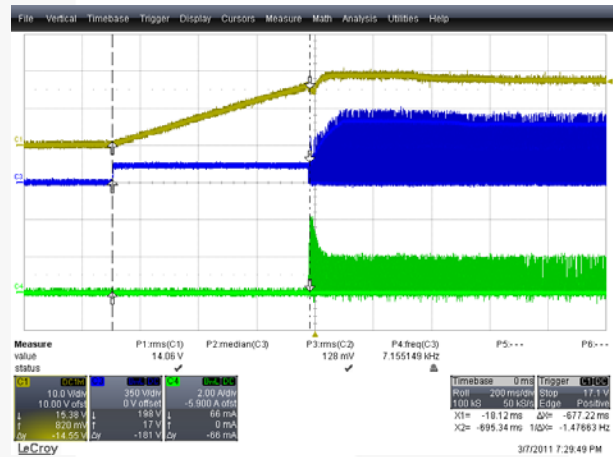


Figure 28. 115 V_{AC} / 60 Hz, CH1 (Yellow): V_{CC(QR)}, CH3 (Blue): V_{DS(QR)}, CH4 (Green): I_{DS(QR)}

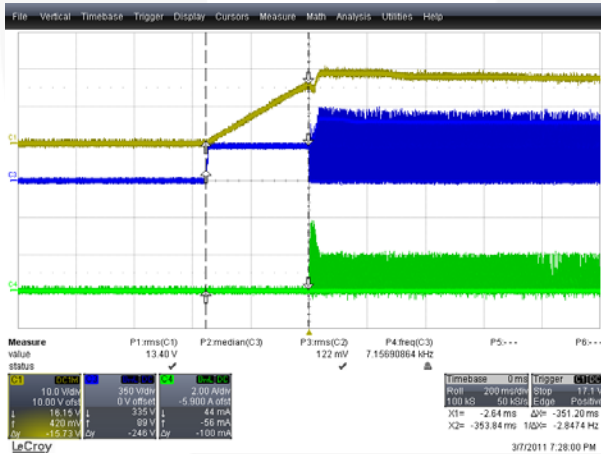


Figure 29. 230 V_{AC} / 60 Hz, CH1 (Yellow): V_{CC(QR)}, CH3 (Blue): V_{DS(QR)}, CH4 (Green): I_{DS(QR)}

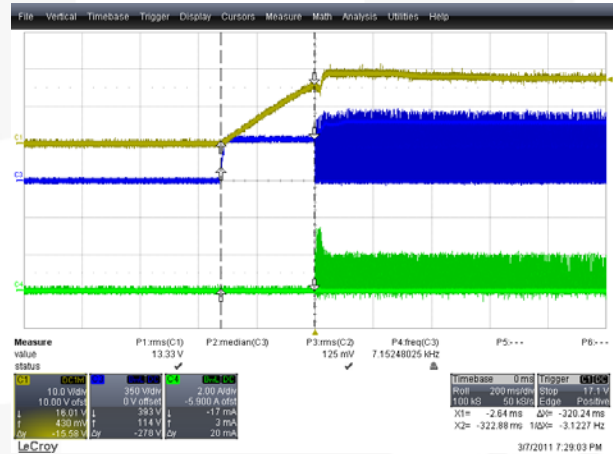


Figure 30. 277 V_{AC} / 60 Hz, CH1 (Yellow): V_{CC(QR)}, CH3 (Blue): V_{DS(QR)}, CH4 (Green): I_{DS(QR)}

8.7. Operation Waveforms

Normal Operation

Figure 31 through Figure 34 show the input current waveforms on the board at different input voltage conditions.

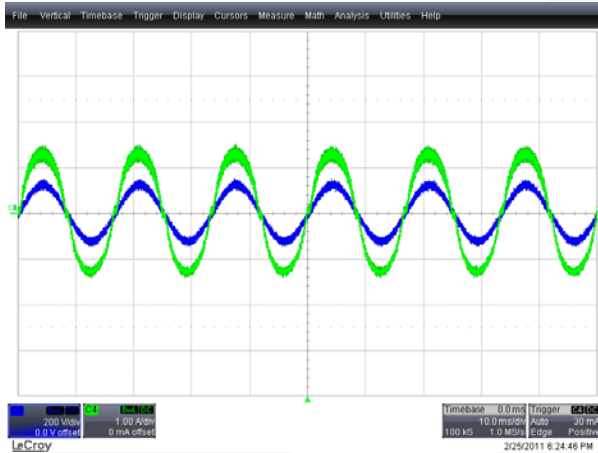


Figure 31. 90 V_{AC} / 60 Hz, CH1 (Yellow): V_{CC(QR)}, CH3 (Blue): V_{DS(QR)}, CH4 (Green): I_{DS(QR)}

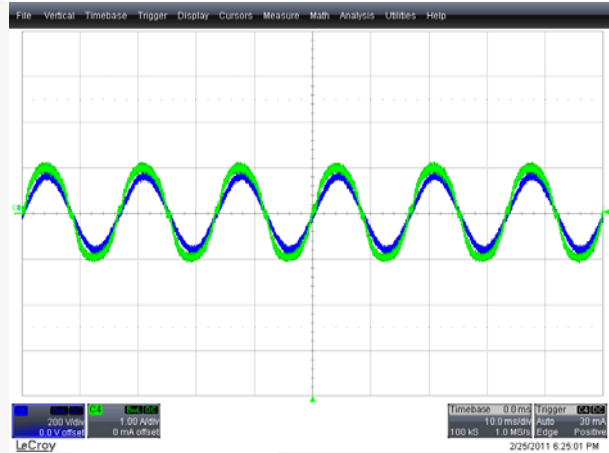


Figure 32. 115 V_{AC} / 60 Hz, CH1 (Yellow): V_{CC(QR)}, CH3 (Blue): V_{DS(QR)}, CH4 (Green): I_{DS(QR)}

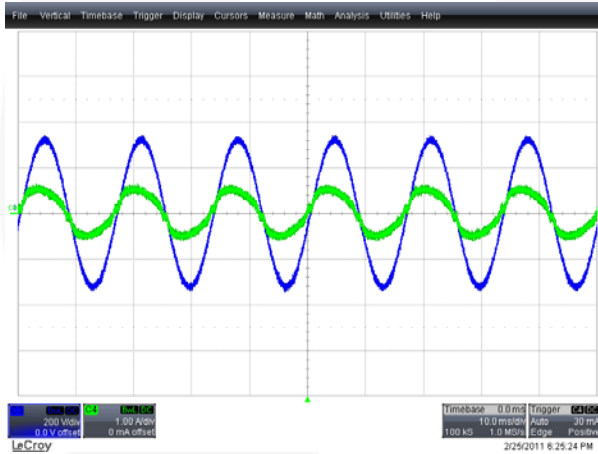


Figure 33. 230 V_{AC} / 60 Hz, CH3 (Blue): V_{IN}, CH4 (Green): I_{IN}

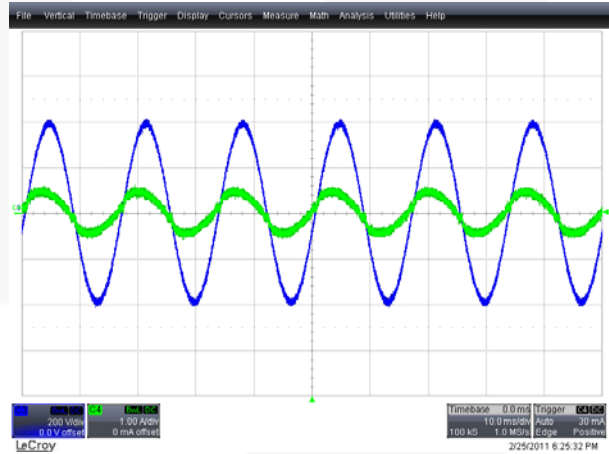


Figure 34. 277 V_{AC} / 60 Hz, CH3 (Blue): V_{IN}, CH4 (Green): I_{IN}

Figure 35 through Figure 38 show the V_{DS} and I_{DS} waveform of the MOSFET (PFC) on the board at different input voltage conditions.

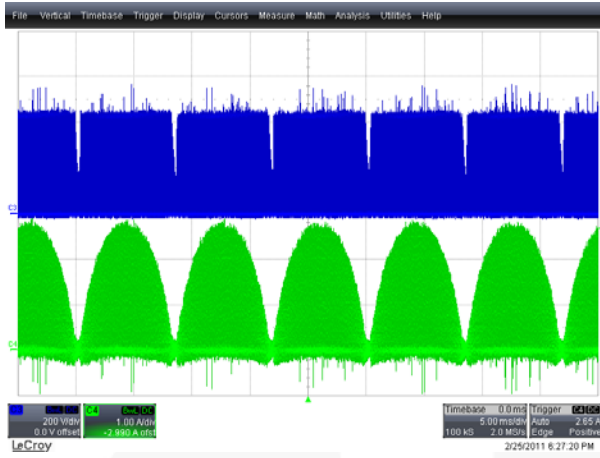


Figure 35. 90 V_{AC} / 60 Hz, CH3 (Blue): V_{DS} (PFC), CH4 (Green): I_{DS} (PFC)

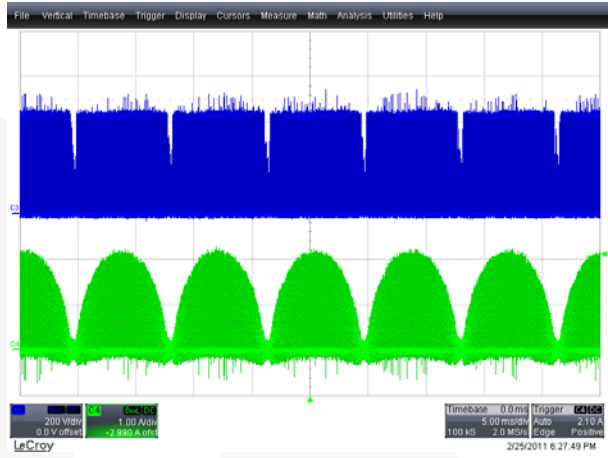


Figure 36. 115 V_{AC} / 60 Hz, CH3 (Blue): V_{DS} (PFC), CH4 (Green): I_{DS} (PFC)

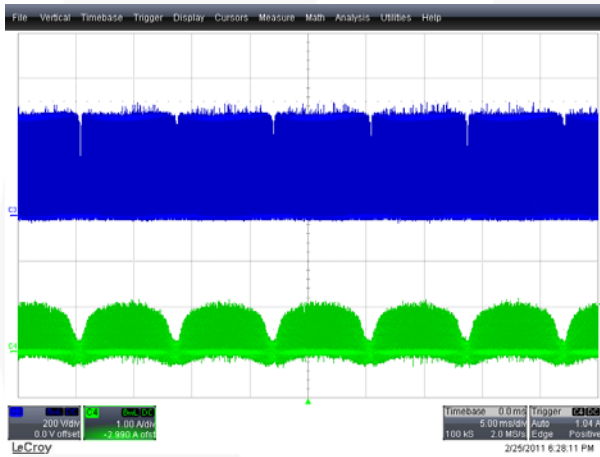


Figure 37. 230 V_{AC} / 60 Hz, CH3 (Blue): V_{DS} (PFC), CH4 (Green): I_{DS} (PFC)

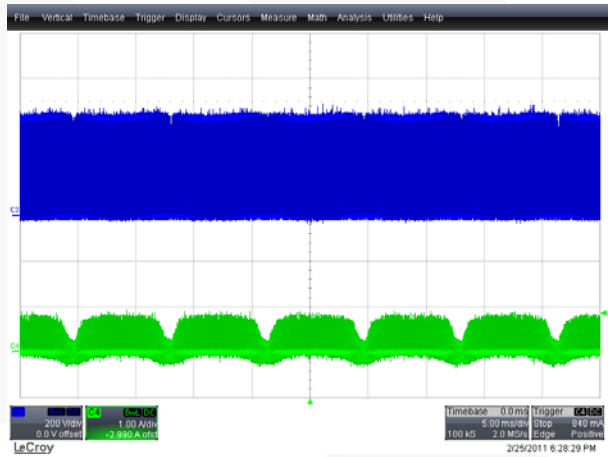


Figure 38. 277 V_{AC} / 60 Hz, CH3 (Blue): V_{DS} (PFC), CH4 (Green): I_{DS} (PFC)

Normal Operation of MOSFET (QR)

Figure 39 and Figure 40 show the V_{DS} and I_{DS} waveforms of the MOSFET (QR) at different input voltage conditions.

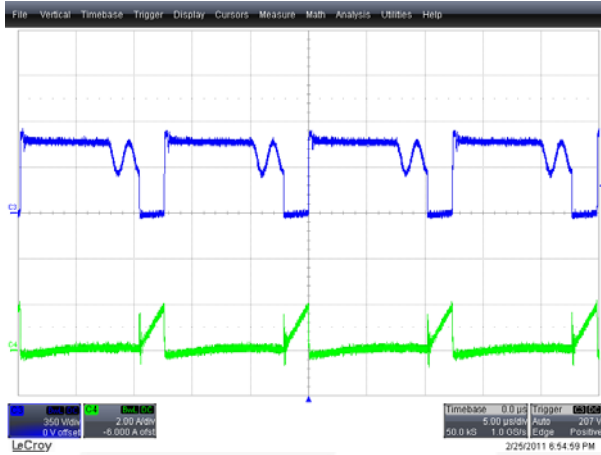


Figure 39. 90 V_{AC} / 60 Hz, CH3 (Blue): V_{DS(QR)}, CH4 (Green): I_{DS(QR)}

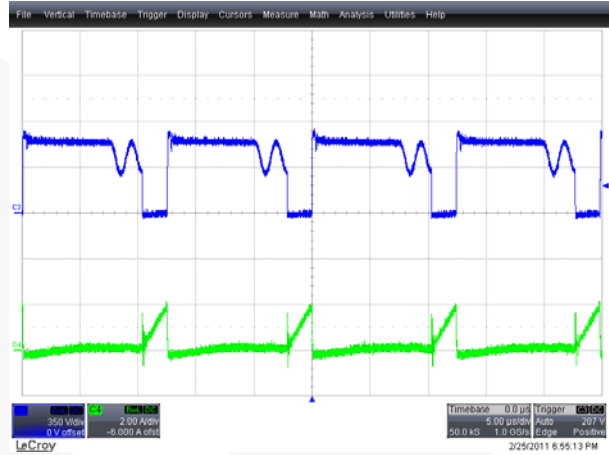


Figure 40. 277 V_{AC} / 60 Hz, CH3 (Blue): V_{DS(QR)}, CH4 (Green): I_{DS(QR)}

Normal Operation of Rectifier

Figure 41 and Figure 42 show the V_{AK} and I_{AK} waveforms of the rectifier at different input voltage conditions.

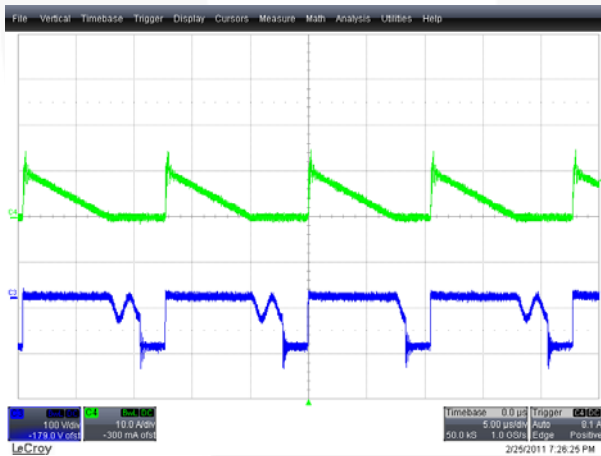


Figure 41. 90 V_{AC} / 60 Hz, CH3 (Blue): V_{AK(Rectifier)}, CH4 (Green): I_{AK(Rectifier)}

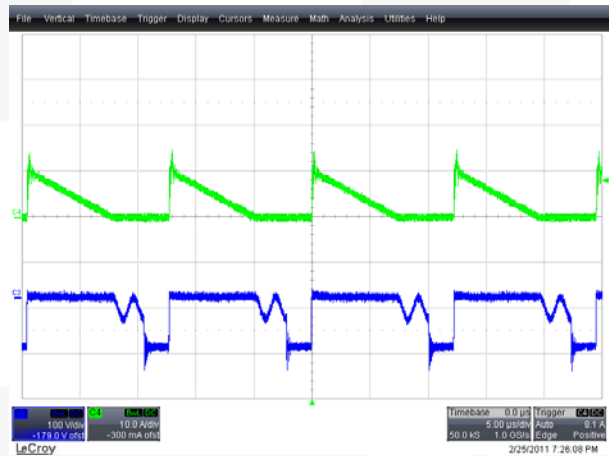


Figure 42. 277 V_{AC} / 60 Hz, CH3 (Blue): V_{AK(Rectifier)}, CH4 (Green): I_{AK(Rectifier)}

8.8. Short-Circuit Protection

Output-Short Protection

Figure 43 and Figure 44 show the V_{DS} and I_{DS} waveforms of the MOSFET (QR) at short-load condition. The IC repeats ON and OFF functions in this mode.

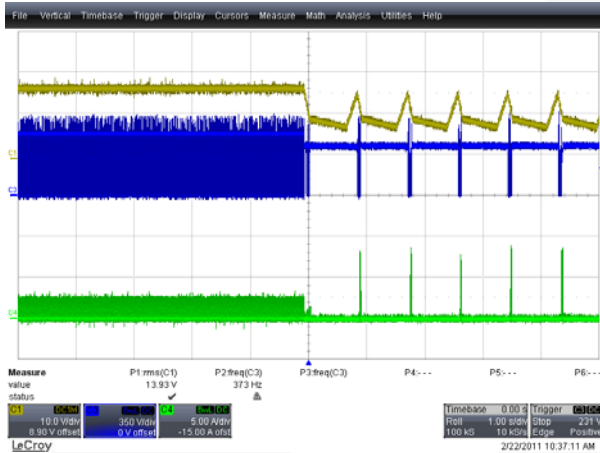


Figure 43. 90 V_{AC} / 60 Hz, CH1 (Yellow): $V_{CC(QR)}$, CH3 (Blue): $V_{DS(QR)}$, CH4 (Green): $I_{DS(QR)}$

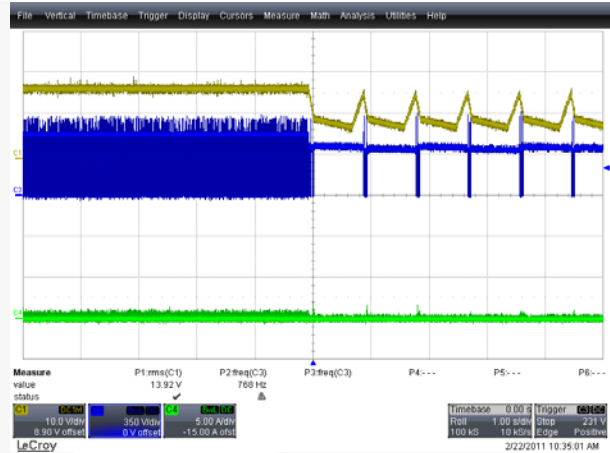


Figure 44. 277 V_{AC} / 60 Hz, CH1 (Yellow): $V_{CC(QR)}$, CH3 (Blue): $V_{DS(QR)}$, CH4 (Green): $I_{DS(QR)}$

Auto-Recovery Protection

Figure 45 and Figure 46 show the V_{DS} and I_{DS} waveforms of the MOSFET (QR) when short circuits at output load were removed.

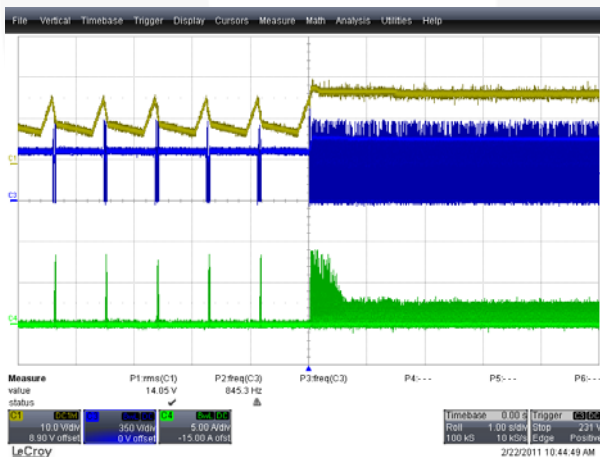


Figure 45. 90 V_{AC} / 60 Hz, CH1 (Yellow): $V_{CC(QR)}$, CH3 (Blue): $V_{DS(QR)}$, CH4 (Green): $I_{DS(QR)}$

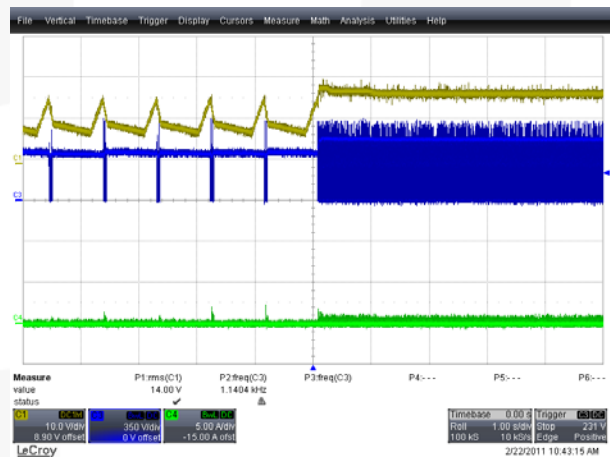


Figure 46. 277 V_{AC} / 60 Hz, CH1 (Yellow): $V_{CC(QR)}$, CH3 (Blue): $V_{DS(QR)}$, CH4 (Green): $I_{DS(QR)}$

8.9. Stress of the MOSFET & Rectifier

MOSFET Voltage Stress of PFC

Figure 47 through Figure 50 shows the voltage stress on the MOSFET of the PFC at startup time with rated load condition.

	90 V _{AC} / 60 Hz	115 V _{AC} / 60 Hz	230 V _{AC} / 60 Hz	277 V _{AC} / 60 Hz	Remark
MOSFET (V _{DS}) PFC	522 V	511 V	500 V	476 V	600 V / 16 A
MOSFET (I _{DS}) PFC	4.64 A	4.10 A	4.00 A	1.20 A	
MOSFET (V _{DS}) QR	686 V	700 V	686 V	668 V	800 V / 8 A
MOSFET (I _{DS}) QR	4.30 A	4.18 A	3.70 A	3.62 A	
Rectifier (V _{AK})	166 V	164 V	160 V	162 V	200 V / 40 A
Rectifier (I _{AK})	23.7 A	26.4 A	23.6 A	23.7 A	

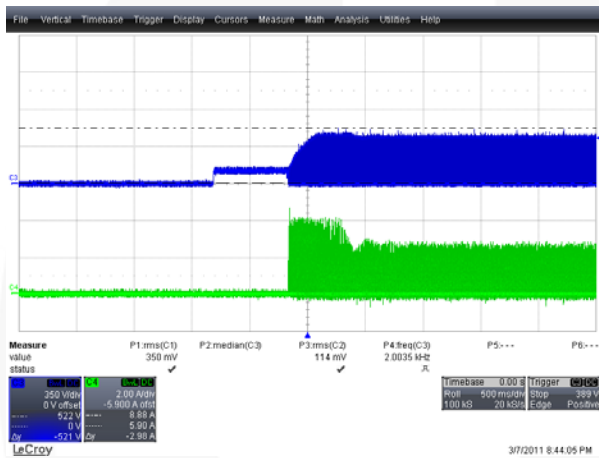


Figure 47. 90 V_{AC} / 60 Hz, CH3 (Blue): V_{DS}, CH4 (Green): I_{DS}

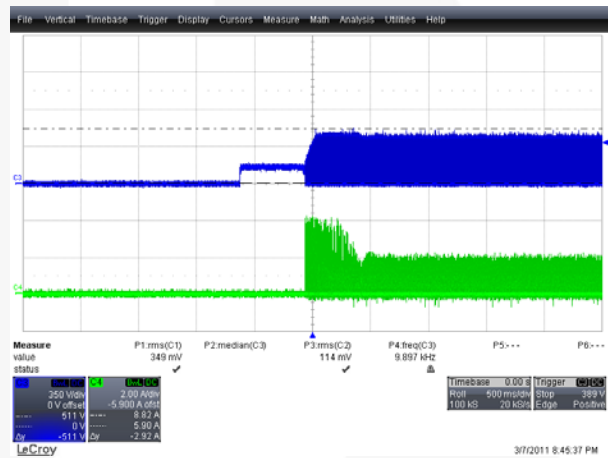


Figure 48. 115 V_{AC} / 60 Hz, CH3 (Blue): V_{DS}, CH4 (Green): I_{DS}

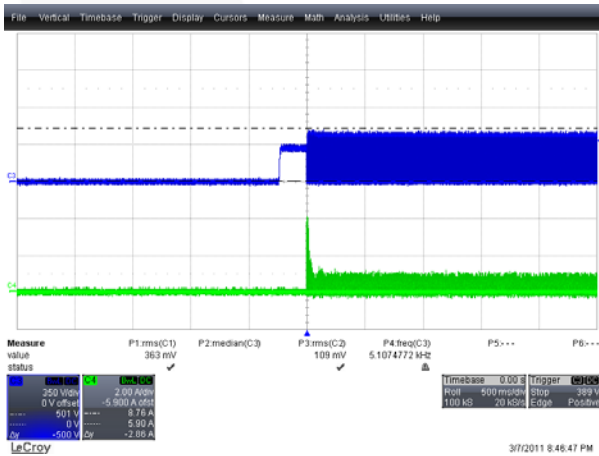


Figure 49. 230 V_{AC} / 60 Hz, CH3 (Blue): V_{DS}, CH4 (Green): I_{DS}

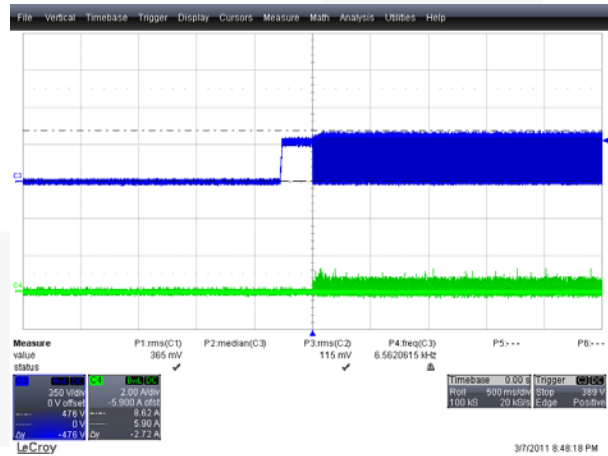


Figure 50. 277 V_{AC} / 60 Hz, CH3 (Blue): V_{DS}, CH4 (Green): I_{DS}

Figure 51 through Figure 54 show the current stress on the MOSFET of PFC at startup time with the rated load condition.

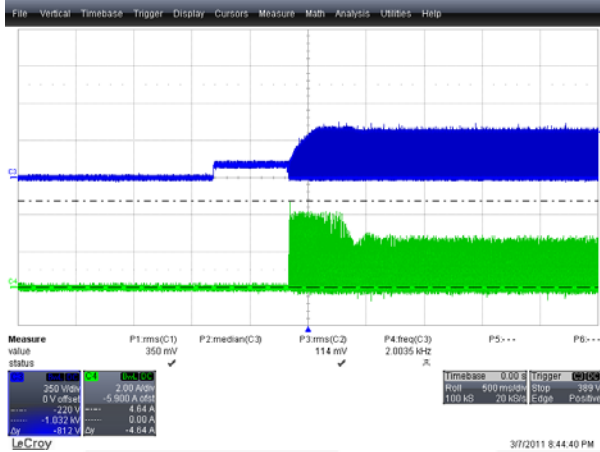


Figure 51. 90 V_{AC} / 60 Hz, CH3 (Blue): V_{DS}, CH4 (Green): I_{DS}

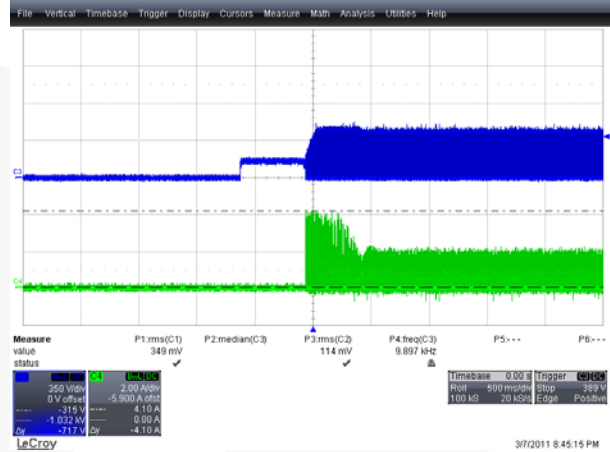


Figure 52. 115 V_{AC} / 60 Hz, CH3 (Blue): V_{DS}, CH4 (Green): I_{DS}

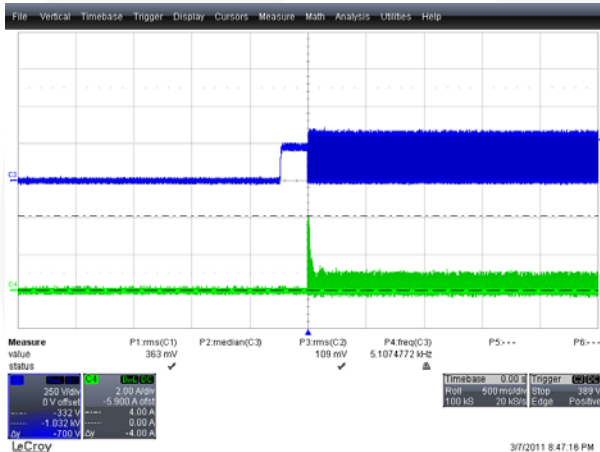


Figure 53. 230 V_{AC} / 60 Hz, CH3 (Blue): V_{DS}, CH4 (Green): I_{DS}

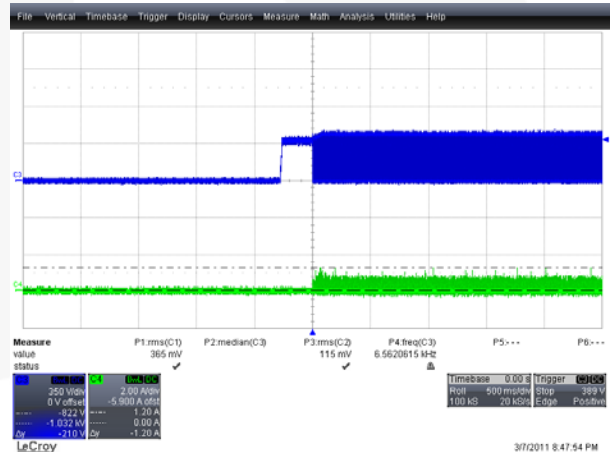


Figure 54. 277 V_{AC} / 60 Hz, CH3 (Blue): V_{DS}, CH4 (Green): I_{DS}

MOSFET Voltage Stress of QR Flyback

Figure 55 through Figure 58 shows the voltage stress on the MOSFET of the QR flyback circuit at startup time with the rated load condition.

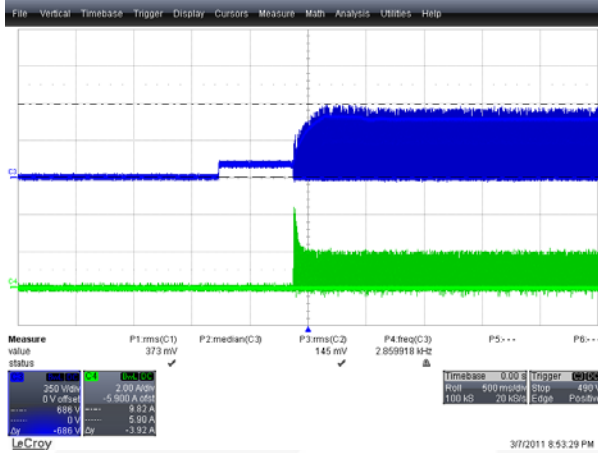


Figure 55. 90 V_{AC} / 60 Hz, CH3 (Blue): V_{DS}, CH4 (Green): I_{DS}

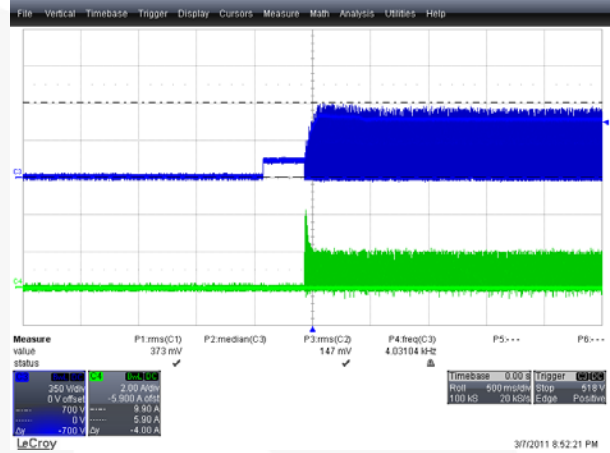


Figure 56. 115 V_{AC} / 60 Hz, CH3 (Blue): V_{DS}, CH4 (Green): I_{DS}

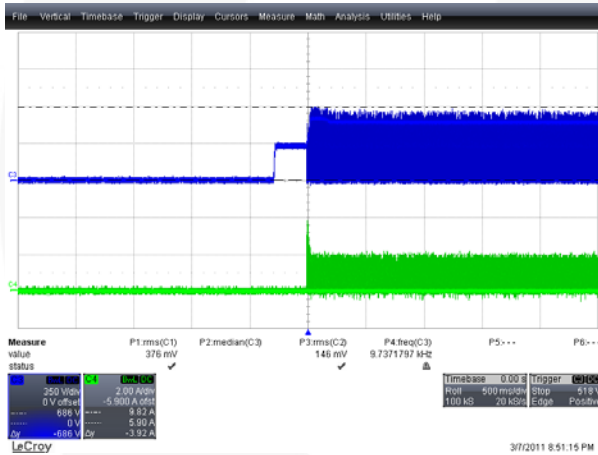


Figure 57. 230 V_{AC} / 60 Hz, CH3 (Blue): V_{DS}, CH4 (Green): I_{DS}

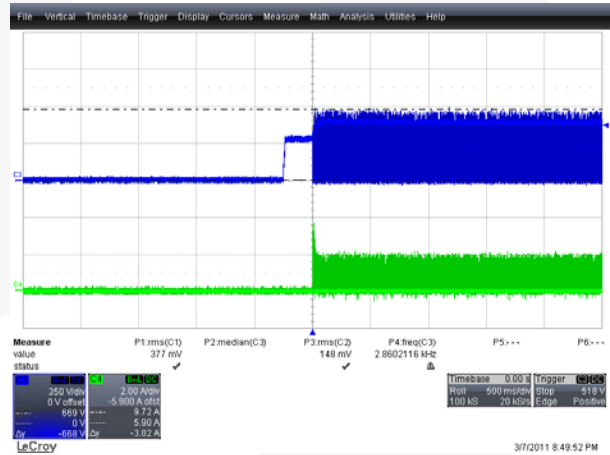


Figure 58. 277 V_{AC} / 60 Hz, CH3 (Blue): V_{DS}, CH4 (Green): I_{DS}

Figure 59 through Figure 62 show the current stress on the MOSFET of the QR flyback circuit at startup time with rated load condition.

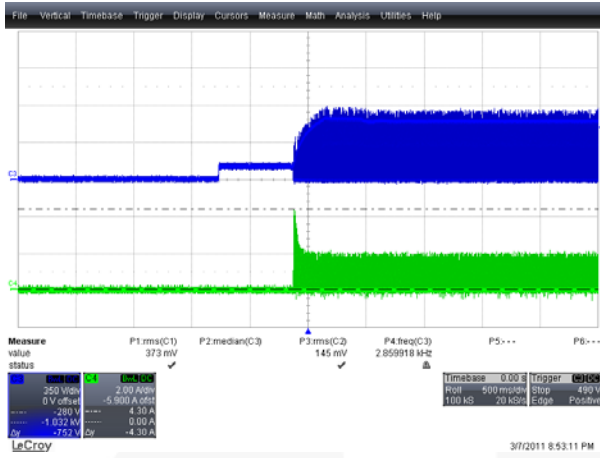


Figure 59. 90 V_{AC} / 60 Hz, CH3 (Blue): V_{DS}, CH4 (Green): I_{DS}

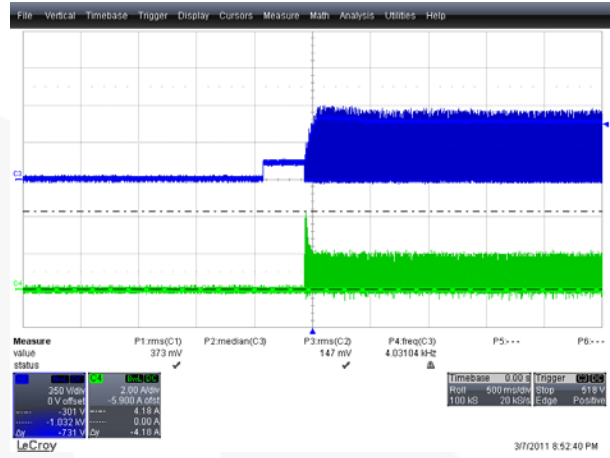


Figure 60. 115 V_{AC} / 60 Hz, CH3 (Blue): V_{DS}, CH4 (Green): I_{DS}

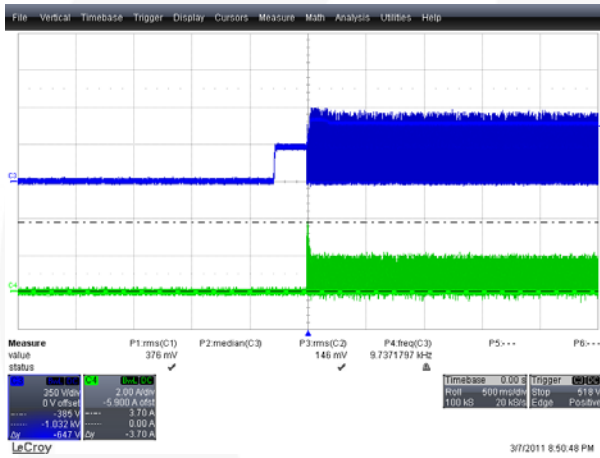


Figure 61. 230 V_{AC} / 60 Hz, CH3 (Blue): V_{DS}, CH4 (Green): I_{DS}

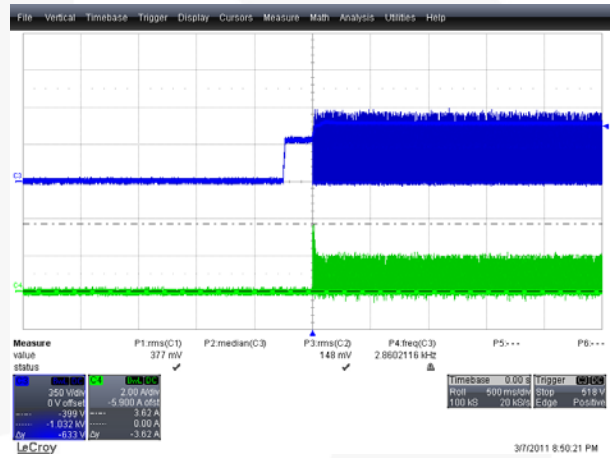


Figure 62. 277 V_{AC} / 60 Hz, CH3 (Blue): V_{DS}, CH4 (Green): I_{DS}

Rectifier Voltage Stress

Figure 63 through Figure 66 show the voltage stress on the output rectifier at startup time with the rated load condition.

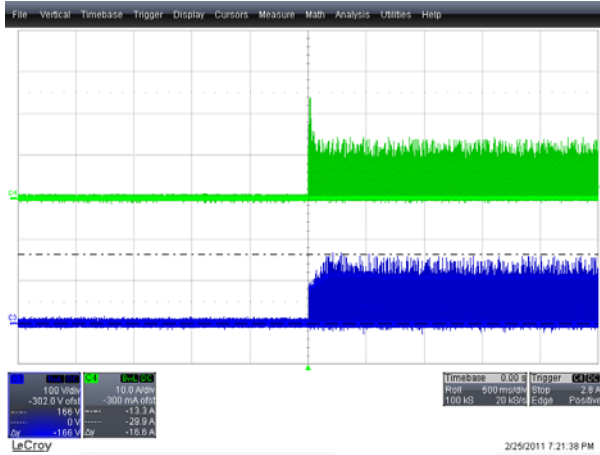


Figure 63. 90 V_{AC} / 60 Hz, CH3 (Blue): V_{AK}, CH4 (Green): I_{AK}

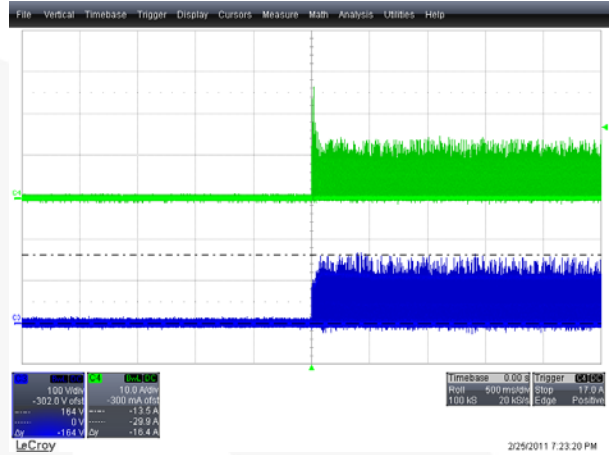


Figure 64. 115 V_{AC} / 60 Hz, CH3 (Blue): V_{AK}, CH4 (Green): I_{AK}

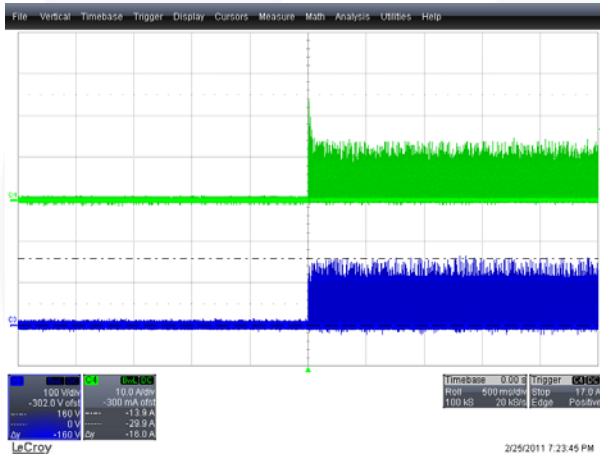


Figure 65. 230 V_{AC} / 60 Hz, CH3 (Blue): V_{AK}, CH4 (Green): I_{AK}

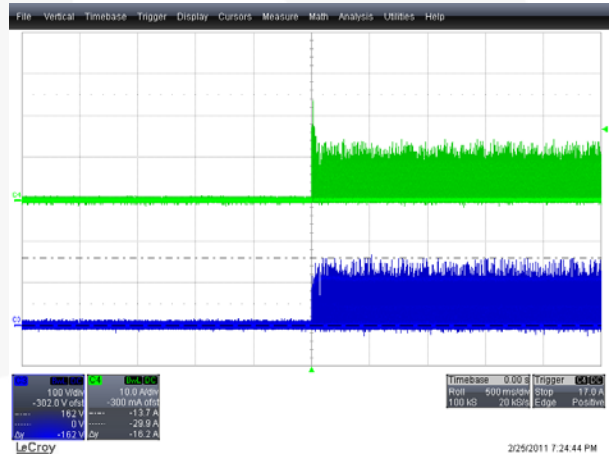


Figure 66. 277 V_{AC} / 60 Hz, CH3 (Blue): V_{AK}, CH4 (Green): I_{AK}

Rectifier Current Stress

Figure 67 through Figure 70 show the current stress on the output rectifier at startup time under the rated load condition.

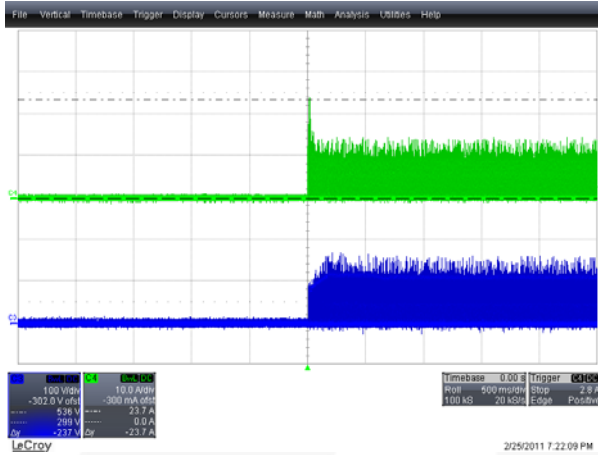


Figure 67. 90 V_{AC} / 60 Hz, CH3 (Blue): V_{AK}, CH4 (Green): I_{AK}

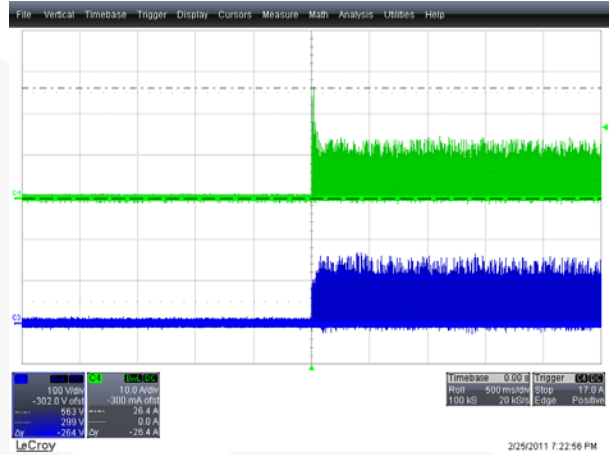


Figure 68. 115 V_{AC} / 60 Hz, CH3 (Blue): V_{AK}, CH4 (Green): I_{AK}

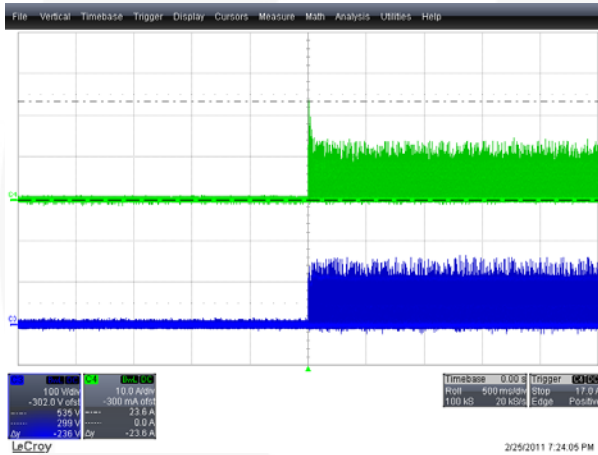


Figure 69. 230 V_{AC} / 60 Hz, CH3 (Blue): V_{AK}, CH4 (Green): I_{AK}

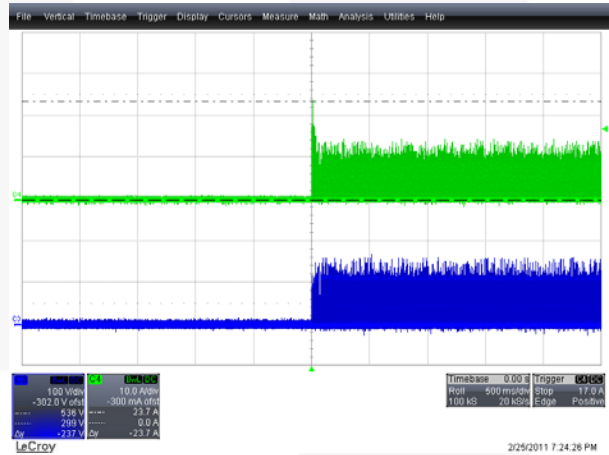


Figure 70. 277 V_{AC} / 60 Hz, CH3 (Blue): V_{AK}, CH4 (Green): I_{AK}

8.10. Electromagnetic Interference (EMI)

All measurements were conducted in observance of CISPR22 criteria.

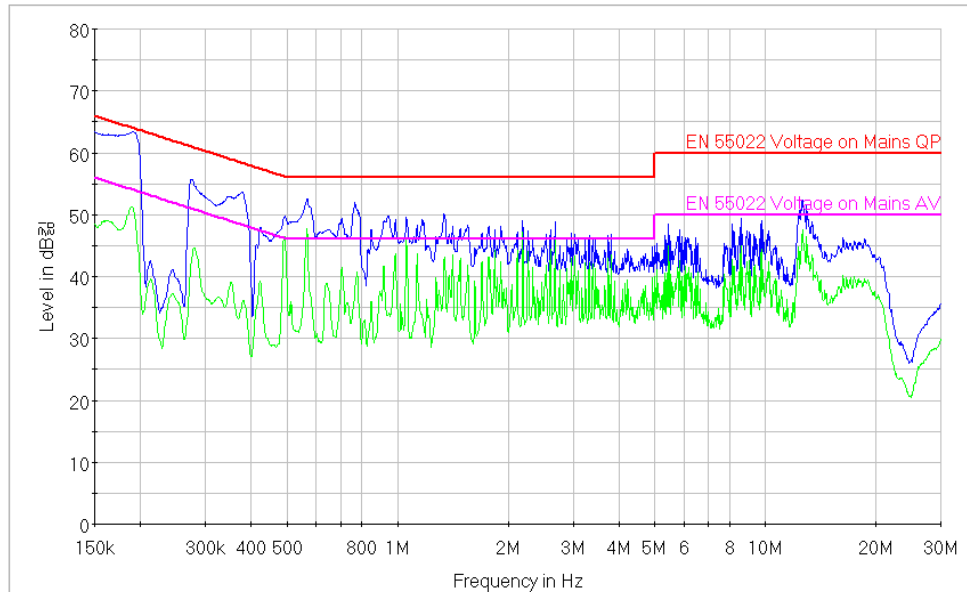


Figure 71. EMI Results (Conducted Emission-Line at 220 V_{AC}, Full-Load (24 V / 2.9 A))

9. Revision History

Rev.	Date	Description
1.0.0	May 2012	Initial Release
1.0.1	Oct. 2012	Modified, edited, formatted document. Changed User Guide number from FEB-L008 to FEBFL6961FL6300_L08U070A

WARNING AND DISCLAIMER

Replace components on the Evaluation Board only with those parts shown on the parts list (or Bill of Materials) in the Users' Guide. Contact an authorized Fairchild representative with any questions.

This board is intended to be used by certified professionals, in a lab environment, following proper safety procedures. Use at your own risk. The Evaluation board (or kit) is for demonstration purposes only and neither the Board nor this User's Guide constitute a sales contract or create any kind of warranty, whether express or implied, as to the applications or products involved. Fairchild warrants that its products meet Fairchild's published specifications, but does not guarantee that its products work in any specific application. Fairchild reserves the right to make changes without notice to any products described herein to improve reliability, function, or design. Either the applicable sales contract signed by Fairchild and Buyer or, if no contract exists, Fairchild's standard Terms and Conditions on the back of Fairchild invoices, govern the terms of sale of the products described herein.

DISCLAIMER

FAIRCHILD SEMICONDUCTOR RESERVES THE RIGHT TO MAKE CHANGES WITHOUT FURTHER NOTICE TO ANY PRODUCTS HEREIN TO IMPROVE RELIABILITY, FUNCTION, OR DESIGN. FAIRCHILD DOES NOT ASSUME ANY LIABILITY ARISING OUT OF THE APPLICATION OR USE OF ANY PRODUCT OR CIRCUIT DESCRIBED HEREIN; NEITHER DOES IT CONVEY ANY LICENSE UNDER ITS PATENT RIGHTS, NOR THE RIGHTS OF OTHERS.

LIFE SUPPORT POLICY

FAIRCHILD'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF FAIRCHILD SEMICONDUCTOR CORPORATION.

As used herein:

- Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, or (c) whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in significant injury to the user.
- A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

ANTI-COUNTERFEITING POLICY

Fairchild Semiconductor Corporation's Anti-Counterfeiting Policy. Fairchild's Anti-Counterfeiting Policy is also stated on our external website, www.fairchildsemi.com, under Sales Support.

Counterfeiting of semiconductor parts is a growing problem in the industry. All manufacturers of semiconductor products are experiencing counterfeiting of their parts. Customers who inadvertently purchase counterfeit parts experience many problems such as loss of brand reputation, substandard performance, failed applications, and increased cost of production and manufacturing delays. Fairchild is taking strong measures to protect ourselves and our customers from the proliferation of counterfeit parts. Fairchild strongly encourages customers to purchase Fairchild parts either directly from Fairchild or from Authorized Fairchild Distributors who are listed by country on our web page cited above. Products customers buy either from Fairchild directly or from Authorized Fairchild Distributors are genuine parts, have full traceability, meet Fairchild's quality standards for handling and storage and provide access to Fairchild's full range of up-to-date technical and product information. Fairchild and our Authorized Distributors will stand behind all warranties and will appropriately address any warranty issues that may arise. Fairchild will not provide any warranty coverage or other assistance for parts bought from Unauthorized Sources. Fairchild is committed to combat this global problem and encourage our customers to do their part in stopping this practice by buying direct or from authorized distributors.

EXPORT COMPLIANCE STATEMENT

These commodities, technology, or software were exported from the United States in accordance with the Export Administration Regulations for the ultimate destination listed on the commercial invoice. Diversion contrary to U.S. law is prohibited.

U.S. origin products and products made with U.S. origin technology are subject to U.S. Re-export laws. In the event of re-export, the user will be responsible to ensure the appropriate U.S. export regulations are followed.

ON Semiconductor and  are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor
19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free
USA/Canada
Europe, Middle East and Africa Technical Support:
Phone: 421 33 790 2910
Japan Customer Focus Center
Phone: 81-3-5817-1050

ON Semiconductor Website: www.onsemi.com
Order Literature: <http://www.onsemi.com/orderlit>
For additional information, please contact your local
Sales Representative