

ON Semiconductor

Is Now

onsemi™

To learn more about onsemi™, please visit our website at
www.onsemi.com

onsemi and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.

Unidirectional versus Bidirectional Protection

Prepared by: Robert Ashton
ON Semiconductor



ON Semiconductor®

<http://onsemi.com>

APPLICATION NOTE

Protection products such as transient voltage suppressors (TVS) are often described as unidirectional and bidirectional. This terminology has often led to confusion. The most common misconception is that unidirectional devices only provide protection for positive or negative stresses, not both. This is not true. The vast majority of unidirectional TVS products provide protection for both stress polarities. This application note will clarify the meanings of unidirectional and bidirectional protection products and give simple examples of their use.

We will begin with the following definitions and then discuss each type in more detail.

Unidirectional TVS: A TVS device with asymmetrical current versus voltage (I-V) properties. A unidirectional TVS is best suited for protecting circuit nodes whose signals

are **unidirectional** or always above or below the reference voltage, usually ground.

Bidirectional TVS: A TVS device with symmetrical I-V properties. A bidirectional TVS is best suited for protecting electrical nodes whose signals are **bidirectional** or can have voltage levels both above and below the reference voltage, usually ground

Unidirectional TVS Devices

The simplest unidirectional TVS device is a Zener or avalanche diode as shown in Figure 1. For negative voltage from cathode to anode the TVS has high conductivity above a forward diode drop. For positive voltages there is high impedance up to the reverse bias breakdown voltage. Above the reverse bias breakdown voltage the diode has low resistance.

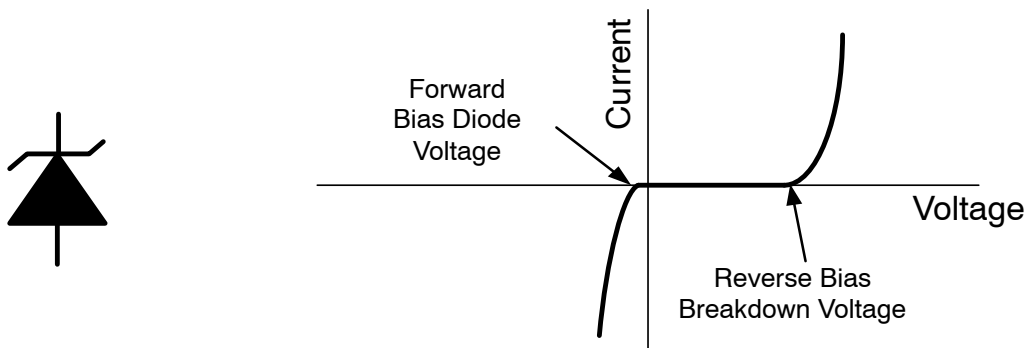


Figure 1. Unidirectional TVS Protection Properties

An application of a unidirectional TVS device is illustrated in Figure 2. A circuit has a sensitive input line which carries a normal signal which is always a positive voltage, for example a 0 to 5 V signal. The normal signal range is shown on the right side of Figure 2. If voltage on the input line goes significantly below 0 V or above 5 V damage

can occur to the circuit, as shown in Figure 2. A unidirectional TVS can be placed between the input and ground to direct current to ground and clamp the voltage below a value that will create damage to the sensitive circuit. The required I-V properties of the unidirectional TVS are shown in Figure 2.

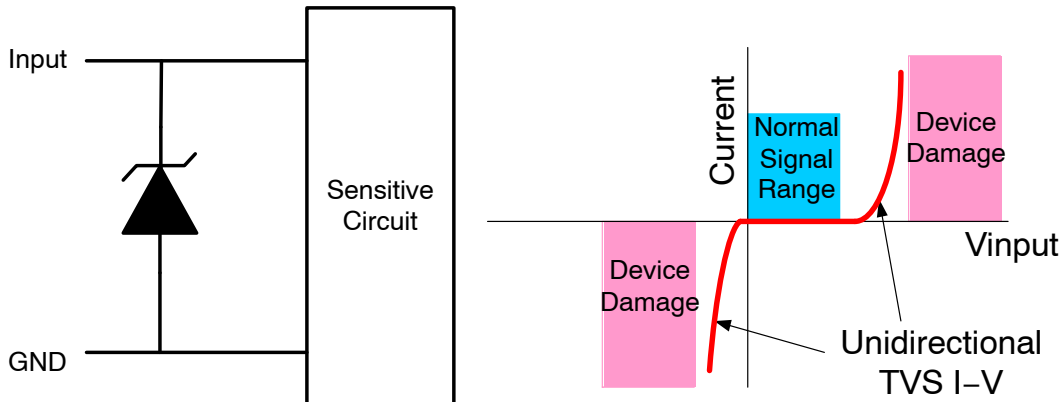


Figure 2. Application of a Unidirectional TVS Device

Note that for circuit nodes whose voltage is always below the reference voltage a unidirectional device can provide protection simply by switching the terminal leads.

positive and negative voltage the impedance is high up to the reverse bias breakdown voltage plus a forward bias diode drop. This is shown on the right side of Figure 3.

Bidirectional TVS Devices

A simple example of a TVS device is a pair of back to back Zener or avalanche diodes, as shown in Figure 3. For both

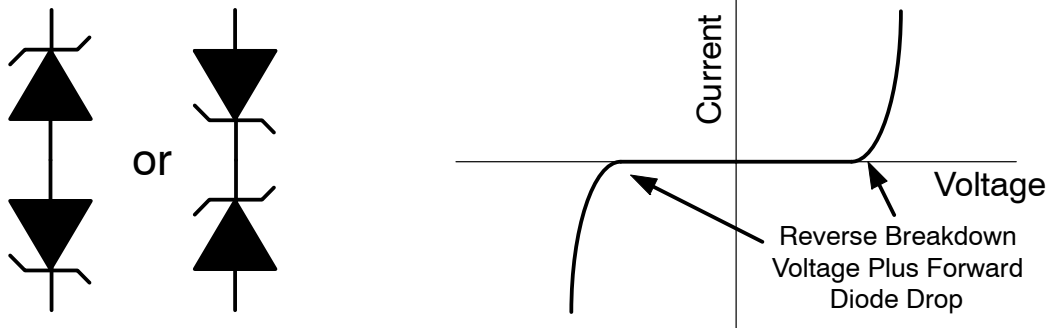


Figure 3. Bidirectional Protection Properties

An application of a bidirectional TVS device is illustrated in Figure 4. A circuit has a sensitive input line which carries a normal signal which ranges symmetrically above and below ground, ± 12 V for example. The normal signal range is shown on the right side of Figure 4. If voltage on the input line goes significantly below -12 V or above $+12$ V damage

can occur to the circuit, also shown in Figure 4. A bidirectional TVS can be placed between the input and ground to direct current to ground, clamping the voltage below voltages that can cause damage. The required I-V properties of the bidirectional TVS are shown in Figure 4.

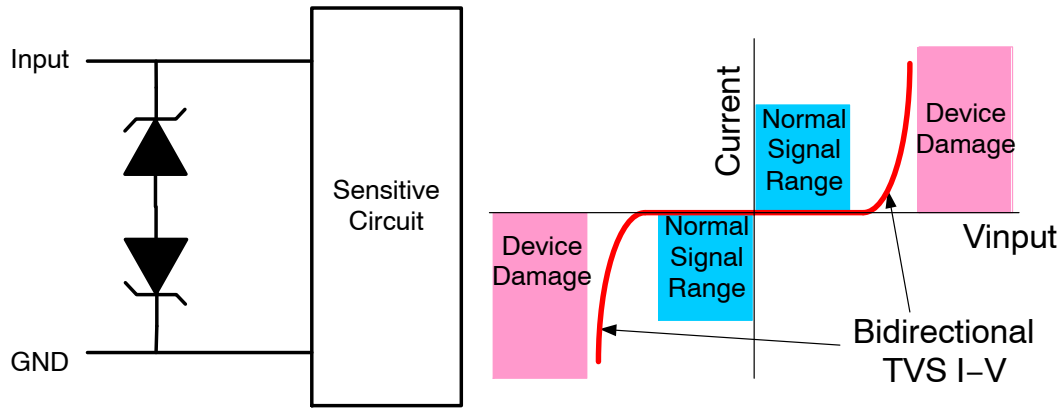



Figure 4. Application of a Bidirectional TVS Device

Summary

The choice of a unidirectional or bidirectional TVS product depends on the properties of the circuit being protected. Unidirectional TVS products protect signal or DC

power nodes with unidirectional signal swings and bidirectional TVS products protect signal or AC power nodes with bidirectional signal swings.

ON Semiconductor and  are registered trademarks of Semiconductor Components Industries, LLC (SCILLC). SCILLC reserves the right to make changes without further notice to any products herein. SCILLC makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does SCILLC assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. "Typical" parameters which may be provided in SCILLC data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. SCILLC does not convey any license under its patent rights nor the rights of others. SCILLC products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the SCILLC product could create a situation where personal injury or death may occur. Should Buyer purchase or use SCILLC products for any such unintended or unauthorized application, Buyer shall indemnify and hold SCILLC and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that SCILLC was negligent regarding the design or manufacture of the part. SCILLC is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:
 Literature Distribution Center for ON Semiconductor
 P.O. Box 5163, Denver, Colorado 80217 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free
 USA/Canada
Europe, Middle East and Africa Technical Support:
 Phone: 421 33 790 2910
Japan Customer Focus Center
 Phone: 81-3-5773-3850

ON Semiconductor Website: www.onsemi.com
Order Literature: <http://www.onsemi.com/orderlit>
 For additional information, please contact your local Sales Representative