

ON Semiconductor

Is Now

onsemi™

To learn more about onsemi™, please visit our website at
www.onsemi.com

onsemi and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.



Product Preview

Secondary Side Regulated LED Driver with the NCL30488

Description

This paper focuses on the experimental results of a LED driver controlled by the secondary side regulated version of the NCL30488.

Introduction

The NCL30488 [1] is a power factor corrected controller with primary side constant voltage (CV) and constant current (CC) control suitable for flyback, buck-boost or SEPIC converters. The NCL30488 is housed in an SOIC 8 package and targets high-performance LED drivers. These controller integrate a proprietary circuit for power factor correction and constant current control allowing to achieve a power factor above 0.9 and total harmonic distortion below 10% for universal mains input. This controller is normally primary side regulated, but the version (*TBD*) is compatible with secondary side regulation. In this version, the COMP pin features a pullup resistor to the internal reference voltage rail and allows directly connecting an optocoupler collector to the pin. The current-mode, quasi-resonant architecture of this controller optimizes the efficiency by turning on the MOSFET when the drain-source voltage is minimal (valley). The valley lockout and frequency foldback circuitry maintain high-efficiency performance in in light load during constant-voltage regulation.

In addition, the circuit contains a set of powerful protections to ensure a robust LED driver design:

- Output over voltage protection
- Cycle-by-cycle peak current limit
- Winding and output diode short circuit protection
- Output short circuit protection
- V_{CC} pin over voltage protection
- Floating/short pin detection: the circuit can detect most of these situations which is of great help to pass safety tests.

APPLICATION NOTE

LED DRIVER SPECIFICATION

Table 1. LED DRIVER SPECIFICATION

Description	Symbol	Value	Units
LED DRIVER SPECIFICATION			
Minimum input voltage	$V_{in,min}$	85	V rms
Maximum input voltage	$V_{in,max}$	277	V rms
Power factor	PF	> 0.9	
Minimum output voltage	$V_{out,min}$	24	V
Output voltage for constant voltage regulation	$V_{out,max}$	40	V
Output voltage level to activate the over voltage protection	$V_{out(OVP)}$	52	V
Output current (nominal)	I_{out}	0.5	A
Output rectifier voltage drop (estimated)	V_f	0.6	V
OTHER PARAMETERS			
Estimated efficiency	η	85	%
Estimated lump capacitor	C_{lump}	50	pF
Switching frequency at $P_{out,max}$, $V_{in} = 115$ V rms	F_{sw}	65	kHz

The LED driver is designed to meet the specifications of Table 1.

DESCRIPTION OF THE BOARD

This secondary side regulated LED driver has been designed using the guidelines provided in the application notes AND9200/D [2] and ANDXXXX/D [3]. Figure 1 shows the schematic of the board with the NCL30488 implanted.

There are specific considerations for secondary side design.

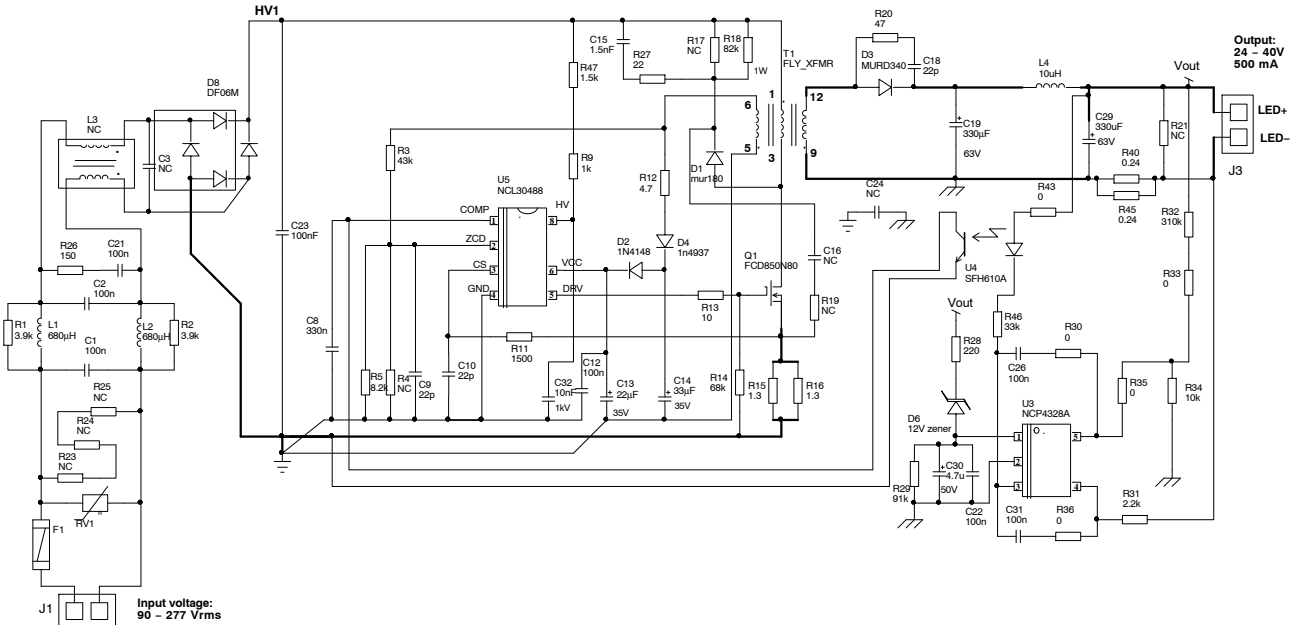


Figure 1. Evaluation Board Schematic for the NCL30 488

The MOSFET current sense resistors R15 and R16 set the output current limit from the primary side. This current limit must be set higher than the output nominal current. If not, the primary side current control implemented in the NCL30488 will take over the regulation and limit the output current. For this design, the maximum output current is set to:

$$I_{out} = \frac{V_{REF}}{2N_{sp}R_{sense}} \quad (eq. 1)$$

With:

- V_{REF} : constant current reference voltage of the NCL30488 (see datasheet)
- N_{sp} : secondary to primary turns ratio: $N_{sp} = N_s / N_p$
- R_{sense} : MOSFET current sense resistors

$$I_{out} = \frac{0.33}{2 \times 0.469 \times 0.65} = 546 \text{ mA} \quad (eq. 2)$$

The NCP4328A is chosen for the secondary side Constant Voltage (CV) and Constant Current (CC) regulation. This part has a very low threshold voltage for CC operation: this helps decreasing the power dissipated in the secondary side sense resistors R40 and R45.

The output current for CC regulation is set to $I_{out,nom} = 500 \text{ mA}$. The secondary side sense resistors are calculated with:

$$R_{sense,sec} = \frac{V_{REF(CC)}}{I_{out,nom}} = \frac{0.0625}{0.5} = 0.125 \Omega \quad (eq. 3)$$

With:

- $R_{sense,sec}$: secondary side current sense resistor
- $V_{REF(CC)}$: NCP4328 voltage reference for the constant current operation

The output voltage $V_{out,nom}$ is set to 40 V by R_{32} , R_{33} and R_{34} .

R_{34} chosen value is 10 k Ω to have small current in the resistor bridge (125 μA). Then R_{33} and R_{34} values are calculated:

$$R_{32} + R_{33} = \left(\frac{V_{out,nom}}{V_{REF(CV)}} - 1 \right) R_{34} \quad (eq. 4)$$

With

- $V_{REF(CV)}$: NCP4328 voltage reference for the CV operation

AND90015

A type 2 compensator is built around the NCP4328 to stabilize the power supply. R_{46} set the mid-band gain of the compensator to have a crossover frequency f_c around 10 Hz. The internal pullup resistor of the NCL30488 R_{pullup} forms a pole with C_8 to filter the line frequency. This pole is set to 26 Hz in this design. This pole is common to both the CC and the CV loop.

The zeroes of the CV loop and the CC loop are selected to provide enough phase boost to have a phase margin above 45° over the load range.

The document “Designing a type 2 compensator with the NCP4328/4352” [5] explains how to calculate the compensation network for the NCP4328. The Zener diode D_6 limits the voltage supplied to the NCP4328 as the max rating for this controller is 35 V.

The varistor RV1 protects the power supply in case of line surge.

The resistors R1 and R2 damp the oscillation caused by the self-resonant frequency of the coils L1 and L2. This is only for EMI filtering purpose.

The damper circuit formed by R26 and C21 reduces the peaking of the output impedance of the L-C EMI filter composed of L1, L2 and C2.

R3, R4 and R5 set the output overvoltage fast protection to 52 V. Also, these resistors together with C9 capacitor delay the zero-voltage crossing event and help to tune the turn-on instant when the drain voltage is in the valley.

R11 is the line feedforward resistor that compensates the output current variation caused by the propagation delays (for primary side constant current control).

R9 and R47 limit the voltage on HV pin in case of surge.

R18, R27 and C15 clamp the drain voltage excursion when the MOSFET turns off.

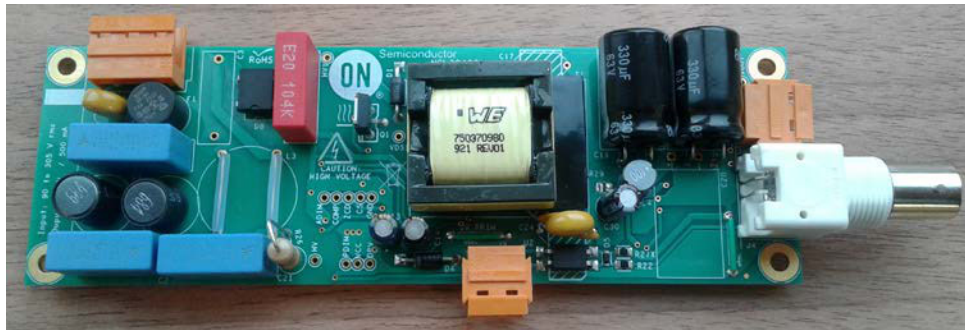


Figure 2. Photograph of the EVB Top Side

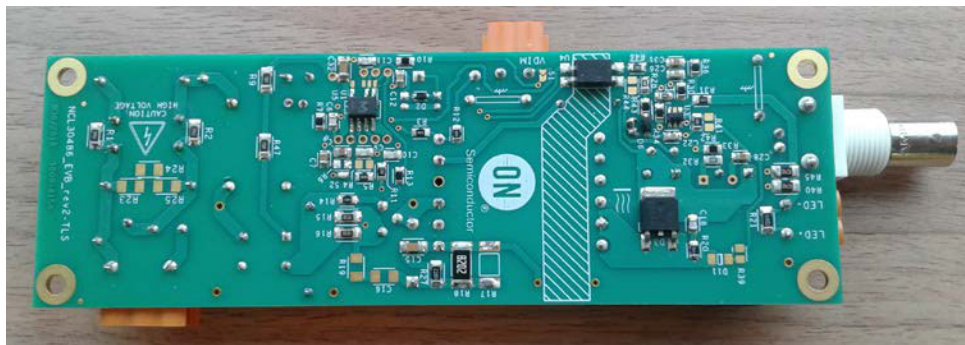


Figure 3. Photograph of the EVB Bottom Side



Figure 4. EVB Side Picture: Board Height is 15 mm

OUTPUT VOLTAGE AND CURRENT REGULATION

An electronic load in constant resistance mode is used to obtain the CC/CV characteristic of the flyback converter (output voltage versus output current) controlled by the NCL30488. The CC/CV curve is plotted for various input voltage: 100, 120, 230 and 277 Vrms.

Thanks to the secondary side controller, the output voltage and output current are regulated very precisely.

The output current regulation is estimated by calculating the median value of the output current $I_{out(mean)}$ considering the maximum and the minimum value measured:

$$I_{out(mean)} = \frac{I_{out(max)} + I_{out(min)}}{2} \quad (eq. 5)$$

Then, we calculate the gap from the maximum value to the median value to deduce the current regulation expressed as a percentage of $I_{out(mean)}$:

$$\delta I_{out} = 100 \frac{\Delta I_{out}}{I_{out(mean)}} = 100 \frac{I_{out(max)} - I_{out(min)}}{I_{out(mean)}} \quad (eq. 6)$$

For the measurements shown in Figure 6, we have the following results:

$$I_{out(mean)} = 510.4 \text{ mA}$$

$$I_{out(max)} = 512 \text{ mA}$$

$$I_{out(min)} = 508.8 \text{ mA}$$

$$\delta I_{out} = \pm 0.3 \%$$

The output current regulation is $\pm 0.3 \%$ with line and load variation included.

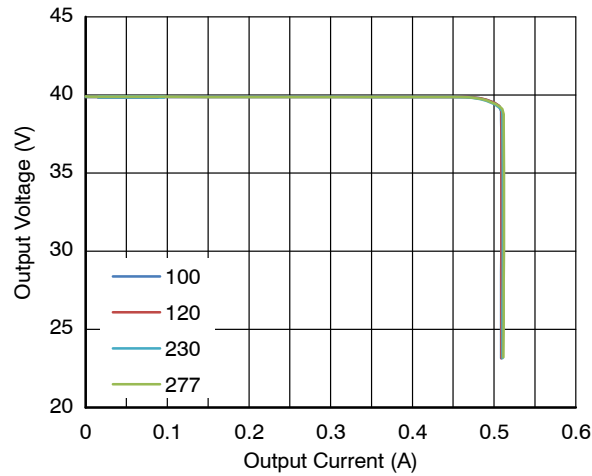


Figure 6. Line and Load Regulation for I_{out}

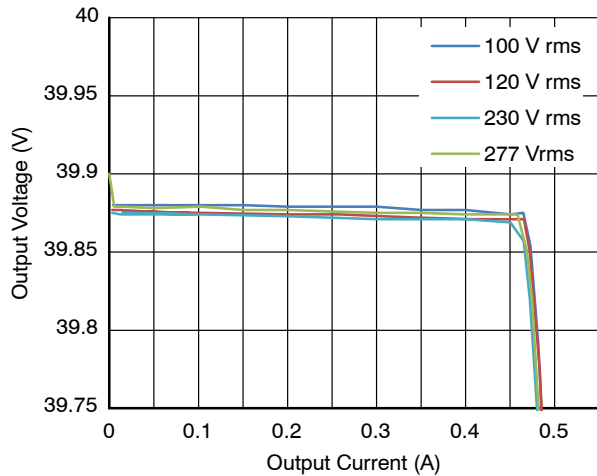


Figure 5. CV Curve Zoom for $V_{in} = 100$ to 277 V rms

In the same way, we can estimate the output voltage regulation:

$$V_{out(mean)} = 39.88 \text{ V}$$

$$V_{out(max)} = 39.90 \text{ V}$$

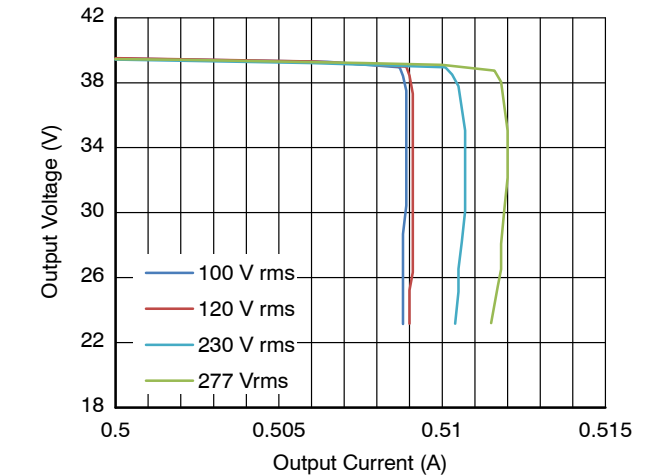


Figure 7. CC Curve Zoom for $V_{in} = 100$ to 277 V rms

$$V_{out(min)} = 39.86 \text{ V}$$

$$\delta V_{out} = 0.05\%$$

The constant voltage regulation is $\pm 0.05\%$ over the input voltage range.

EFFICIENCY, POWER FACTOR AND TOTAL HARMONIC DISTORTION

The measurements were made after the board was operated during 5 minutes at maximum output load (20 W), low line, with an open frame and at ambient temperature.

The input power, the PF and the THD were measured with the power meter 66202 from Chroma.

The output current and the output voltage were measured using the electronic load with the output voltage sensed at the board output. The electronic load was used in constant resistance mode and programmed to draw 100%, 75%, 50% and 25% of the board maximum output power. Figure 8,

Figure 9 and Figure 10 summarizes the measurements results.

With an average efficiency of 88.3% at 115 V rms and 88.1% at 230 V rms, the board exceed the Tier 2 of the Code of Conduct on Energy Efficiency of External Power Supplies.

The THD is also excellent and stays below 10% down when the output load is 25% of the maximum rated power over the line range.

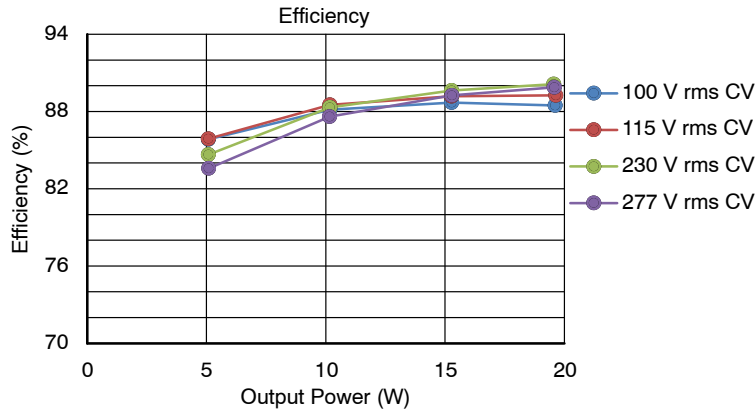


Figure 8. Efficiency

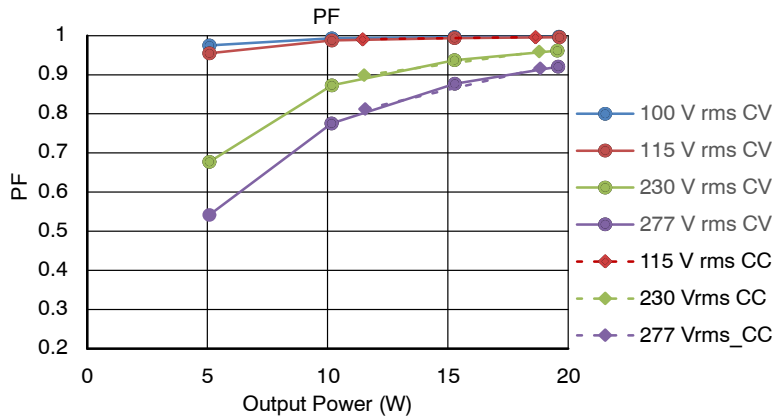


Figure 9. Power Factor

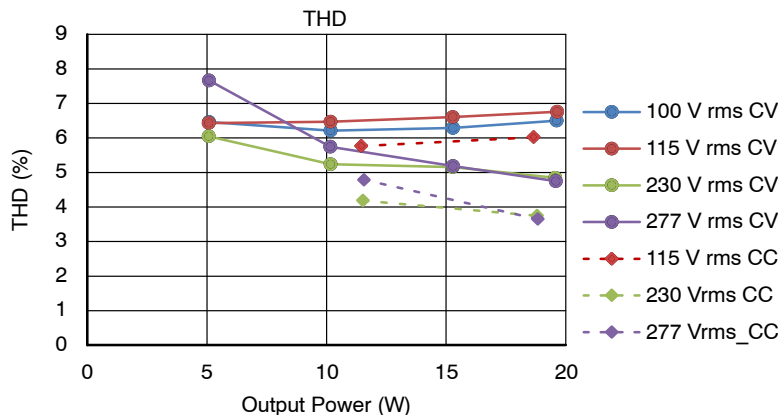


Figure 10. THD for V_{in} = 100 to 277 V rms

TRANSIENT LOAD STEP

Figure 11 and Figure 12 show the output voltage and the output current variation when the output load is varied abruptly from 100% to 25% and from 100% to 50% of the maximum output load (20 W), the electronic load being in constant resistance mode. For the 100% to 25% output load

variation, the output voltage overshoot is contained at 46.2 V and the voltage undershoot is at 33.4 V, which represents respectively 15.5% and -16.5% of the output voltage regulation level.

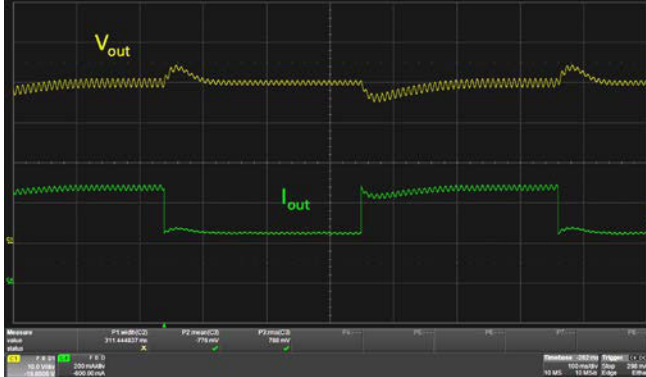


Figure 11. Transient Load Step Response from 100% to 50% Output Load



Figure 12. Transient Load Step Response from 100% to 25% Output Load

STANDBY POWER CONSUMPTION

Thanks to the standby mode featured by the NCL30488, the power consumption when no load is connected to the board is small. Table 2 summarizes the results obtained.

Table 2. STANDBY POWER MEASUREMENT

Input Voltage (V rms)	Input Power (mW)
277	127
230	113

CONCLUSION

This application note has shown the experimental results of a LED driver controlled by the NCL30488 secondary side regulation compatible version.

A very good regulation of the output current and the output voltage is obtained as well as excellent THD.

AND90015

Table 3. BOM FOR NCL30488 20 W SSR EVB

Reference	QTY	Description	Value / Tol	Footprint	Manufacturer	Manufacturer Part Number
RV1	1	Varistor	420 V	through hole	Würth	820474211
F1	1	Fuse, 300 Vac	1 A			
L1, L2	3	Radial coil	680 μ H, 340 mA	through hole	Coilcraft	RFB1010-152L
L3	0	common mode choke	Not connected	through hole	Würth	7446622002
L4	1	Inductor	10 μ H	through hole	Würth	744779100
D1	0	Ultra fast diode	MUR180	axial	ON Semiconductor	MUR180E
D2, D5	1	Diode	1N4148	SOD-323	ON Semiconductor	1N4148WS
D3	1	Ultra fast rectifier	MURD340	DPAK	ON Semiconductor	
D4	2	Diode	1N4937	axial	ON Semiconductor	1N4937G
D6	1	Zener diode	12 V, 0.5 W	SMD	ON Semiconductor	MMSZ12T1G
D8	1	Diode bridge	1.5 A, 600 V	through hole	ON Semiconductor	DF06M
D11	1	Diode fast	Not connected		ON Semiconductor	ES1JFL
Q1	1	MOSFET	6 A, 800 V, 0.85 Ω	TO-251 (IPAK)	ON Semiconductor	FCU850N80Z
C1, C2, C21	3	X2 capacitors	100 nF, 330 V ac	through hole	EPCOS	B32912A3104
C6	1	Capacitor	100 pF	SMD 0805		
C8	2	Capacitor	330 nF	SMD 0805		
C9, C10, C11, C18	4	Capacitor	22 pF	SMD 0805		
C12, C22, C26, C31	4	Capacitor	100 nF	SMD 0805		
C11	1	Capacitor	47 pF	SMD 0805		
C13	1	Electrolytic capacitor	22 μ F, 35 V	radial	Panasonic	EEUFC1V220
C14	1	Electrolytic capacitor	33 μ F, 35 V	radial	Panasonic	EEUFM1V330
C15	1	Ceramic capacitor	1.5 nF, 1 kV	SMD1206		
C17, C24	1	Y capacitor	1 nF			
C19, C29	2	Electrolytic capacitor	330 μ F, 63 V, 1.58 A	radial	Panasonic	EEUFR1J331B
C23	1	Capacitor	100 nF, 630 V	through hole	Würth	890303422005CS
C30	1	Electrolytic capacitor	4.7 μ F, 63 V	through hole	Nichicon	UPW1J4R71TD
R1, R2	2	Resistor	3.9 k Ω	SMD1206		
R3	1	Resistor	43 k Ω	SMD0805		
R5	1	Resistor	8.2 k Ω	SMD 0805		
R7, R10, R30, R33, R36, R27x, R44	7	Resistor	0 Ω	SMD 0805		
R9	1	Resistor	1 k Ω	SMD 1206		
R11	1	Resistor	1.5 k Ω , 1%	SMD 0805		
R12	1	Resistor	4.7 Ω	SMD 0805		
R14, R21	1	Resistor	68 k Ω	SMD 1206		
R15, R16	1	Resistor	1.3 Ω , 1%, 0.33 W	SMD1206		
R18	1	82 k Ω , 1W	82 k Ω , 1W	SMD2512		
R20	1	Resistor	47 Ω	SMD1206		
R21	1	Resistor	43 k Ω	SMD1206		
R22	1	Resistor	1 k Ω	SMD0805		

AND90015

Table 3. BOM FOR NCL30488 20 W SSR EVB (continued)

Reference	QTY	Description	Value / Tol	Footprint	Manufacturer	Manufacturer Part Number
R26	1	Resistor	150 Ω , 2 W	axial		
R27	1	Resistor	22 Ω	SMD 1206		
R28	1	Resistor	220 Ω	SMD 0805		
R29	1	Resistor	36 k Ω	SMD 0805		
R31	1	Resistor	2.2 k Ω	SMD 0805		
R32	1	Resistor	310 k Ω	SMD 0805		
R34	1	Resistor	10 k Ω	SMD 0805		
R40, R45	2	Resistor	0.24 Ω , 1%, 0.5 W	SMD 1210		
R43	1	Resistor	0 Ω	SMD 0805		
R46	1	Resistor	33 k Ω	SMD0805		
R47	1	Resistor	1.5 k Ω	SMD0805		
U1	1	NCL30488	NCL30488	SOIC8	ON Semiconductor	NCL30488
U4	1	Optocoupler	SFH6106-3	SMD		SFH6106-3
U3	1	CC/CV controller	NCP4328A	TSOP 6	ON Semiconductor	NCP4328A
J1	1	Input connector male		through hole	WEIDMULLER	SL5.08/3/90 4.5
J1a	1	Input connector female			WEIDMULLER	BL5.08/3
J2, J3	1	Input connector male		through hole	WEIDMULLER	
J2a, J3a	1	Input connector female			WEIDMULLER	
J4	1	BNC connector				
T1	1	Flyback Transformer		through hole	Würth	750370980

AND90015

TRANSFORMER SPECIFICATION

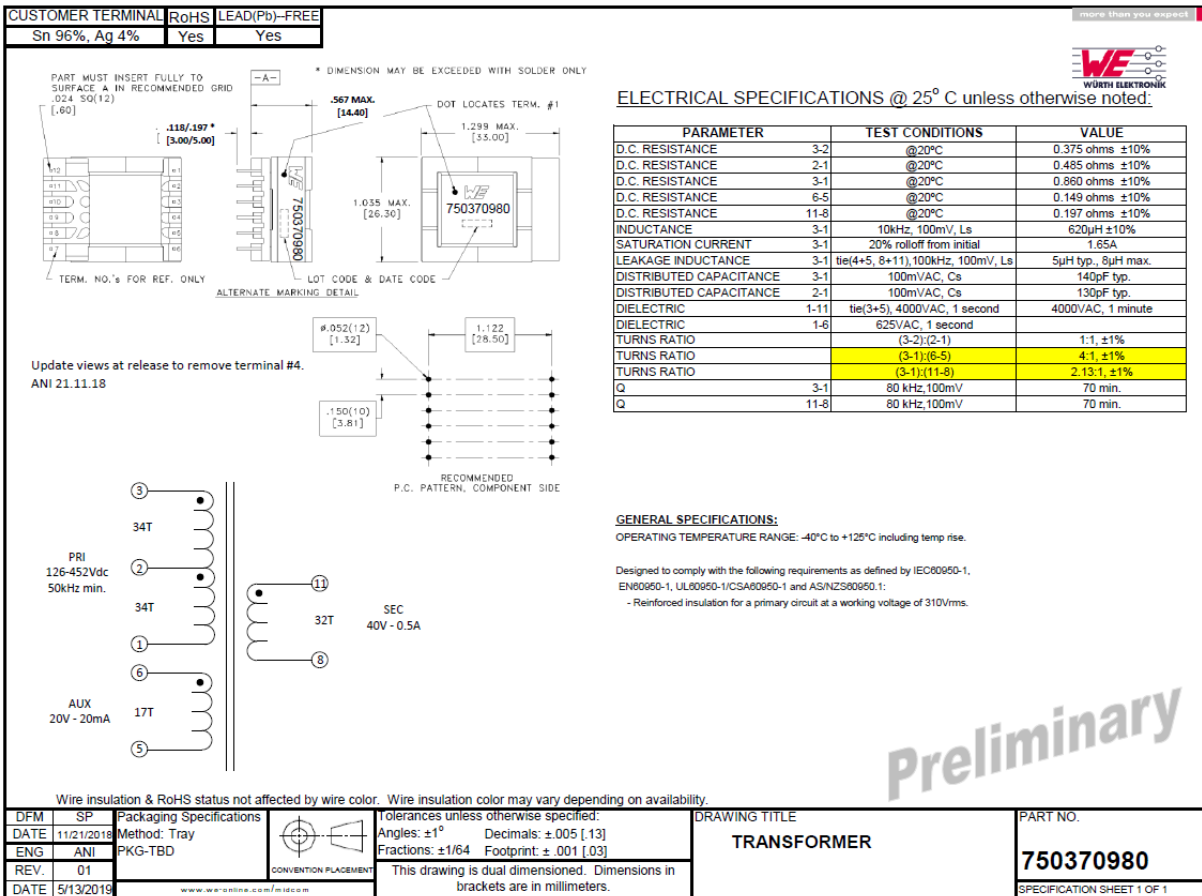


Figure 13. Transformer Specification

REFERENCES

1. [NCL30488](#) Datasheet
2. Joel Turchi, “4 Key Steps to Design a NCL30088–Controlled LED Driver”, [AND9200/D](#)
3. Stéphanie Cannenterre, “Designing a LED driver with the NCL30486/88”, [ANDXXXX](#)
4. [NCP4328](#) Datasheet
5. Christophe Basso, “Designing a type 2 compensator with the [NCP4328](#) / [NCP4352](#)”

ON Semiconductor and are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor’s product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. “Typical” parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including “Typicals” must be validated for each customer application by customer’s technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:
 Email Requests to: orderlit@onsemi.com

TECHNICAL SUPPORT
 North American Technical Support:
 Voice Mail: 1 800-282-9855 Toll Free USA/Canada
 Phone: 011 421 33 790 2910

Europe, Middle East and Africa Technical Support:
 Phone: 00421 33 790 2910
 For additional information, please contact your local Sales Representative