

# ON Semiconductor

## Is Now

# onsemi™

To learn more about onsemi™, please visit our website at  
[www.onsemi.com](http://www.onsemi.com)

---

**onsemi** and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.

## Efficiency Improvements Using DSN2 Schottky Diodes

Prepared by: Edwin Romero  
ON Semiconductor



ON Semiconductor®

<http://onsemi.com>

### APPLICATION NOTE

#### ABSTRACT

This application note describes the advantages of using Low Forward Voltage ( $V_f$ ) Schottky diodes in a variety of applications. The lower voltage drop results in a significant increase in efficiency.

#### Lower Forward Voltage Drop

Figure 1 shows the relative improvement in forward voltage drop,  $V_f$ , with the DSN2 Schottky diodes technology. The comparison is made to industry SOD-323 EP Schottky diodes.

It is clear that such a significant improvement can have major impact on the efficiency of many circuit applications.

The forward voltage drop of the DSN2 Schottky diodes is shown in Table 1. The data are taken from the typical data charts on the data sheet at 25°C at the devices rated specifications. A comparison can be made between a 20 V device and a 30 or 40 V device. Four surface mount footprints are shown, 0201, 0402, 0502 and 0603. The forward voltage drop is presented at rated currents.

All Schottky diodes have a negative temperature coefficient of approximately 1 mV/°C. The forward voltage drop can be as much as 0.100 V lower at 125°C when compared to the voltage drop at 25°C.

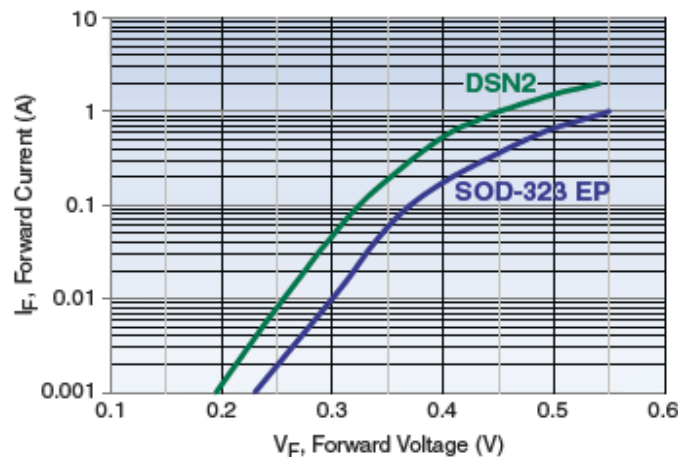


Figure 1. Low Forward Voltage Comparison

**Table 1. FORWARD VOLTAGE FOR DSN2 SCHOTTKY DIODES AS A FUNCTION OF FORWARD CURRENT, ALL VALUES ARE AT 25°C**


	NSR01F30NX	NSR02F30NX	NSR05F20NX	NSR05F30NX	NSR05F40NX	NSR10F20NX	NSR10F30NX	NSR10F40NX	NSR20F20NX	NSR20F30NX
I <sub>F</sub>	0.1 A	0.2 A	0.5 A	0.5 A	0.5 A	1.0 A	1.0 A	1.0 A	2.0 A	2.0 A
V <sub>R</sub>	30 V	30 V	20 V	30 V	40 V	20 V	30 V	40 V	20 V	30 V
DSN2 Package	0201	0201	0402	0402	0402	0502	0502	0502	0603	0603
V <sub>F</sub> @ Rated I <sub>F</sub>	500 mV	550 mV	390 mV	400 mV	420 mV	430 mV	450 mV	445 mV	450 mV	445 mV

**OR'ing Diode Applications**

In the application shown in Figure 2, a low forward voltage drop part is desired. In this example, it is more cost effective to use a single Schottky diode than to use a rectifier. This can be useful where multiple power supplies are needed for redundancy to improve the mean-time-between-failure (MTBF) for a power supply system.

The current rating of the OR'ing device is often much higher than the current flowing through the device used. As an example, a NSR10F20NXT might be used for applications where only 1.0 A of load current is needed for the load. This is used only to keep the energy loss to a minimum. The forward voltage drop is approximately 0.43 V for the NSR10F20NXT at room temperature, as shown by Table 1 above.

If one of the power supplies is a battery, the forward voltage drop is important. The lower the forward voltage drop, the greater the amount of energy available for use as a standby power supply.

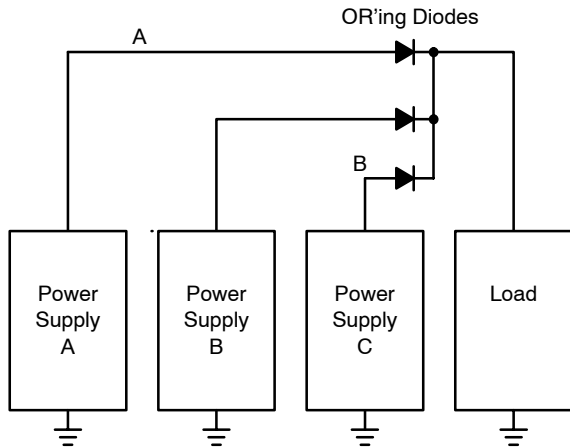

**Figure 2. OR'ing Diode Application**

**Diodes for Reverse Battery Protection**

Another application where a low V<sub>F</sub> Schottky diode is often desired is in the reverse battery protection. This is shown in Figure 4.


In order to prevent damage to the electronic circuits inside the product caused by reverse polarity or surge event, a series diode is used. This device has a typical forward

voltage drop of 0.9 V at 1.0 A. The battery voltages can range between 1.4 V and 1.65 V depending upon the state of charge and current draw. Using a 1.5 V cell, the ratio of 0.9/1.5 indicates that 60% of one cell's voltage is used to overcome the protection diode. In a typical application where there are four cells, the ratio of forward diode voltage to battery voltage is between 13.64 and 16%: (0.9/(4\*1.65) = 0.1364 or 13.64%) or (0.9/(4\*1.40) = 0.16 or 16%)

Instead of using a standard diode, substitute a 1 A low forward voltage Schottky or a 0.5 A device. The burden voltage of the NSR10F20NXT is only 0.430 V, which is a 52.2% reduction, ((0.9 - 0.430)/0.9 = 0.522) over a standard diode. Using the NSR05F30NXT at 0.400 V, the percentage gain is even higher at 55.6 percent, ((0.9 - 0.40)/0.9 = 0.555) over the industry standard rectifier.

The burden voltage is very critical if the batteries are Lithium ion (Li-Ion) or nickel metal hydride (NiMH). There are many consumer applications where using a low V<sub>F</sub> device is key in helping improve the systems efficiency. The use of a NSR10F20NXT can provide protection and not be a major burden on the battery voltage needed for the application.

The forward voltage drop can be reduced further by using the 20 V Schottky, (NSR05F20NXT), which has a forward voltage drop of only 0.390 V at 0.5 A.

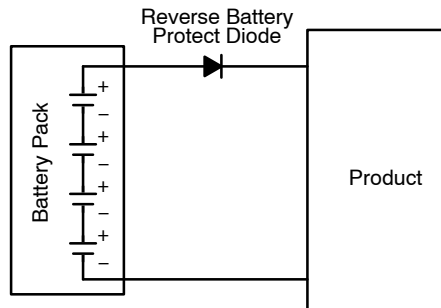

**Figure 3. Reverse Battery Protection**

**DC to DC Converters**

Another application where the use of low V<sub>F</sub> Schottky diodes improves efficiency is the DC to DC converter circuit. In portable type products where a multiple cell NiCd, NiMH, or lithium ion (Li-Ion) rechargeable battery pack is

used as a power source, a buck regulator can produce output voltages such as 1.5 V, 2.2 V, or even 3.3 V. A buck regulator can be very efficient. An alternative method of obtaining 1.8, 2.2 or 3.3 V at the output is to use a linear regulator, but this can be inefficient. When implementing the controller as a buck regulator and using different Schottky rectifiers, it can be shown that the lower the forward voltage drop of the diode, the greater the efficiency of the buck regulator. Such a schematic is shown in Figure 5.

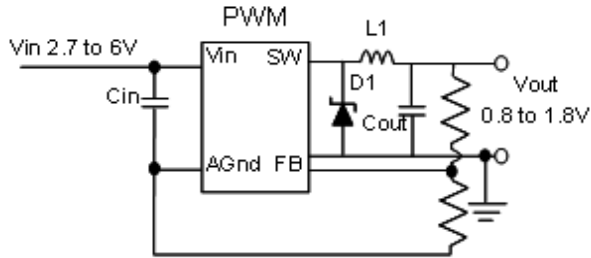


Figure 4. Buck Converter Circuit

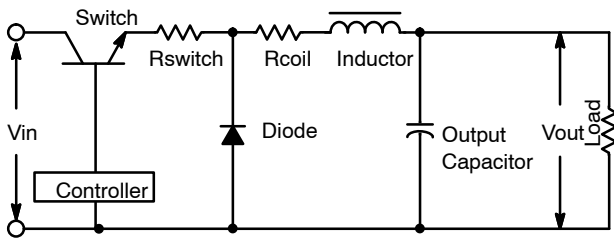


Figure 5. Simple Buck Regulator

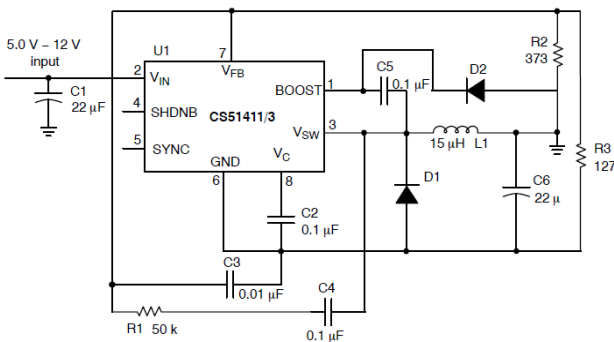


Figure 6. Inverter Converter

**Diode Selection**

The diode in the buck converter provides the inductor current path when the power switch turns off. The peak reverse voltage is equal to the maximum input voltage. The peak conducting current is clamped by the current limit of the IC. The average current can be calculated from:

$$I_{D(AVG)} = \frac{I_O(V_{IN} - V_O)}{V_{IN}}$$


The worst case of the diode average current occurs during maximum load current and maximum input voltage. For the diode to survive the short circuit condition, the current rating of the diode should be equal to the Foldback Current Limit.

**Conclusion**

When selecting a Schottky diode it's important to keep in mind the forward voltage and reverse blocking voltage characteristics. Choosing the proper Schottky diode will help reduce the impact of power losses in various applications. On Semiconductor has a range of Schottky diodes in variation of package from SOT-23 down to the smallest 0201 to suit any application.

**References**

1. NSR05F20/D, "Schottky Barrier Diode", Data Sheet, ON Semiconductor.
2. NSR10F20/D, "Schottky Barrier Diode", Data Sheet, ON Semiconductor.
3. NSR20F20/D, "Schottky Barrier Diode", Data Sheet, ON Semiconductor.
4. NSR05F30/D, "Schottky Barrier Diode", Data Sheet, ON Semiconductor.
5. NSR10F30/D, "Schottky Barrier Diode", Data Sheet, ON Semiconductor.
6. NSR20F30/D, "Schottky Barrier Diode", Data Sheet, ON Semiconductor.
7. NSR05F40/D, "Schottky Barrier Diode", Data Sheet, ON Semiconductor.
8. NSR10F40/D, "Schottky Barrier Diode", Data Sheet, ON Semiconductor.
9. Sheet, ON Semiconductor.
10. NSR02F30/D, "Schottky Barrier Diode", Data Sheet, ON Semiconductor.
11. CS51411/D, "1.5 A, 260 kHz and 520 kHz, Low Voltage Buck Regulators with External Bias or Synchronization Capability", Data Sheet, ON Semiconductor.
12. AN920/D, "Theory and Applications of the MC34063 and µA78S40 Switching Regulator Control Circuits", Application Note, ON Semiconductor.
13. M. Rashid, Power Electronics, Circuits, Devices, and Applications, 2<sup>nd</sup> Ed. © 1988, 1993, Prentice Hall, Englewood Cliff, NJ 07632, ISBN 0-13-678996-X
14. Mohan, Undeland, Robbins, Power Electronics: Converter, Applications, and Design, 1<sup>st</sup> & 2<sup>nd</sup> Ed., ©1989, 1995, John Wiley & Son, NY. ISBN 0-471-61342-8

**ON Semiconductor** and  are registered trademarks of Semiconductor Components Industries, LLC (SCILLC). SCILLC reserves the right to make changes without further notice to any products herein. SCILLC makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does SCILLC assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. "Typical" parameters which may be provided in SCILLC data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. SCILLC does not convey any license under its patent rights nor the rights of others. SCILLC products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the SCILLC product could create a situation where personal injury or death may occur. Should Buyer purchase or use SCILLC products for any such unintended or unauthorized application, Buyer shall indemnify and hold SCILLC and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that SCILLC was negligent regarding the design or manufacture of the part. SCILLC is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

**PUBLICATION ORDERING INFORMATION**

**LITERATURE FULFILLMENT:**

Literature Distribution Center for ON Semiconductor  
P.O. Box 5163, Denver, Colorado 80217 USA  
**Phone:** 303-675-2175 or 800-344-3860 Toll Free USA/Canada  
**Fax:** 303-675-2176 or 800-344-3867 Toll Free USA/Canada  
**Email:** orderlit@onsemi.com

**N. American Technical Support:** 800-282-9855 Toll Free  
USA/Canada  
**Europe, Middle East and Africa Technical Support:**  
Phone: 421 33 790 2910  
**Japan Customer Focus Center**  
Phone: 81-3-5773-3850

**ON Semiconductor Website:** [www.onsemi.com](http://www.onsemi.com)  
**Order Literature:** <http://www.onsemi.com/orderlit>  
For additional information, please contact your local  
Sales Representative