

SEC-6K6W-CLLC-GEVK: 6.6/7.2 kW On Board Charger (OBC) CLLC Reference Design Kit Power Board (SEC-6K6W-CLLC-PB-GEVB)

TND6378/D

Use together with the 6.6/7.2 kW OBC CLLC Control Board.

SPECIFICATIONS

| Device | Application | Input Voltage | Output Power | Topology | I/O Isolation |
|--|---------------------|--|--------------|--|---------------|
| NVHL020N090SC1 NVHL040N120SC1 NCV57000DWR2G NCV4274CST33T3G NCV2901DR2G NCV890100PDR2G NCV210RSQT2G NCV2003SN2T1G NCV8715SQ33T2G NCV431AIDR2G SC431AVSNT1G NCID9401 NCD98010XDPT3G FSL538APG FSL4110LRN ... | On Board EV Charger | 350 – 750 Vdc G (Grid) to B (Battery) mode 250 – 450 Vdc B (Battery) to G (Grid) mode | 7.2 kW | Full bridge CLLC in main converter Flyback, Buck-boost, and Buck in auxiliary power | Yes |

OTHER SPECIFICATIONS

| | |
|------------------------------|--|
| Output Voltage (G to B Mode) | 250 – 450 Vdc adjustable |
| Output Current (G to B Mode) | 0 – 20 A adjustable |
| Typical Efficiency | 97% |
| Dimension | 229 x 178 x 70 mm + Transformer + Resonant Capacitor Boards + Controller Board |

PHOTOGRAPH OF THE REFERENCE DESIGN BOARDS

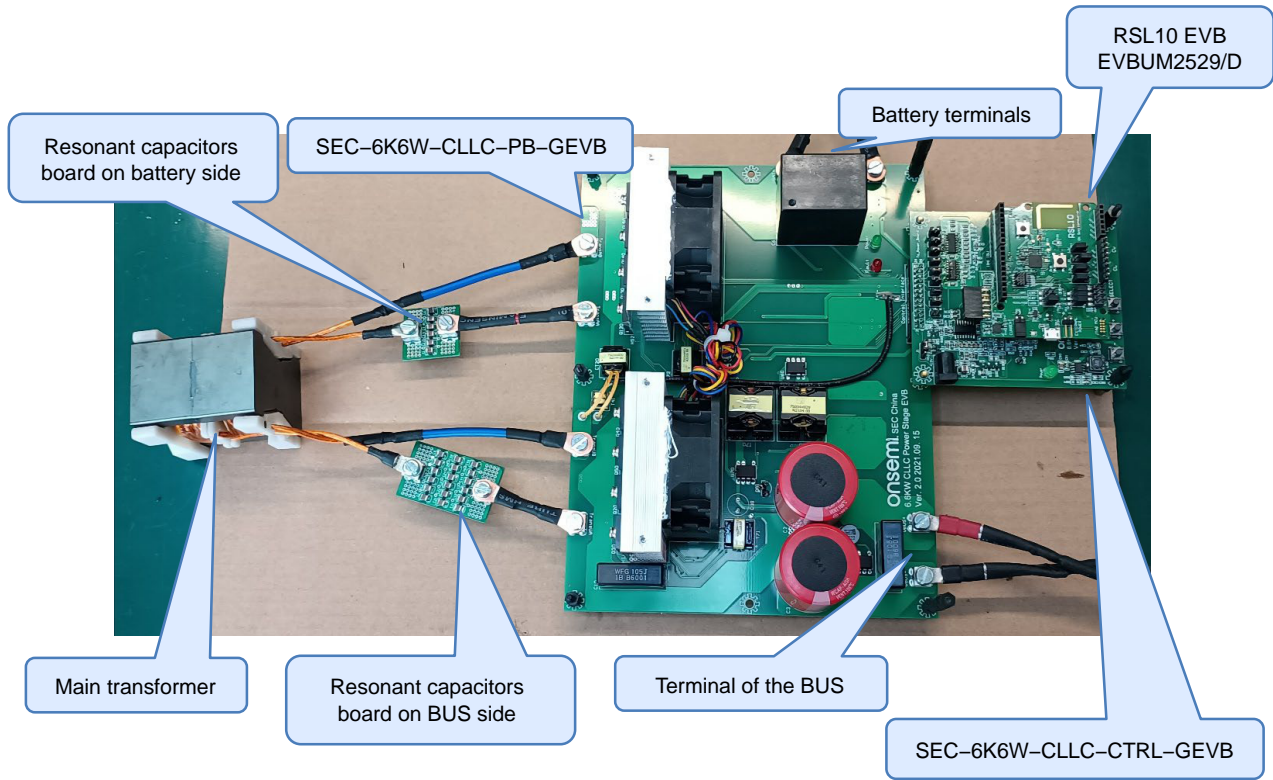


Figure 1. Whole System

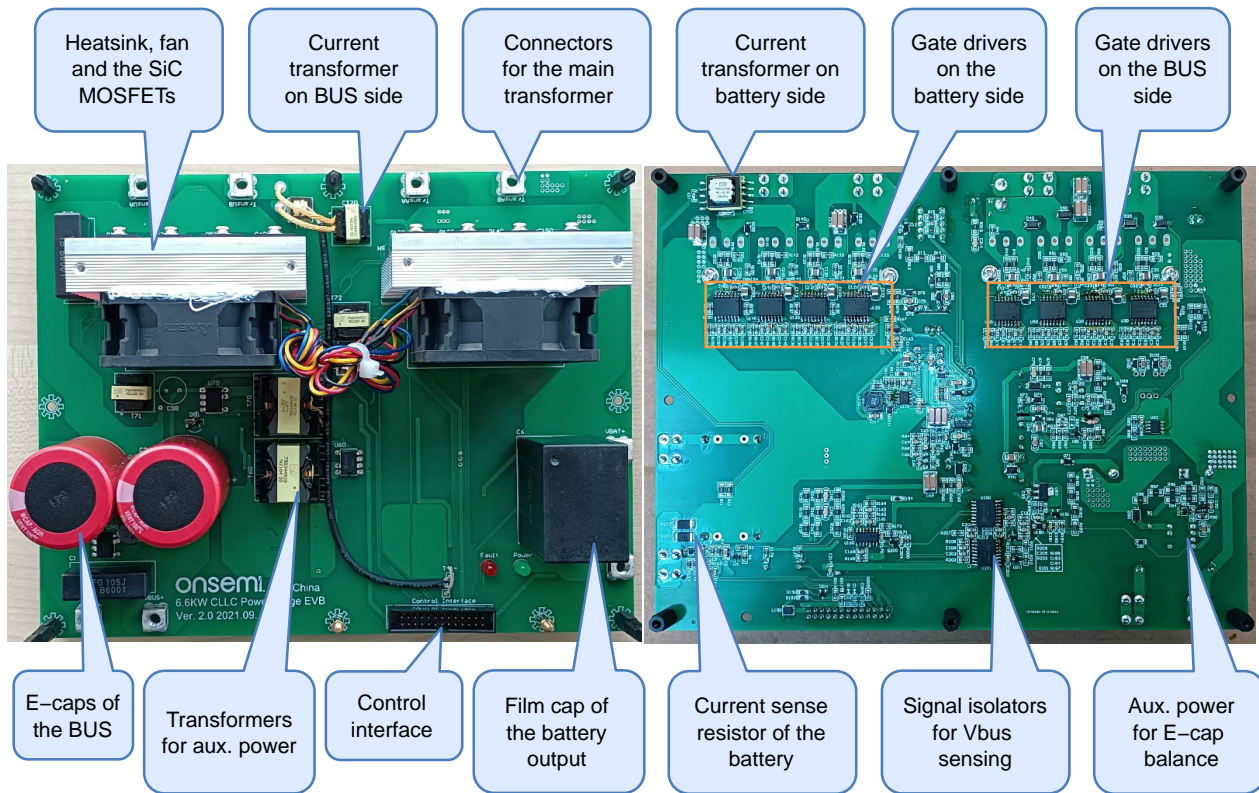


Figure 2. Top Side of the Power Board

Figure 3. Bottom Side of the Power Board

SYSTEM OVERVIEW

Key Features

- Full bridge SiC MOSFETs on both sides allowing for operational modes such as Pulse Frequency Modulation, Pulse Width Modulation, Phase Shifted Full Bridge modulation and mixed operation.
- Flexible control interface to allow for adaptation to different controller boards.
- Hardware protection on both sides for over-voltage, battery port over-current, and DESAT of each SiC MOSFET.

- Onboard auxiliary power system to supply every circuit on the board and the control board. No outside DC source required.
- Innovative active Bus Capacitor Voltage Balancing circuit combined with the auxiliary power supply provides an economical solution for safely balancing the voltages across the capacitors, while minimizing additional power losses in the circuit.

Block Diagram of Hardware

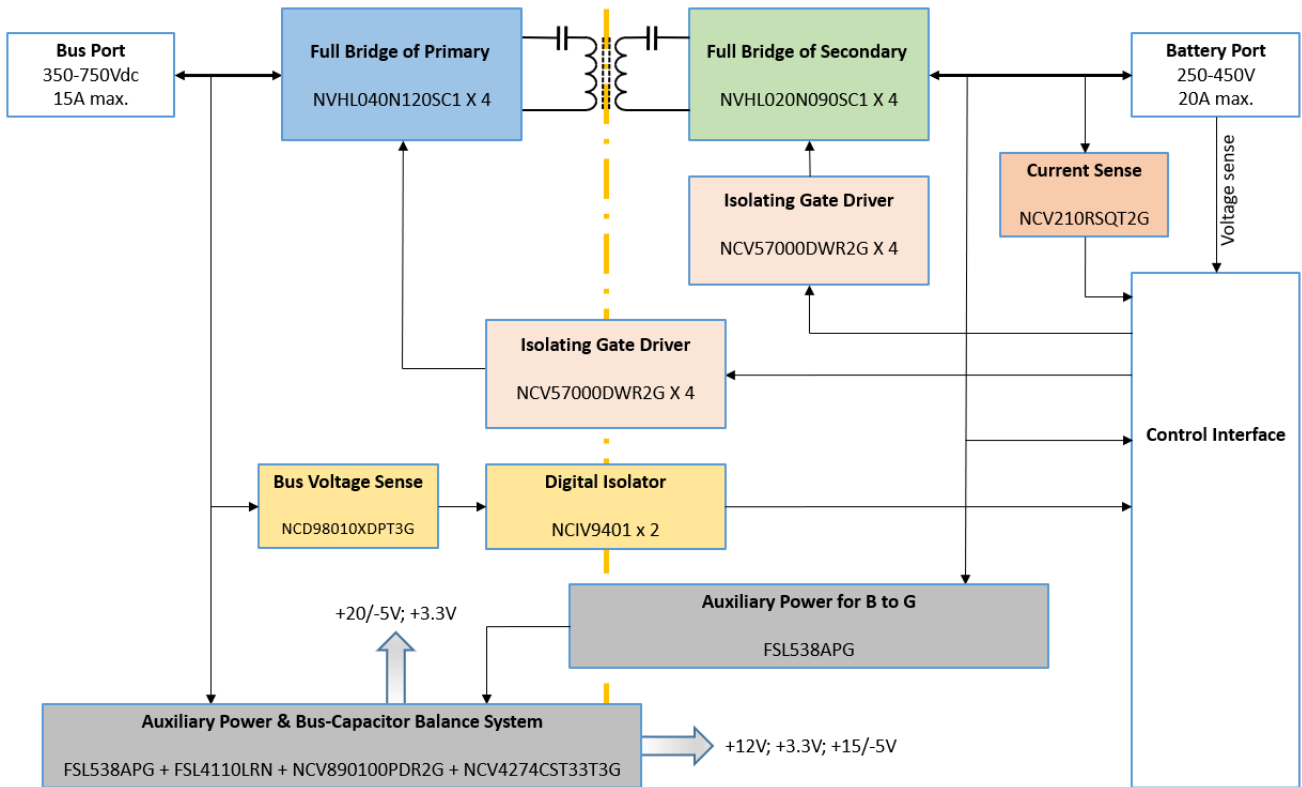


Figure 4. Block Diagram of Hardware

SCHEMATICS AND CIRCUIT DESCRIPTION

Full Bridges, Drivers and the Resonate Tank

Figure 5 shows the schematic with full bridges on both the Bus side (Primary) and the Battery side (secondary). The full bridge on the Bus side is realized by using 40 mΩ SiC MOSFETs (1200 V rated) for Q20, Q30, Q40 & Q50 being driven by +20 V/-5 V. This implementation can accept up to 750 V or even higher bus voltage but is limited by the E-caps. The full bridge on the Battery side is realized by using 20 mΩ SiC MOSFETs (900 V rated) for Q120, Q130, Q140 & Q150 being driven by +15 V/-5 V. This implementation is designed for 400 V battery systems and can accept up to 450 V for a typical system but is capable of handling battery voltages up to 600 V. For 800 V battery systems the main change required would be to update the Battery side (secondary) SiC MOSFETs to 1200 V from 900 V.

Each SiC MOSFET is driven by an AEC qualified [NCV57000DWR2G](#) which is a galvanically isolated high-current, high-performance gate driver. The

NCV57000 series gate driver was originally designed to drive IGBTs, but the device is capable of driving SiC MOSFETs. The built-in the desaturation protection function of the NCV57000DWR2G, in case of a short-circuit or over-current fault happening, will pull the gate voltage low and pull the FLT pin low at same time. The FLT pins of each NCV57000DWR2G are tied to the FLT node. The FLT pin is a fault indication signal, we will talk it more on the following content.

Figure 6 shows the schematic of the resonant tank and the main transformer. The resonant capacitors on both sides are assembled in separated small PCBs for ease of location. Multiple capacitors are installed in a series and parallel configuration on the Bus side to provide enough margin for current and voltage. The resonant inductor is integrated into the main transformer for cost and form factor improvements. The specifications of the transformer from two different suppliers are shown in the figures 7a and 7b.

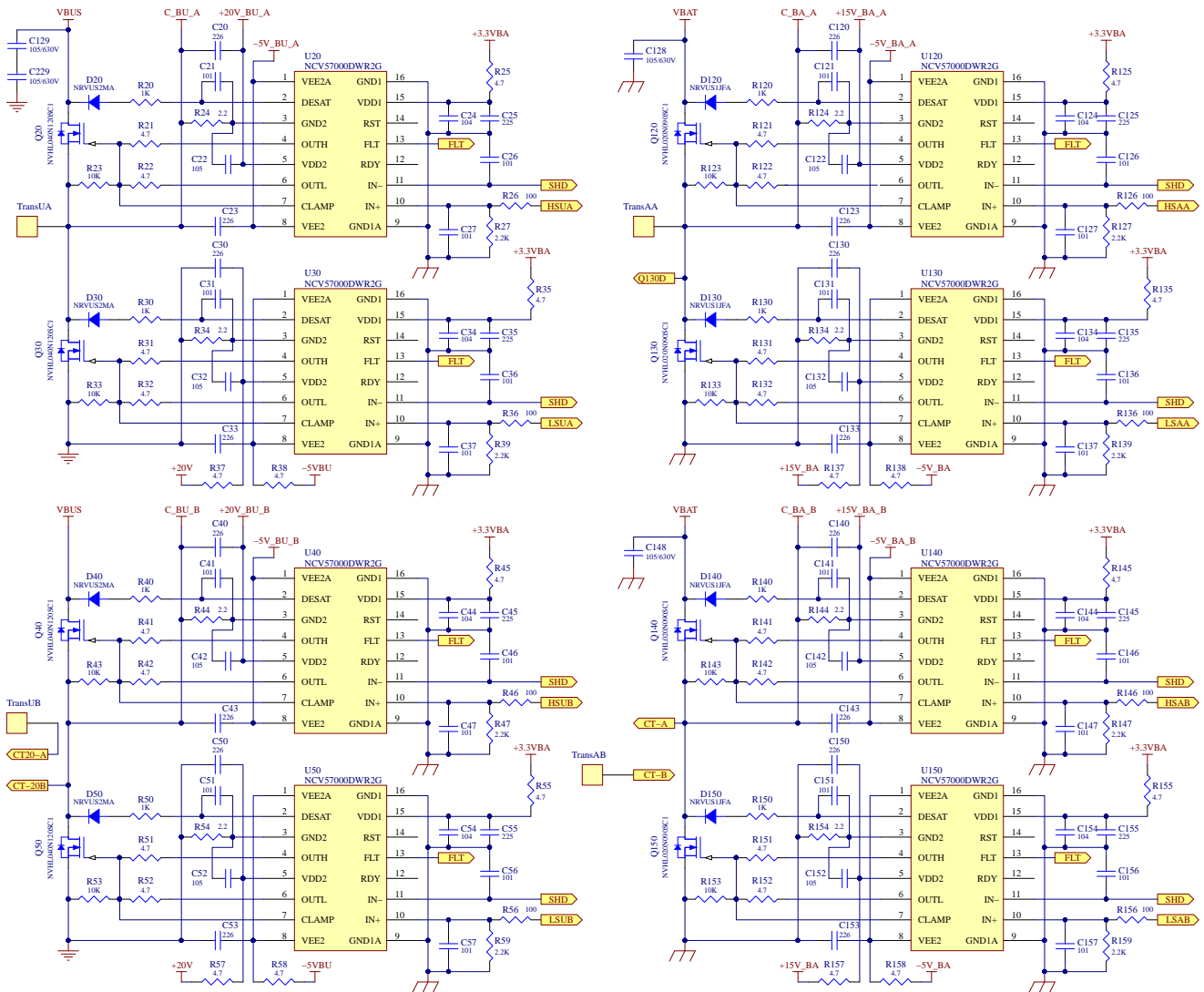


Figure 5. Schematic of the Full Bridges and the Drivers

TND6378/D


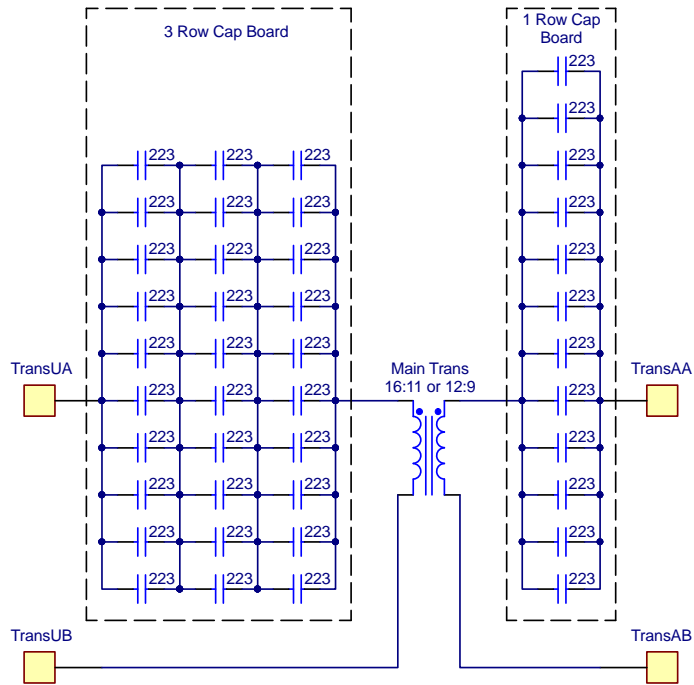


Figure 6. Schematic of the Resonant Tank

Proposal of Automotive Electronics Transformers for ATWPPQ655462B202T


| Approved By | Checked By | Prepared By |
|-------------|------------|-------------|
| Jinbo Cai | Teresa Luo | Dingwei Zhu |
| 2021/11/17 | 2021/11/17 | 2021/11/17 |

1. Structure and Material

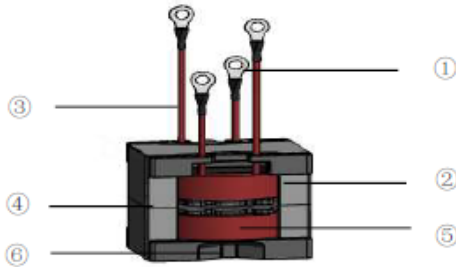

| No. | Part Name | Material Name | UL. NO |
|-----|-----------|--------------------------|--------|
| ① | Terminal | C1100 | / |
| ② | Core | Mn-Zn Ferrite | / |
| ③ | Wire | Mylar Wire (Ø0.1mm*300P) | / |
| ④ | Glue | Epoxy | / |
| ⑤ | Tape | Kapton Tape (180°C) | E24883 |
| ⑥ | Bobbin | PM-9630 | E39252 |

2. Shape and Dimensions (unit: mm)

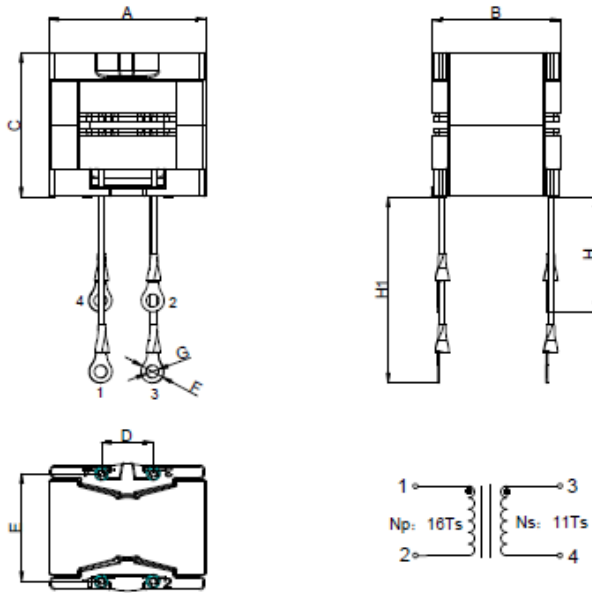

Note : For RoHS compliant products:
 1. Solder : Sn /Ag /Cu .
 2. Marking Code: A2111012 Sunlord Code
 3. Date Code : ** ** ****
 ① ② ③

① Year
 ② Week
 ③ Trace Code

Shape and Dimensions

| Item | A | B | C | D | E | F | G | H | H1 |
|--------------|---------|---------|---------|---------|---------|--------|--------|---------|----------|
| Sunlord Spec | 66.2Max | 54.0Max | 62.0Max | 22.0Ref | 45.0Ref | 9.3Ref | 5.3Ref | 65.0Ref | 165.0Ref |

3. Electrical Characteristics @ 25 °C : (Operating Temperature: - 40 °C to + 125 °C ; Operating Frequency:150kHz)

Sunlord P/N:ATWPPQ655462B202T


| Parameters | Inductance (Lp) | Leakage Inductance (Lk) | DCR | | TURNS RATIO | HI-POT |
|----------------|------------------------------|------------------------------|------------------|------------------|-------------------------------|-------------------------|
| | Unit | Unit | Unit | Unit | Unit | Unit |
| Test Terminal | Pin(1-2) | Pin(1-2), shorted Pin (3-4) | Pin(1-2) | Pin(3-4) | Pin(1-2):(3-4) | Pri to Sec |
| Sunlord Design | 170.0±10% | 25.0uH±10% | 30.0 Max | 20.0 Max | 16:11±0.5 | 3000Vao/50Hz/ 5mA/2s |
| Test Condition | Measured at 150KHz,0.1V 25°C | Measured at 150KHz,1.0V 25°C | Measured at 25°C | Measured at 25°C | Measured at 15.75KHz,1V, 25°C | Measured at 25°C |

Note: •Wave soldering reference JB/T 7488-2008, the soldering time is 3s~5s at the soldering temperature of 250±2°C
 •MLS level 1 •RoHS compatible


Revision:01

Figure 7a. Specification of the Main Transformer from Sunlord

SCHEMATIC

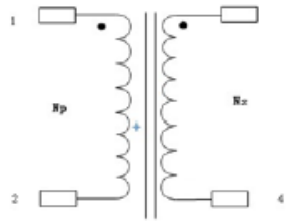

DIMENSION(unit:mm)

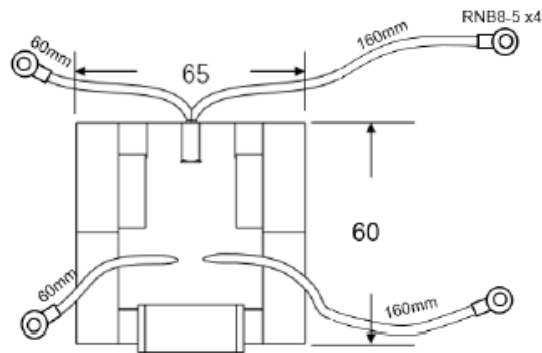

SPECIFICATION

Core: PC95

Type: PQ65/60

Inductance: 175uH±10%

Leakage: 25uH±10%

Turns Ratio: $N_p:N_s = 12:9$

DCRp: 9 mΩ MAX

DCRs: 7 mΩ MAX

Insulation Level : CLASS F

HI-POT: 3.3kVac/rms

Primary coils: 0.05*900*2 Litz Wire

Secondary coils: 0.05*900*2 Litz Wire

Figure 7b. Specification of the Main Transformer from Magsonder

Sensing, Protection, and the Control Interface

Figure 8 shows the schematic of the voltage, current sensing, over-current, voltage protection, and the control interface.

The battery voltage VBAT is divided down by 3 different resistor strings for various measurements.

- Resistors R195, R196 & R197 divide VBAT down to the voltage signal VSAM which is sent to the control board for battery voltage monitoring. The lower divider resistor is located on the control board for better noise immunity. Additionally, the signal is clamped to +12 V by D191 to prevent high-voltage in the case where the control board is not connected.
- Like VSAM, the VSAF voltage signal is derived from VBAT by the divider of R260, R261 & R262 which is

clamped by D192. The VSAF signal is for feedback of the output voltage for the analog control method. The capacitors C260 and C261 help to speed up the response of the control loop.

- VTHH is divided by R160 and R161+R162 from the reference voltage of +6 V, providing a stable reference of 1.825 V.
- The divider made by R250, R251, R252 and R168 is for over-voltage protection. Once VBAT goes higher than 477 V ($1.825 \times 3011.5 / 11.5$) the FLT pin is pulled low by the comparator U160C and the shutdown signal SHD is pulled high by Q160. From the datasheet of NCV57000 gate driver, if the IN- (SHD) is high, then the output of the gate drivers will be low and the converter stops working.

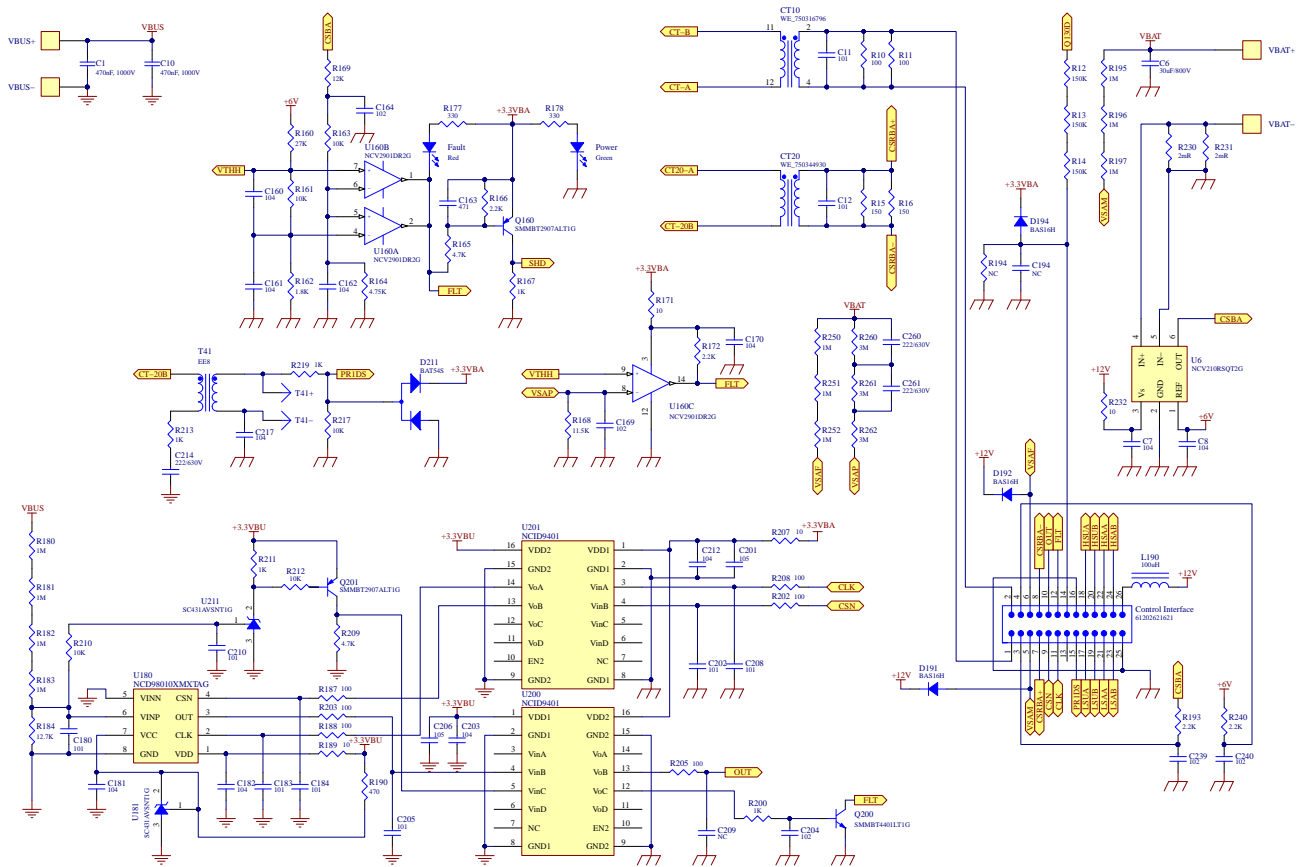


Figure 8. Schematic of the Sensing, Protection, and the Control Interface

Sensing the VBUS voltage is more challenging than sensing VBAT due to the isolation requirement. Thanks to the [High-Speed Quad-Channel Digital Isolator NCID9401](#), we can digitize the VBUS measurement and send this value across the isolation boundary from the bus side to the battery side. The VBUS measurement is digitized by using the [12-Bit Low Power SAR ADC NCD98010XMXTAG](#). This SAR ADC with 3-wire SPI interface performs the analog to digital conversion and this information is easier to transmit

by NCID9401 than the I²C bus. The analog supply and ADC reference voltage Vcc (pin7 of U180) are regulated by the 2.5 V reference U181. VBUS is divided by R180, R181, R182, R183 and R184 with a maximum sensing input voltage of 800 V. Once VBUS becomes greater than 800 V, U211 turns on Q201 and pulls the VinC pin of U200 high. The FLT pin is also pulled low by Q200 and the converter shuts down.

TND6378/D

The battery terminal current is sensed by the shunt resistors R230 and R231, then amplified 200 times by the AEC qualified [Current Sense Amplifier NCV210RSQT2G](#) for power loss reduction on the resistors. The window comparator made by U160 A and B protects for an over-current fault on the battery terminal. If the current is larger than ± 20 A, the FLT pin will be pulled low.

The bus and battery side currents from the resonant tank are sensed by the current transformers CT20 and CT10. The turns ratio of each current transformer is 1:200. The key difference between two transformers is that CT20 needs reinforced insulation, while CT10 only needs functional insulation. For more information about the current transformers, please check the specifications from the supplier in figures 9 and 10.

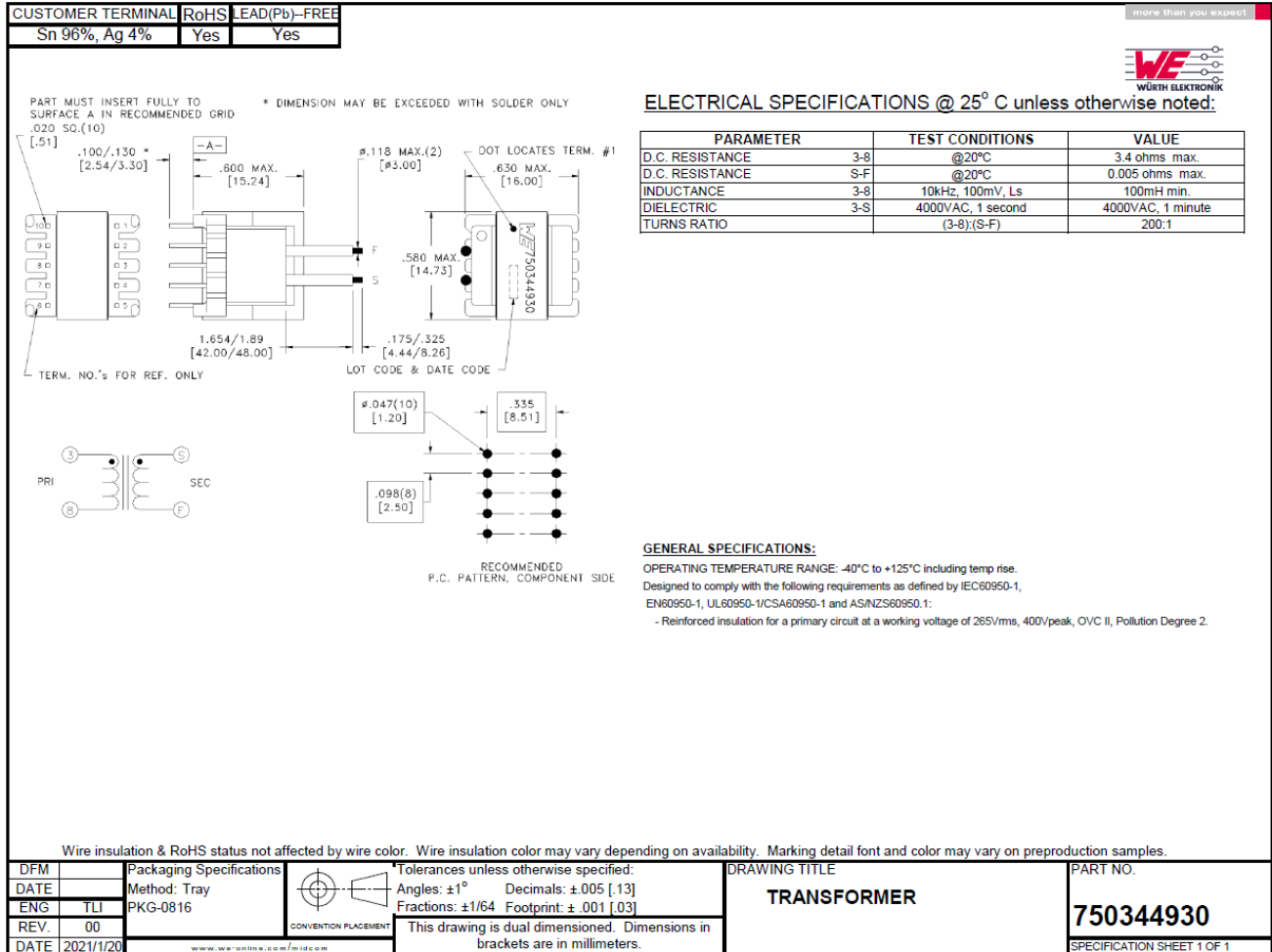


Figure 9. Specification of the Current Transformer CT20. 750344930

TND6378/D

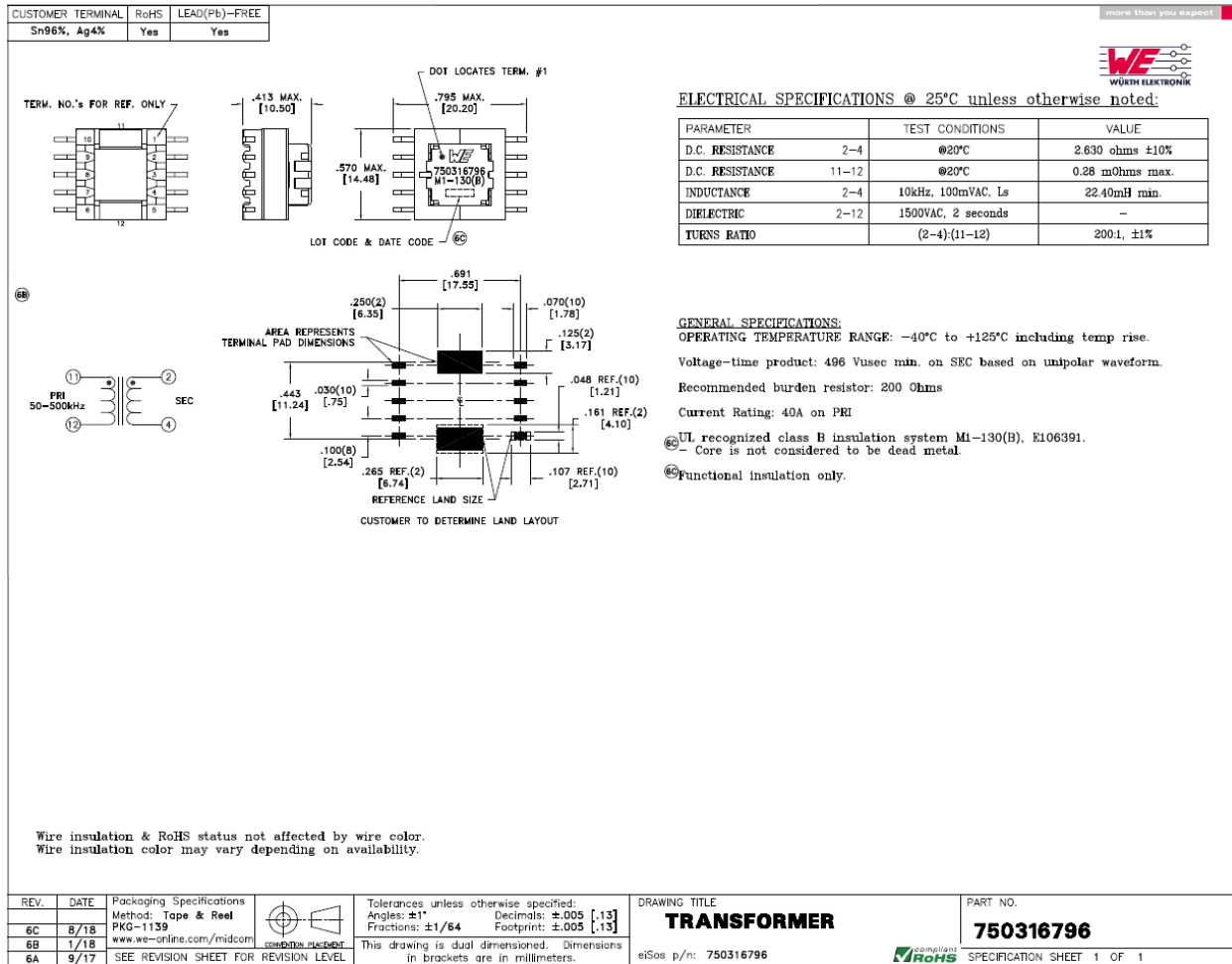


Figure 10. Specification of the Current Transformer CT10. 750316796

The DC current of the bus terminal is not sensed directly. If you need this signal, it is available for monitoring from the Bus (primary) side resonant tank current via the control interface header pins.

For a synchronous rectifier, some control methods need to sense the V_{ds} signals. The V_{ds} signals from both the primary and secondary sides are sent to the control interface for this usage. The V_{ds} of battery side (SR1DS) comes from the

drain of Q130 and is divided by R12, R13 and R14. The lower divider resistor is located on the control board for noise immunity and the signal is clamped to 3.3 V by D194. The V_{ds} of bus side (PR1DS) comes from the drain of Q50 (CT-20B). The pulse transformer T41 scales down and provides reinforced insulation for the signal, with D211 clamping the signal between 0 – 3.3 V. Figure 11 shows the details of the T41.

TND6378/D

The 26-pin dual row connector connects the power board and the control board. Table 1 show the pin definitions.

Table 1. SIGNALS OF THE CONTROL INTERFACE

| Pin | Name | Type | Direction* | Description |
|-----|--------|---------|------------|--|
| 1 | CSRBU+ | Analog | Output | Positive current of Resonant tank of Battery side. |
| 2 | CSRBU- | Analog | Output | Negative current of Resonant tank of Battery side. |
| 3 | CSA+ | Analog | Output | Positive current on Battery terminal. |
| 4 | CSA- | Analog | Output | Negative current on Battery terminal (Reference). |
| 5 | VSAM | Analog | Output | Voltage of the Battery for Measurement. |
| 6 | VSAF | Analog | Output | Voltage of the Battery for Feedback. |
| 7 | CSRBA+ | Analog | Output | Positive current of Resonant tank of Bus side. |
| 8 | CSRBA- | Analog | Output | Negative current of Resonant tank of Bus side. |
| 9 | CSN | Digital | Input | Chip select of the ADC (Read Vbus from battery side. Active low). |
| 10 | OUT | Digital | Output | Data output of the ADC (Read Vbus from battery side). |
| 11 | CLK | Digital | Input | Clock of the ADC (Read Vbus from battery side). |
| 12 | FLT | Digital | I/O | Fault output. Open drain with 2.2 kΩ pull high resistor. Active Low. |
| 13 | NC | - | - | |
| 14 | SR1DS | Digital | Output | Battery side switching edge. Clamp to 3.3 V. |
| 15 | PR1DS | Digital | Output | BUS side switching edge. Transferred to Battery side and clamped to 3.3 V. |
| 16 | GND | - | - | GND |
| 17 | LSUA | Digital | Input | Low side PWM signal of Bus side half bridge A. |
| 18 | HSUA | Digital | Input | High side PWM signal of Bus side half bridge A. |
| 19 | LSUB | Digital | Input | Low side PWM signal of Bus side half bridge B. |
| 20 | HSUB | Digital | Input | High side PWM signal of Bus side half bridge B. |
| 21 | LSAA | Digital | Input | Low side PWM signal of Battery side half bridge A. |
| 22 | HSAA | Digital | Input | High side PWM signal of Battery side half bridge A. |
| 23 | LSAB | Digital | Input | Low side PWM signal of Battery side half bridge B. |
| 24 | HSAB | Digital | Input | High side PWM signal of Battery side half bridge B. |
| 25 | GND | - | - | GND |
| 26 | +12V | Power | Output | ±1 V; 0 – 0.2 A |

*The signal Direction Input/Output is based on the power board.

*Voltage level of all digital signals = 3.3 V.

Auxiliary Power Supply and Electrolytic Capacitors Balancing

The bus voltage on this board can be as high as 800 V before OVP. This design challenge affects both the auxiliary power circuit and the electrolytic capacitors. If we use a traditional flyback converter for the auxiliary power, a 1200 V switching device should be used which will make the cost higher. On the other hand, the maximum voltage rating of standard electrolytic capacitors is 450 Vdc. In the case where the bus voltage is higher than 400 V, frequently 2 or more electrolytic capacitors will be connected in series. When the electrolytic capacitors are in series, leakage

current differences between each capacitor can't be ignored, which can make the voltage on the capacitors unbalanced and may damage a capacitor in the worst case. The traditional solution is to parallel the balancing resistors on each capacitor. For this type of solution, choosing the suitable resistance is a design challenge. When choosing lower resistance the balancing effect is better, but the resistors consume larger amounts power. If choosing larger resistance the power consumption on the resistors is lower, but the balancing effect is not good enough. In this reference design, a creative solution was used to solve these two problems simultaneously.


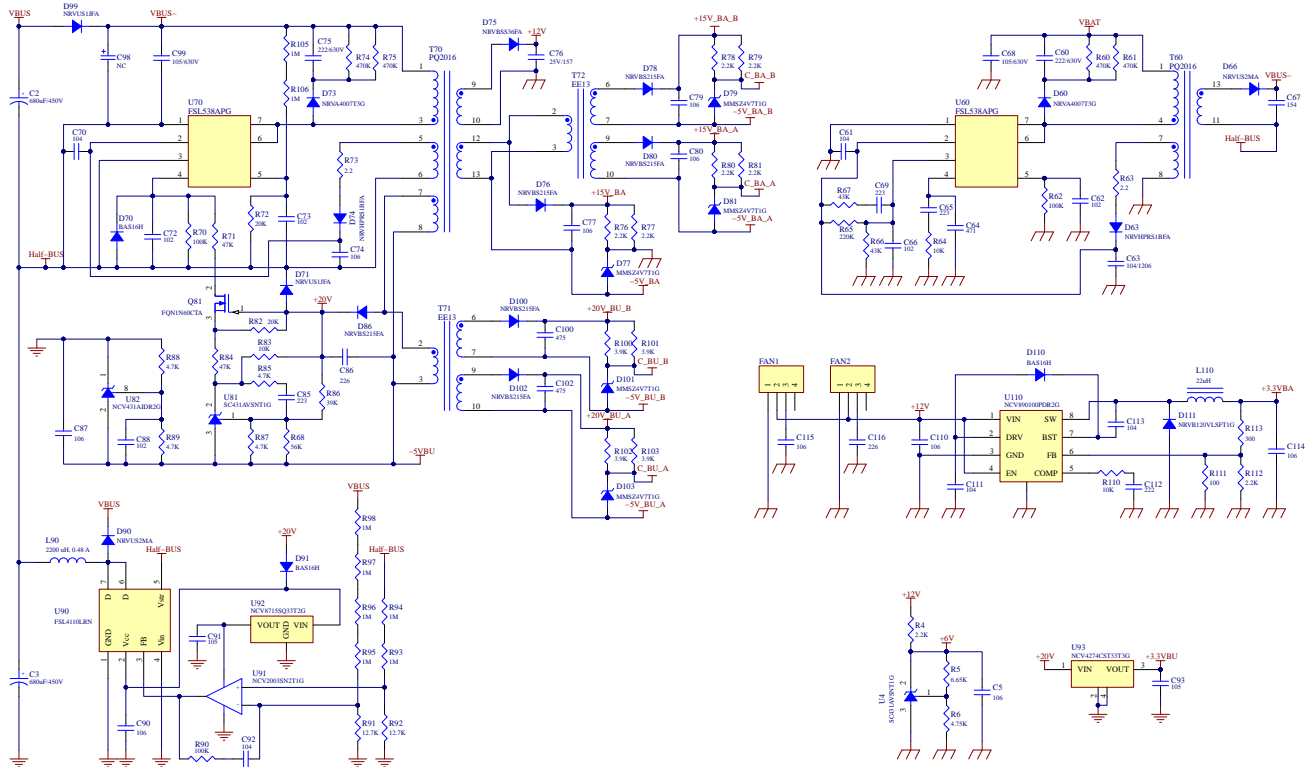


Figure 12. Schematic of the Auxiliary Power Supply

Figure 12 shows the schematic of the auxiliary power of the board, and C2 along with C3 are the electrolytic capacitors in series connected to VBUS. The main flyback converter U70 derives input power from across C2, rather than the whole bus which is different from a traditional solution. When the voltage on C2 and C3 is balanced, the maximum voltage on C2 will be 400 Vdc. U70 drawing power from C2 can make the voltage on C2 drop, and another source is needed to maintain the voltage balance. A solution to this design challenge is provided by U90, U91, and U92. U90 along with L90 and D90 compose a Buck-boost converter, providing a mechanism to balance the voltage between C3 to C2. U91 compares the voltage on

C3 (Half-bus) with VBUS and then adjusts the PWM duty cycle accordingly. The target is to make the Half-BUS node equal to 1/2 of the actual VBUS voltage, and as long as the loop is closed the voltage will be balanced across C2 and C3.

For this design the 1000 V Integrated Power Switcher FSL4110LRN was chosen to meet the voltage stress requirements for the buck-boost converter which is $V_{in} + V_{out}$. From the waveforms on figure 13 we can see the voltage spike is under 835 V during steady state operation when VBUS = 800 V. The solution provided by U90, U91 and U92 keeps the voltage balanced during both startup and steady state. For more information please click the [FSL4110LRN](#) link.

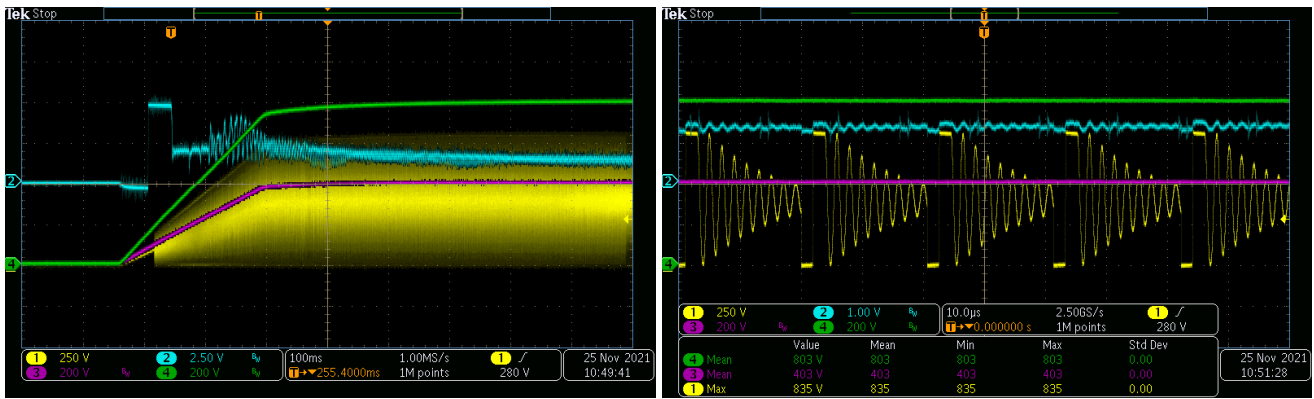

*CH1: Vds of U90; CH2: Vfb (Pin 3) of U90; CH3: Half-bus; CH4: VBUS.

Figure 13. Key Waveforms on the Buck-boost Converter (U90)

On the main flyback converter (U70), we chose the High Performance 800 V Off-line Switcher [FSL538APG](#). The whole board needs 7 power rails which are listed on table 2.

Table 2. OUTPUT RAILS OF THE MAIN AUXILIARY POWER U70

| No. | Name | Rating Current | Load |
|-----|----------------------|----------------|--|
| 1 | +12V | 1 A | Cooling fan, control board, sensing and protection circuits. |
| 2 | +20V – –5VBU | 0.2 A | Vdd2 – Vee2 of U30 and U50. |
| 3 | +20V_BU_A – –5V_BU_A | | Vdd2 – Vee2 of U20. |
| 4 | +20V_BU_B – –5V_BU_B | | Vdd2 – Vee2 of U40. |
| 5 | +15V_BA – –5V_BA | 0.25 A | Vdd2 – Vee2 of U130 and U150. |
| 6 | +15V_BA_A – –5V_BA_A | | Vdd2 – Vee2 of U120. |
| 7 | +15V_BA_B – –5V_BA_B | | Vdd2 – Vee2 of U140. |

The rails for No. 1, 2 and 5 come directly from the main transformer T70. The specification of T70 is shown in figure 14. Due to pin count limitations, the rails for No. 3, 4,

6 and 7 are derived from the pulse transformers T71 and T72. The specification for T71/T72 is shown in figure 15.

TND6378/D

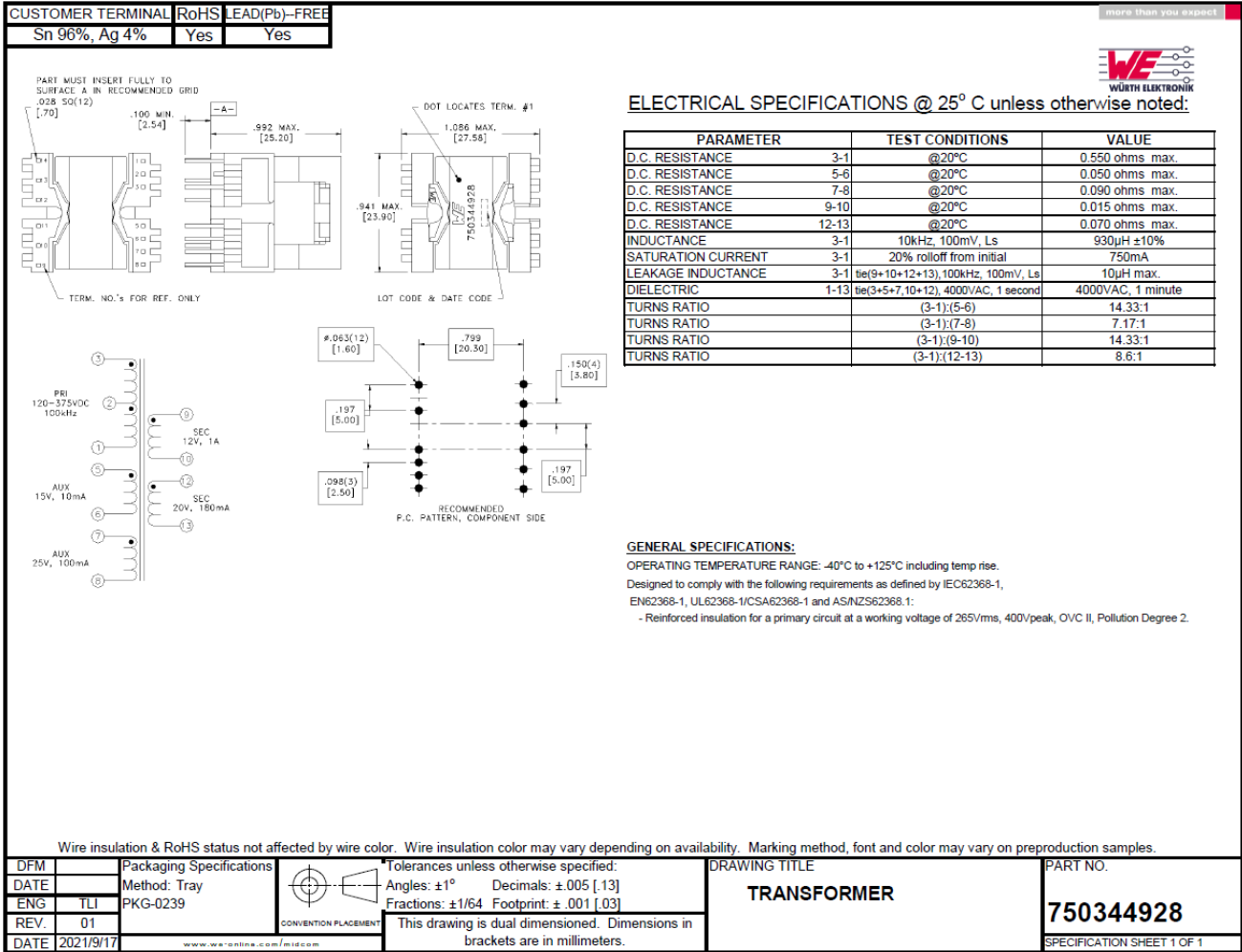


Figure 14. Specification of the Main (G to B) Transformer T70. 750344928

TND6378/D

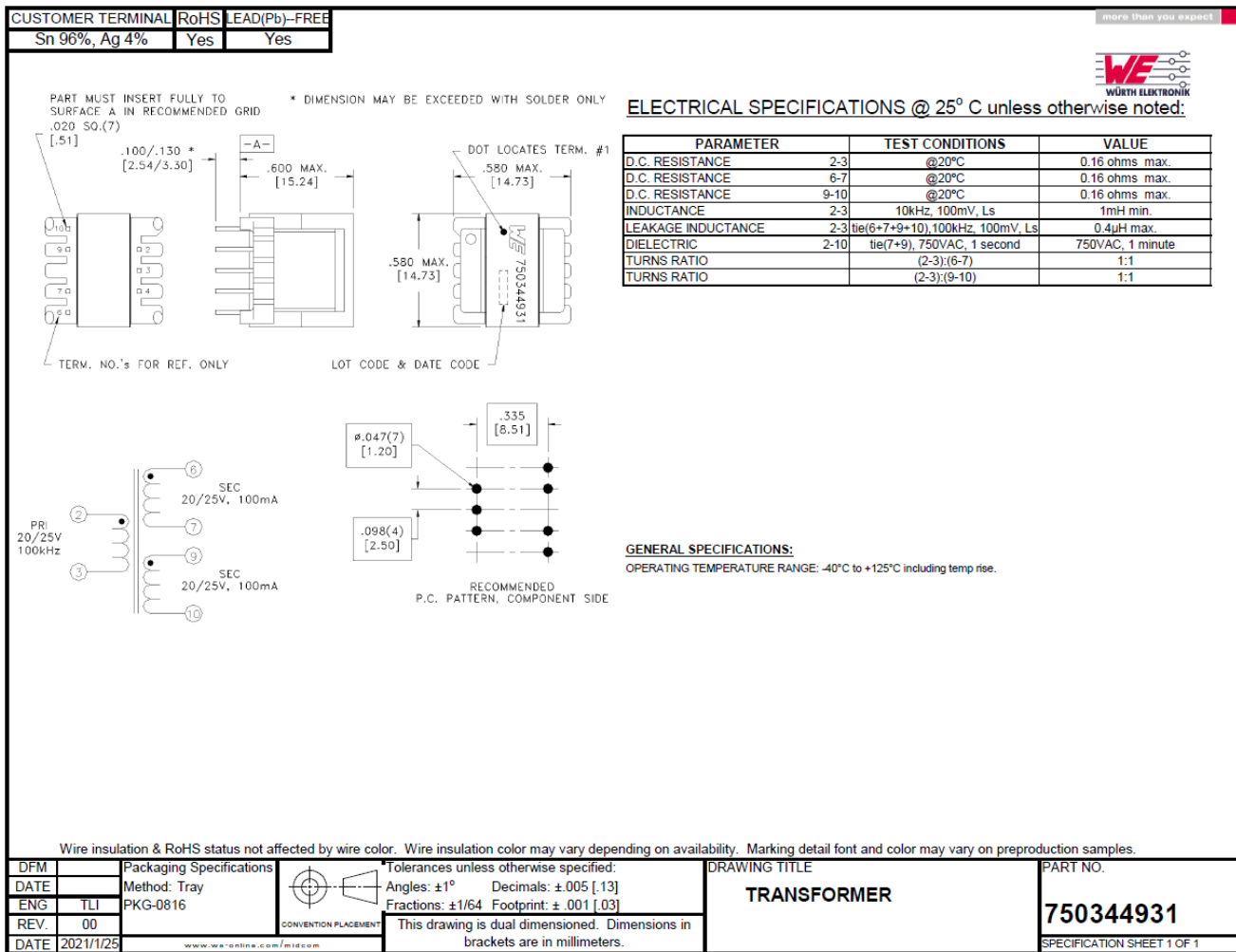


Figure 15. Specification of the Pulse Transformer T71, T72, 750344931

For the SiC MOSFETs to remain in a stable and safe operating condition, the gate driver voltage needs to be well regulated. Since the performance of an opto-coupler is not optimal for use in an automotive design, we feedback the +20V and -5VBU outputs and use Q81 to transfer the error

signal from the primary GND rail to the U70 GND (Half_BUS) rail. In B to G mode D71 charges C3 to 20 V to ensure Q81 functions properly, while during G to B mode C2 must charge to >101 Vdc (the brown-in level) for U70 to startup.

TND6378/D

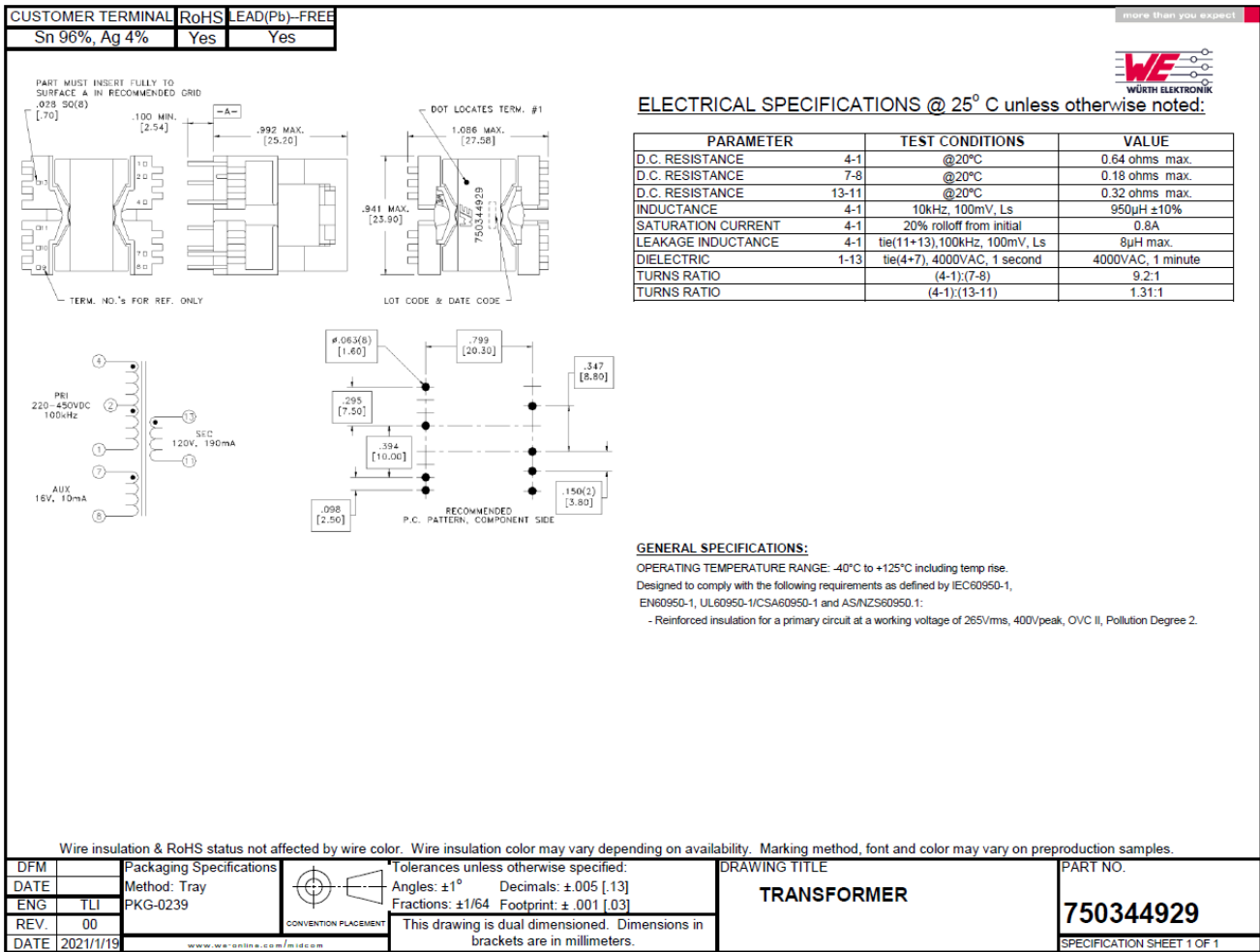


Figure 16. Specification of the B to G transformer T60. 750344929


In the B to G mode U60 will start-up first and charge C99 to 110 Vdc, then U70 will start-up. D99 blocks the current flow to C2 in order to prevent a U70 start-up failure if VBUS is connected to a heavy load. Once the converter is up and running in B to G mode, C2 is charged to higher than 110 Vdc and U60 works under no load condition.

U60 is the FSL538APG which will work under VBAT = 480 Vdc (before OVP). Since the voltage

requirement is not precise, the U60 feedback from Vcc is a simple circuit. The specification of the transformer T60 is shown on figure 16.


The key waveforms of U70 and U60 are shown in figures 17 and 18. We can see, the voltage stresses are acceptable.

TND6378/D

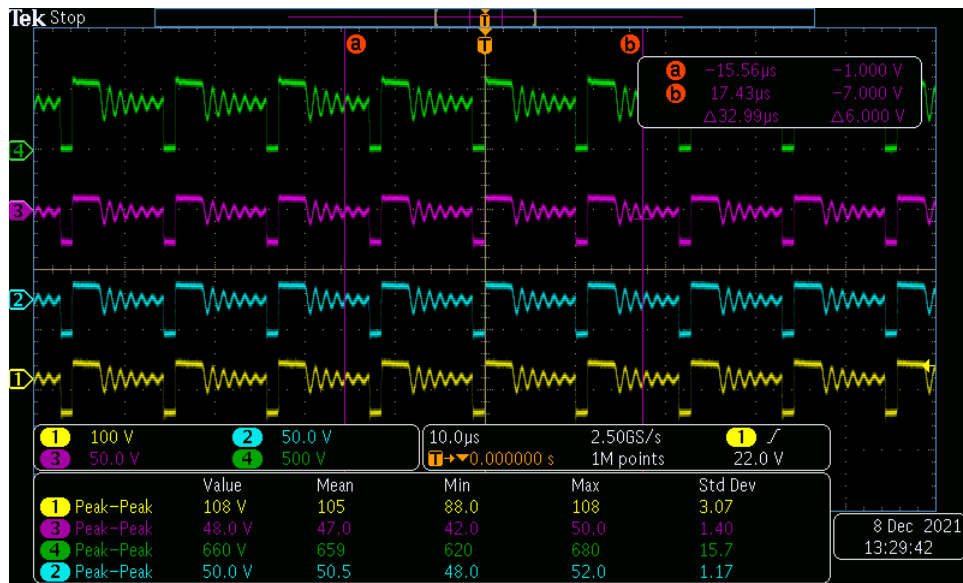

*CH1: Pin 7-8 of T70; CH2: Pin 9-10 of T70; CH3: Pin 5-6 of T70; CH4: Vds of U70.

Figure 17. Key Waveforms on T70 at VBUS = 800 V

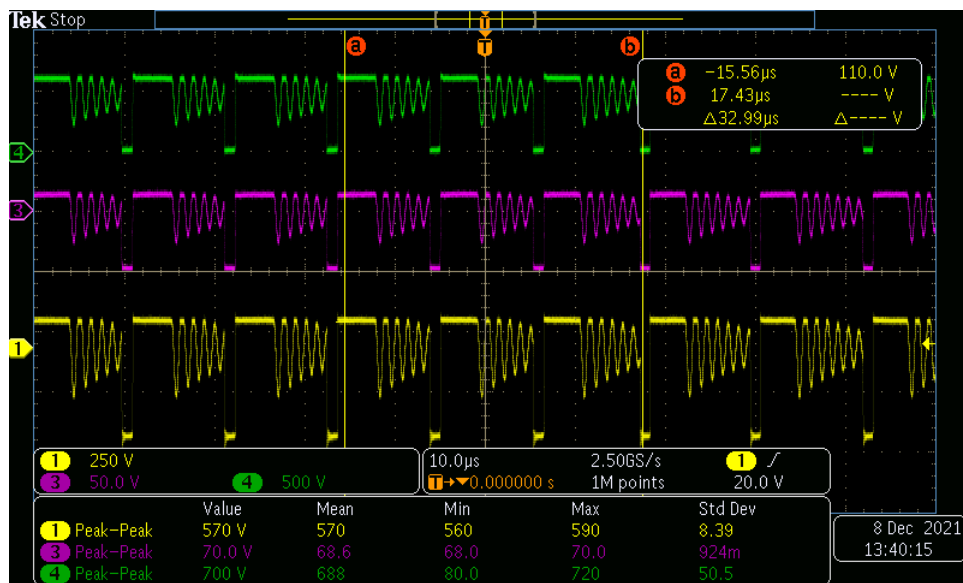

*CH1: Pin 13-11 of T60; CH3: Pin 7-8 of T60; CH4: Vds of U60.

Figure 18. Key Waveforms on T60 at VBAT = 480 V

Besides the above rails, the reference design also needs a +3.3V rail on both the bus side and battery side. The loads of the +3.3VBA include Vdd1 of the gate drivers, Vdd1/Vdd2 of the digital isolator U201/U200, Vdd of the comparator U160, and the LEDs. We use the buck converter U110 connected to +12V to supply the +3.3VBA rail.

The loads of the +3.3VBU include Vdd2/Vdd1 of the digital isolator U201/U200, and Vcc of the ADCs U180 and U181. The load current is light, so a LDO is used for U93. While the LDO is a lower efficiency solution, it serves another purpose; it is also a dummy load for the +20V rail.

TEST RESULTS

Grid to Battery Operation

Efficiency of Grid to Battery Operation

For Grid to Battery mode, the converter works in a closed loop. We adjust the Vin for different Vo to set the switching frequency around the resonant point to get maximum efficiency. Table 3 shows the input voltage for each output voltage with Sunlord transformer. The Vin with Magsonder

transformer will be 7.2% lower. Figure 19 shows the efficiency across different Vo and load current settings.

Table 3. INPUT VOLTAGE ON EACH OUTPUT VOLTAGE FOR MAXIMUM EFFICIENCY

| Vo (V) | 250 | 300 | 350 | 400 | 450 |
|---------|-----|-----|-----|-----|-----|
| Vin (V) | 355 | 427 | 495 | 566 | 624 |


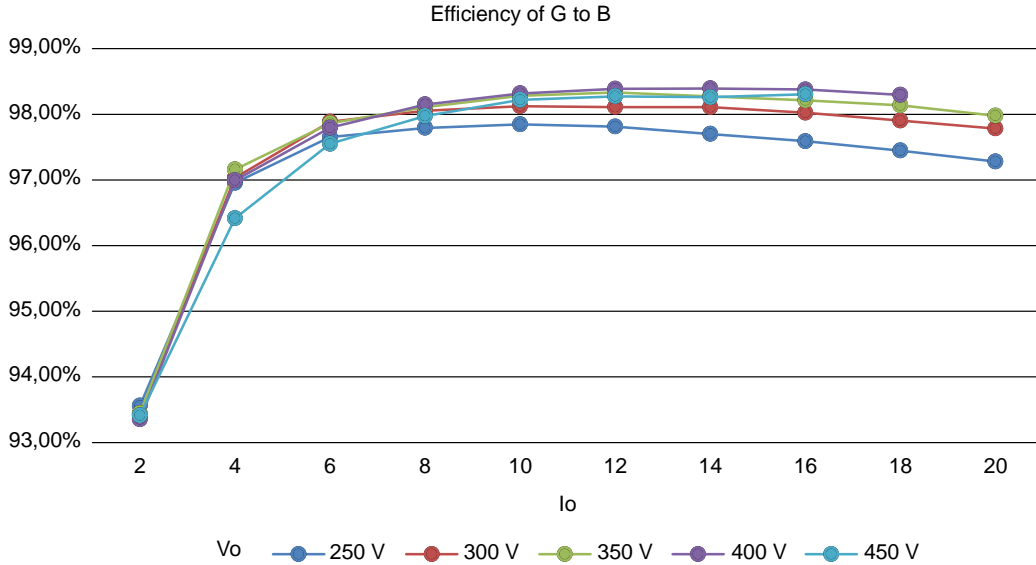


Figure 19. Efficiency for Grid to Battery Mode

Waveforms on Grid to Battery Operation


Figure 20 shows the voltage and current stresses under Vo = 450 V/16 A (Left) and Vo = 350 V/20 A (Right).

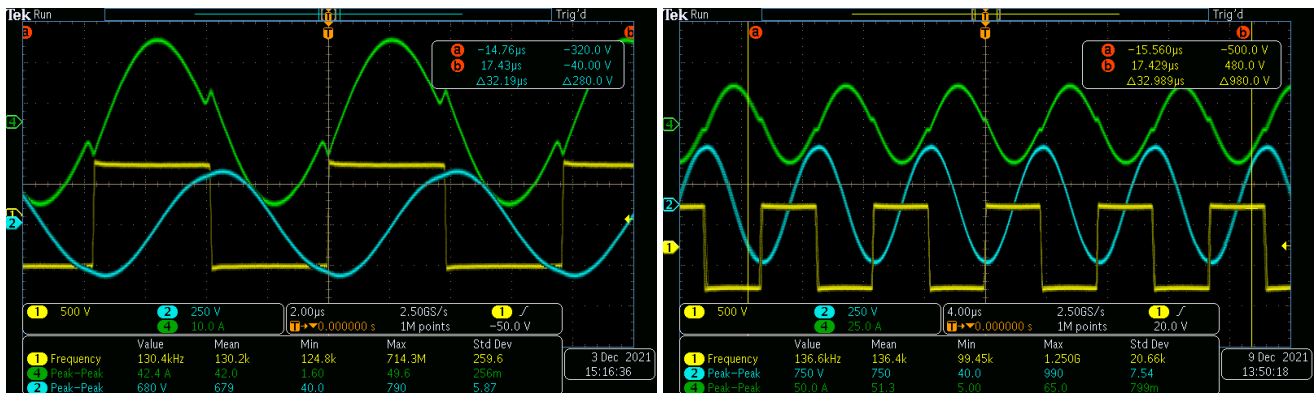

*CH1: Trans UA – Trans UB; CH2: Voltage on Resonant Capacitors; CH4: Current of Resonant tank.

Figure 20. Voltage, Current Stress at Full Load


Figure 21 shows the gate drive signals of the high-side and low-side MOSFETs. We can see the driving voltage and the dead time between each signal.

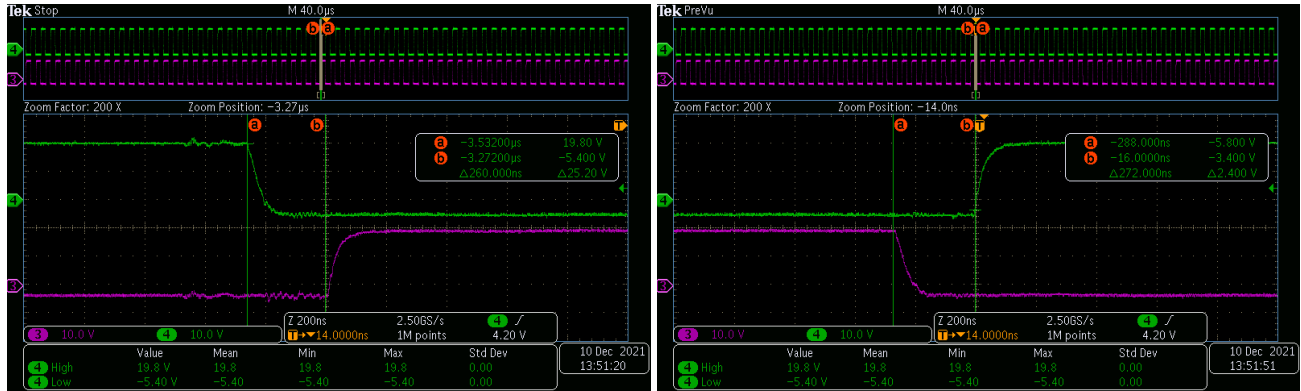

*CH3: Vgs of Q50 (same with Q20); CH4: Vgs of Q30 (same with Q40).

Figure 21. Gate Drive Signal of the SiC MOSFETs

Figure 22 shows the PWM signals from the control interface to the MOSFETs. We can see the delay times on the turn-on and turn-off moment.

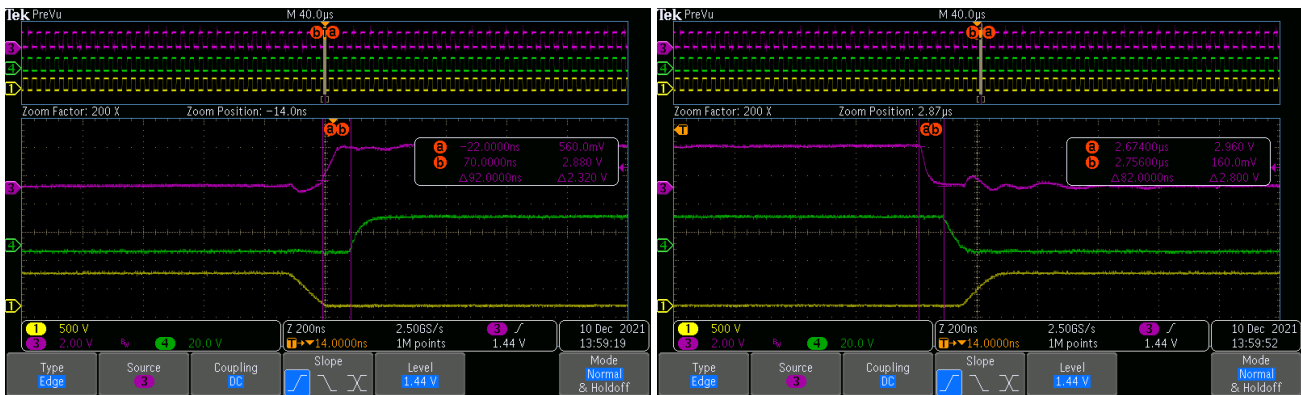


*CH1: Vds of Q30; CH3: Pin17 of the Control interface (LSUA); CH4: Vgs of Q30.

Figure 22. PWM Signals from the Control Interface to the MOSFETs

Figure 23 shows the gate driver waveforms of the synchronous rectifier operation. We can see the synchronous rectifier driver timing minimizes conduction losses and

prevents current feedback from the battery to the transformer. This is achieved with fine control of the gate source drive voltage relative to the turn on and turn off the body diodes.

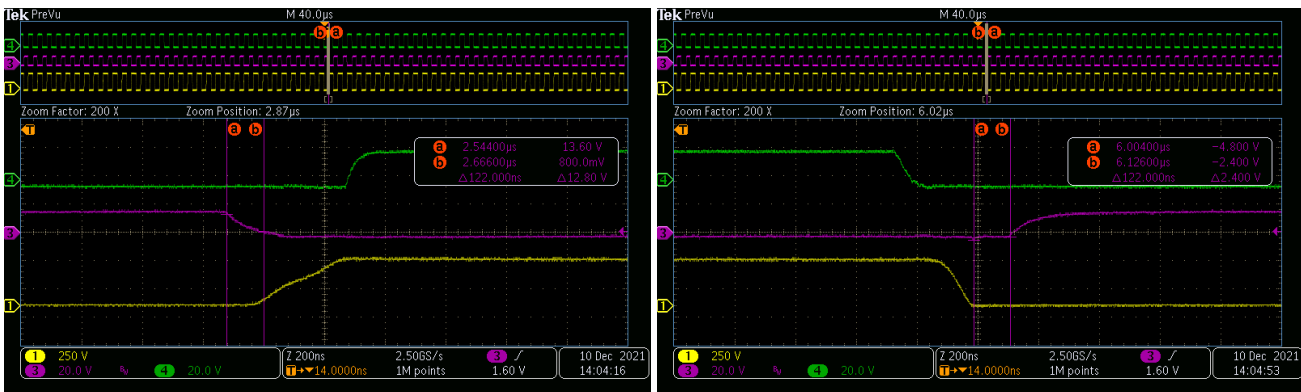

*CH1: Vds of Q150; CH3: Vgs of Q150; CH4: Vgs of Q30.

Figure 23. Gate Driver Waveforms of the Synchronous Rectifier Operation

Battery to Grid Operation

V_{in} and V_{out} for Battery to Grid Operation

In the Battery to Grid mode, the converter works as open loop. The switching frequency is approximately 142 kHz (F₀). Even with V_{in} fixed, the output voltage V_o will have some variation under different load currents. Under a no-load

condition, V_o is much higher and may trip the OVP point due to the parasitic oscillations on the Bus winding of the transformer (the design can handle this without any issues). Table 4 shows the output voltage for different input currents and voltages with the Sunlord transformer. The voltage with the Magsonder transformer will be around 7% lower.

Table 4. OUTPUT VOLTAGE ON DIFFERENT INPUT CURRENT AND VOLTAGE

| I _{in} (A) | 0 | 2 | 4 | 6 | 8 | 10 | 12 | 14 | 16 | 18 | 20 |
|-------------------------|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|
| V _{in} = 250 V | 639 | 363 | 351 | 349 | 348 | 347 | 346 | 344 | 343 | 342 | 340 |
| V _{in} = 300 V | 805 | 434 | 419 | 418 | 417 | 416 | 414 | 413 | 412 | 411 | 410 |
| V _{in} = 350 V | 805 | 507 | 488 | 487 | 486 | 485 | 483 | 482 | 481 | 480 | 479 |
| V _{in} = 400 V | 805 | 581 | 558 | 557 | 556 | 555 | 553 | 552 | 551 | 550 | – |
| V _{in} = 450 V | 805 | 657 | 628 | 627 | 625 | 624 | 623 | 621 | 620 | – | – |

Efficiency for Battery to Grid Operation

Figure 24 shows the efficiency for different V (Battery) and I_{out} (Battery).


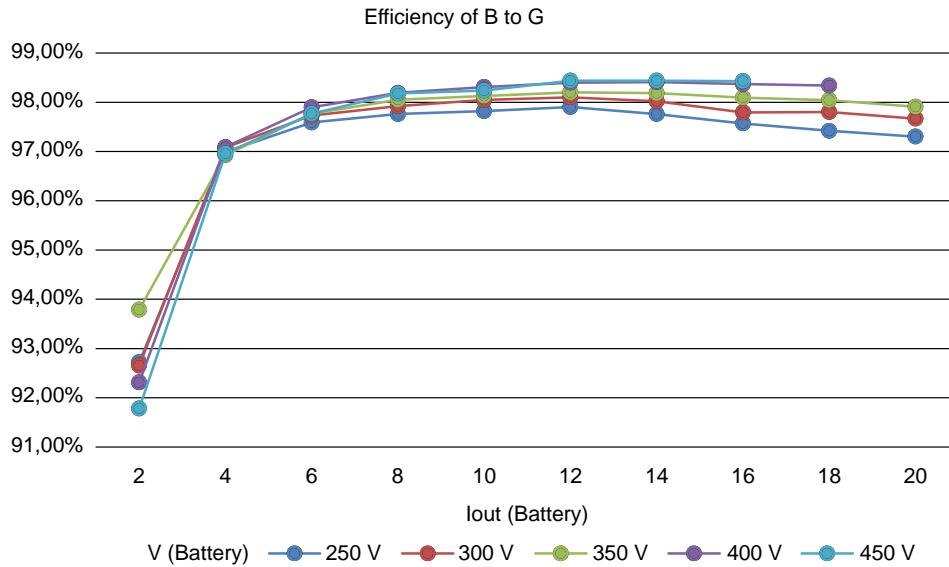


Figure 24. Efficiency for Grid to Battery Mode

Waveforms on Battery to Grid Operation

Figure 25 shows the voltage and current stresses when $V_{in} = 350\text{ V}/20\text{ A}$ (Left) and $V_{in} = 450\text{ V}/16\text{ A}$ (Right).

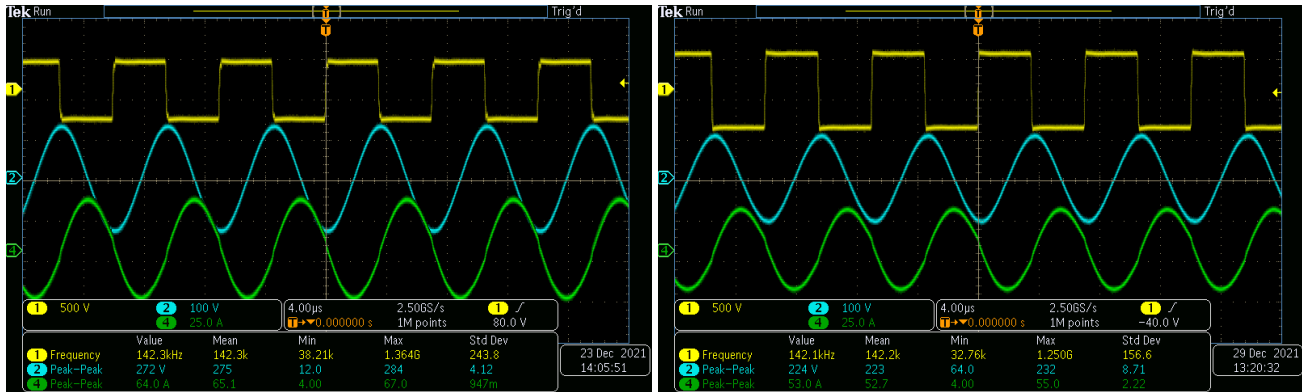

*CH1: TransAB – TransAA; CH2: Voltage on Resonant Capacitors; CH4: Current of Resonant tank.

Figure 25. Voltage, Current Stress on Full Load

PCB Layout

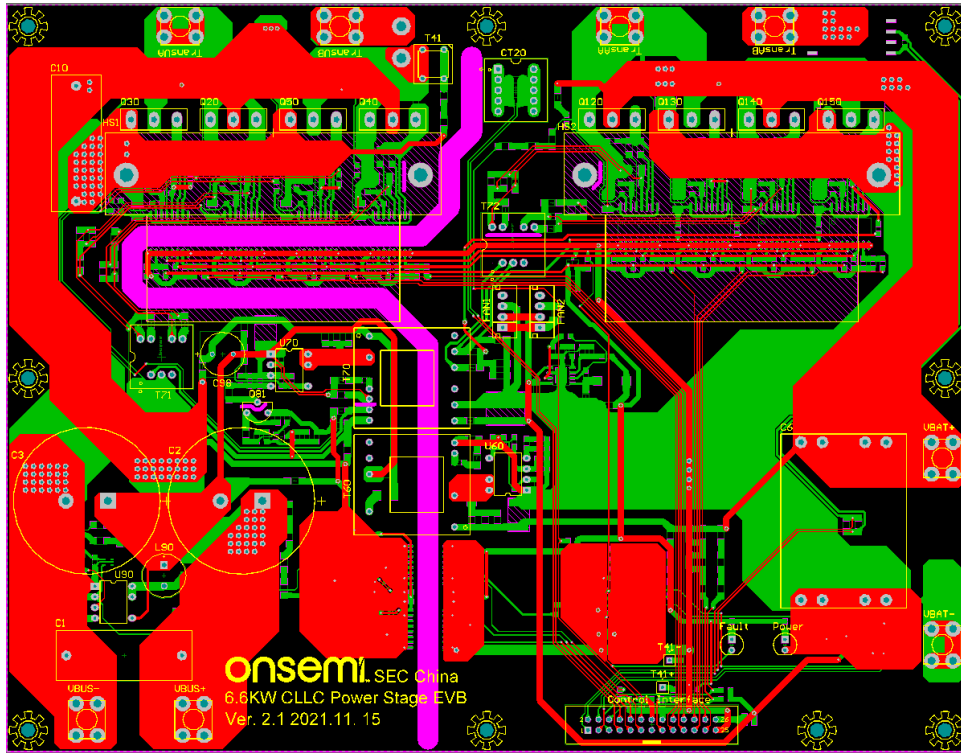


Figure 26. Top View of the Main Board, 228.6 x 177.8 mm

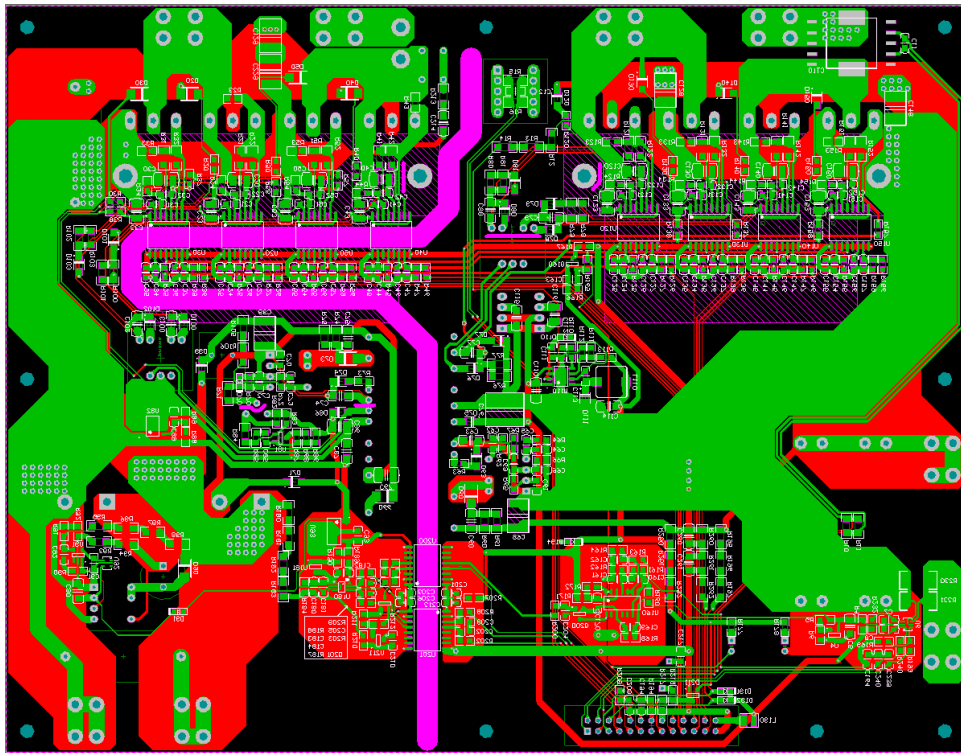


Figure 27. Bottom View of the Main Board, 228.6 x 177.8 mm

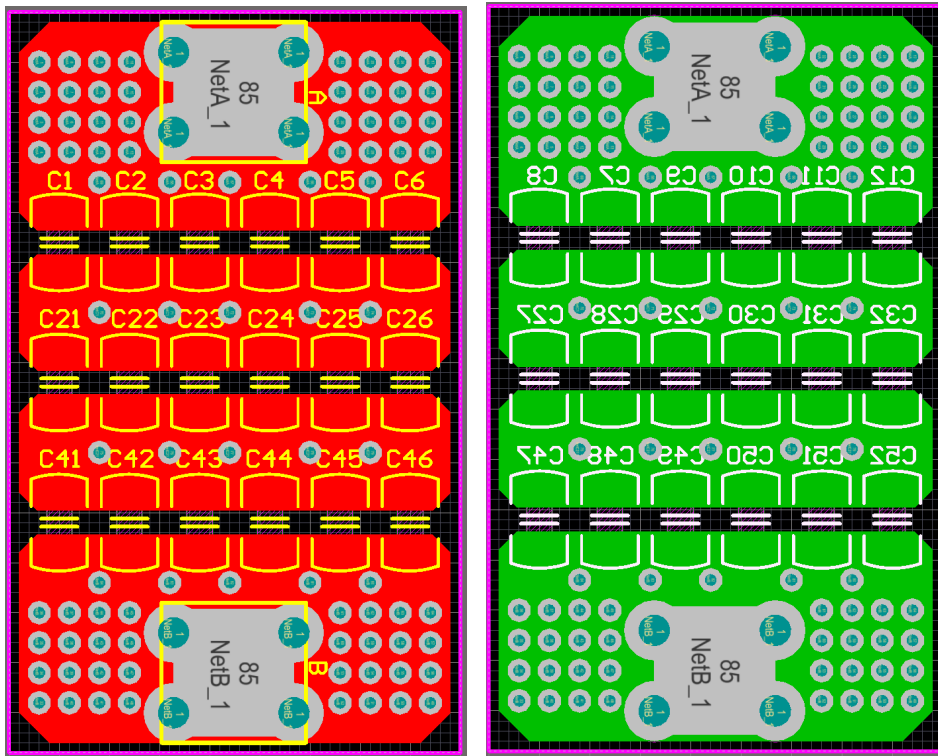


Figure 28. Top, Bottom View of the 3 Rows Resonant Capacitor Board, 47 x 28.6 mm

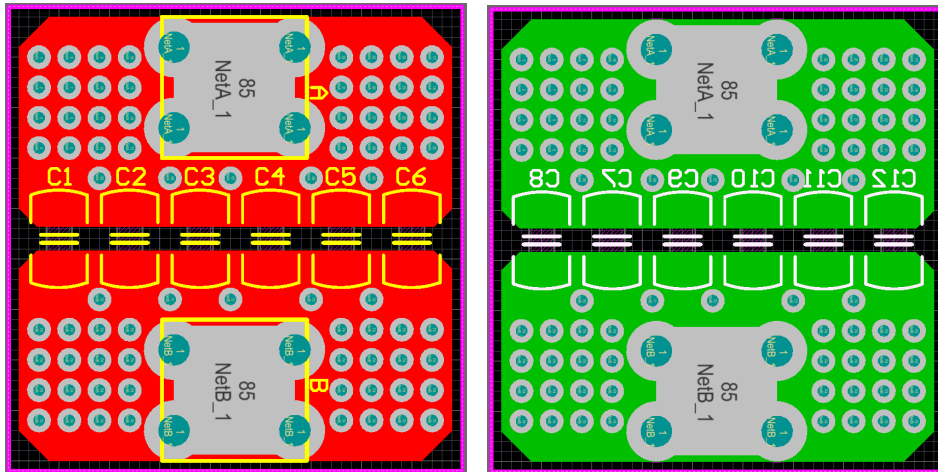


Figure 29. Top, Bottom View of the 1 Row Resonant Capacitor Board, 29.2 x 28.6 mm

TND6378/D

Bill of Materials

Table 5. BOM OF THE MAIN BOARD

| Description | Manufacturer Part Number | Manufacturer | Qty. | Designator |
|---|--------------------------|--------------|------|--|
| IC 12-Bit Low Power SAR ADC, SSop-8 | NCD98010XDPT3G | onsemi | 1 | U180, |
| IC High Speed Quad-Channel Digital Isolator, SOIC-16W | NCID9401 | onsemi | 2 | U200, U201 |
| IC +4/-8 A Galvanic Isolated Gate Driver, SOIC-16W | NCV57000DWR2G | onsemi | 8 | U20, U30, U40, U50, U120, U130, U140, U150 |
| IC 800 V Switcher, 100 kHz, PDIP-7 | FSL538APG | onsemi | 2 | U60, U70 |
| IC 1000 V Switcher, 50 kHz, PDIP-7 | FSL4110LRN | onsemi | 1 | U90 |
| IC Buck Switcher, 1.2 A, 2 MHz, SO8EP | NCV890100PDR2G | onsemi | 1 | U110 |
| IC LDO 400 mA, 3.3 V, SOT-223 | NCV4274CST33T3G | onsemi | 1 | U93 |
| IC Shunt Regulator, SOT23-3L | SC431AVSNT1G | onsemi | 4 | U4, U81, U181, U211 |
| IC Shunt Regulator, Sop-8 | NCV431AIDR2G | onsemi | 1 | U82 |
| IC LDO, 3.3 V, 50 mA, Ultra-Low Iq, SC-88A (SC70-5) | NCV8715SQ33T2G | onsemi | 1 | U92 |
| IC Current Sense Amplifier, SC70-6 | NCV210SQT2G | onsemi | 1 | U6 |
| IC Quad, Single Supply Comparator, Sop-14 | NCV2901DR2G | onsemi | 1 | U160 |
| IC RRO OP Amplifier, SOT-23 5L | NCV2003SN2T1G | onsemi | 1 | U91 |
| | | | | |
| SiC MOSFET 40 mΩ 1200 V, TO-247 | NVHL040N120SC1 | onsemi | 4 | Q20, Q30, Q40, Q50 |
| SiC MOSFET 20 mΩ 900 V, TO-247 | NVHL020N090SC1 | onsemi | 4 | Q120, Q130, Q140, Q150 |
| MOSFET 600 V 11.5 Ω, TO92 | FQN1N60CTA | onsemi | 1 | Q81 |
| Transistor 40 V 0.6 A NPN, SOT23 | SMMBT4401LT1G | onsemi | 1 | Q200 |
| Transistor 40 V 0.6 A PNP, SOT23 | SMMBT2907ALT1G | onsemi | 2 | Q160, Q201 |
| | | | | |
| Diode 600 V 1 A 75 nS, SOD-123FL | NRVUS1JFA | onsemi | 6 | D71, D99, D120, D130, D140, D150 |
| Diode 1000 V 1 A, SMA | NRVA4007T3G | onsemi | 2 | D60, D73 |
| Diode 1000 V 1.5 A 75 nS, SMA | NRVUS2MA | onsemi | 6 | D20, D30, D40, D50, D66, D90 |
| Diode 100 V 0.8 A 150 nS, SOD-123FL | NRVHPRS1BFA | onsemi | 2 | D63, D74 |
| Schottky Diode 2 A 150 V, SOD-123FL | NRVBS215FA | onsemi | 6 | D76, D78, D80, D86, D100, D102 |
| Schottky Diode 1 A 20 V, SOD-123FL | NRVB120VLSFT1G | onsemi | 1 | D111 |
| Schottky Diode 3 A 60 V, SOD-123FL | NRVBSS36FA | onsemi | 1 | D75 |
| Schottky Diode Dual 0.2 A 30 V, SOT-23-3L | NSVBAT54SWT1G | onsemi | 2 | D211 |
| Switching Diode 0.2 A 100 V, SOD323 | BAS16H | onsemi | 6 | D70, D91, D110, D191, D192, D194 |
| ZENER Diode 0.5 W 4.7 V, SOD123 | SZMMSZ4V7T1G | onsemi | 5 | D77, D79, D81, D101, D103 |
| LED D = 5 mm THT Green | 151051VS04000 | WURTH | 1 | Power |
| LED D = 5 mm THT Red | 151051RS11000 | WURTH | 1 | Fault |
| | | | | |
| Chip resistor 0805 2.2 Ω-J | | Any | 10 | R24, R34, R44, R54, R63, R73, R124, R134, R144, R154 |
| Chip resistor 0805 4.7 Ω-J | | Any | 16 | R25, R35, R37, R38, R45, R55, R57, R58, R125, R135, R137, R138, R145, R155, R157, R158 |
| Chip resistor 0805 10 Ω-J | | Any | 4 | R171, R189, R207, R232 |
| Chip resistor 0805 100 Ω-J | | Any | 15 | R26, R36, R46, R56, R111, R126, R136, R146, R156, R187, R188, R202, R203, R205, R208 |
| Chip resistor 0805 300 Ω-J | | Any | 1 | R113 |

TND6378/D

Table 5. BOM OF THE MAIN BOARD (continued)

| Description | Manufacturer Part Number | Manufacturer | Qty. | Designator |
|------------------------------|--------------------------|--------------|------|--|
| Chip resistor 0805 330 Ω-J | | Any | 2 | R177, R178 |
| Chip resistor 0805 470 Ω-J | | Any | 1 | R190 |
| Chip resistor 0805 1 kΩ-J | | Any | 12 | R20, R30, R40, R50, R120, R130, R140, R150, R167, R200, R211, R219 |
| Chip resistor 0805 1.8 kΩ-J | | Any | 1 | R162, |
| Chip resistor 0805 2.2 kΩ-J | | Any | 14 | R4, R27, R39, R47, R59, R112, R127, R139, R147, R159, R166, R172, R193, R240 |
| Chip resistor 0805 4.7 kΩ-J | | Any | 6 | R85, R87, R88, R89, R165, R209 |
| Chip resistor 0805 4.75 kΩ-F | | Any | 2 | R6, R164 |
| Chip resistor 0805 6.65 kΩ-F | | Any | 1 | R5 |
| Chip resistor 0805 10 kΩ-J | | Any | 16 | R23, R33, R43, R53, R64, R83, R110, R123, R133, R143, R153, R161, R163, R210, R212, R217 |
| Chip resistor 0805 11.5 kΩ-F | | Any | 1 | R168 |
| Chip resistor 0805 12 kΩ-J | | Any | 1 | R169 |
| Chip resistor 0805 12.7 kΩ-F | | Any | 3 | R91, R92, R184 |
| Chip resistor 0805 20 kΩ-J | | Any | 2 | R72, R82 |
| Chip resistor 0805 27 kΩ-J | | Any | 1 | R160 |
| Chip resistor 0805 39 kΩ-J | | Any | 1 | R86 |
| Chip resistor 0805 43 kΩ-J | | Any | 2 | R66, R67 |
| Chip resistor 0805 56 kΩ-J | | Any | 1 | R68 |
| Chip resistor 0805 100 kΩ-J | | Any | 3 | R62, R70, R90 |
| Chip resistor 0805 220 kΩ-J | | Any | 1 | R65 |
| Chip resistor 1206 4.7 Ω-J | | Any | 16 | R21, R22, R31, R32, R41, R42, R51, R52, R121, R122, R131, R132, R141, R142, R151, R152 |
| Chip resistor 1206 100 Ω-J | | Any | 2 | R10, R11 |
| Chip resistor 1206 150 Ω-J | | Any | 2 | R15, R16 |
| Chip resistor 1206 1 kΩ-J | | Any | 1 | R213 |
| Chip resistor 1206 2.2 kΩ-J | | Any | 6 | R76, R77, R78, R79, R80, R81 |
| Chip resistor 1206 3.9 kΩ-J | | Any | 4 | R100, R101, R102, R103 |
| Chip resistor 1206 47 kΩ-J | | Any | 2 | R71, R84 |
| Chip resistor 1206 150 kΩ-J | | Any | 3 | R12, R13, R14 |
| Chip resistor 1206 470 kΩ-J | | Any | 4 | R60, R61, R74, R75 |
| Chip resistor 1206 1 MΩ-J | | Any | 18 | R93, R94, R95, R96, R97, R98, R105, R106, R180, R181, R182, R183, R195, R196, R197, R250, R251, R252 |
| Chip resistor 1206 3 MΩ-J | | Any | 3 | R260, R261, R262, |
| Chip resistor 2512 2 mΩ-F | SMA25A2FR002T | SART | 2 | R230, R231 |
| Chip resistor 2512 2 mΩ-F | ERJMS4SF2M0* | Panasonic | 2 | R230, R231 |
| MLCC 0805-450V-100pFJ-NP0 | CGA4C4C0G2W101J | TDK | 33 | C11, C12, C21, C26, C27, C31, C36, C37, C41, C46, C47, C51, C56, C57, C121, C126, C127, C131, C136, C137, C141, C146, C147, C151, C156, C157, C180, C183, C184, C202, C205, C208, C210 |

TND6378/D

Table 5. BOM OF THE MAIN BOARD (continued)

| Description | Manufacturer Part Number | Manufacturer | Qty. | Designator |
|---------------------------|--------------------------|--------------|------|--|
| MLCC 0805-450V-100pFJ-NP0 | GCM21A5C2J101JX01 | Murata | 33 | C11, C12, C21, C26, C27, C31, C36, C37, C41, C46, C47, C51, C56, C57, C121, C126, C127, C131, C136, C137, C141, C146, C147, C151, C156, C157, C180, C183, C184, C202, C205, C208, C210 |
| MLCC 0805-450V-471J-NP0 | CGA4C4C0G2W471J | TDK | 2 | C64, C163 |
| MLCC 0805-450V-471J-NP0 | GCM21A5C2J471JX01 | Murata | 2 | C64, C163 |
| MLCC 0805-100V-102J-NP0 | CGA4C2C0G2A102J | TDK | 10 | C62, C66, C72, C73, C88, C164, C169, C204, C239, C240 |
| MLCC 0805-50V-222J-NP0 | CGA4C2C0G1H222J | TDK | 1 | C112 |
| MLCC 0805-50V-223J-NP0 | CGA4J2C0G1H223J125AA | TDK | 3 | C65, C69, C85 |
| MLCC 0805-50V-223J-NP0 | GCM21B5C1H223JA16 | Murata | 3 | C65, C69, C85 |
| MLCC 0805-100V-104K-X7R | CGA4J2X7R2A104K | TDK | 24 | C7, C8, C24, C34, C44, C54, C61, C70, C92, C111, C113, C124, C134, C144, C154, C160, C161, C162, C170, C181, C182, C203, C212, C217 |
| MLCC 0805-100V-104K-X7R | GCM21BR72A104KA37L | Murata | 24 | C7, C8, C24, C34, C44, C54, C61, C70, C92, C111, C113, C124, C134, C144, C154, C160, C161, C162, C170, C181, C182, C203, C212, C217 |
| MLCC 0805-50V-105K-X7R | CGA4J3X7R1H105K125AB | TDK | 12 | C22, C32, C42, C52, C91, C93, C122, C132, C142, C152, C201, C206 |
| MLCC 0805-50V-105K-X7R | GCM21BR71H105KA03L | Murata | 12 | C22, C32, C42, C52, C91, C93, C122, C132, C142, C152, C201, C206 |
| MLCC 0805-25V-225K-X7R | CGA4J3X7R1E225K | TDK | 8 | C25, C35, C45, C55, C125, C135, C145, C155 |
| MLCC 0805-25V-225K-X7R | GCM21BR71E225KA73L | Murata | 8 | C25, C35, C45, C55, C125, C135, C145, C155 |
| MLCC 1206-50V-475K-X7R | CGA5L3X7R1H475K | TDK | 2 | C100, C102 |
| MLCC 1206-50V-475K-X7R | GCM31CC71H475KA03 | Murata | 2 | C100, C102 |
| MLCC 1206-25V-106K-X7R | CGA5L1X7R1E106K | TDK | 10 | C5, C74, C77, C79, C80, C87, C90, C110, C114, C115 |
| MLCC 1206-25V-106K-X7R | GCM31CC71E106KA03 | Murata | 10 | C5, C74, C77, C79, C80, C87, C90, C110, C114, C115 |
| MLCC 1206-50V-104J-C0G | CGA5L2C0G1H104J160AA | TDK | 1 | C63 |
| MLCC 1206-50V-104J-C0G | GCM31C5C1H104JA16 | Murata | 1 | C63 |
| MLCC 1206-630V-222K-X7R | CGA5H4X7R2J222K | TDK | 5 | C60, C75, C214, C260, C261 |
| MLCC 1206-630V-222K-X7R | GCJ31BR72J222KXJ1 | Murata | 5 | C60, C75, C214, C260, C261 |
| MLCC 1210-25V-226K-X7R | CGA6P3X7R1E226M250AB | TDK | 18 | C20, C23, C30, C33, C40, C43, C50, C53, C86, C116, C120, C123, C130, C133, C140, C143, C150, C153 |
| MLCC 1210-25V-226K-X7R | GCM32EC71E226KE36 | Murata | 18 | C20, C23, C30, C33, C40, C43, C50, C53, C86, C116, C120, C123, C130, C133, C140, C143, C150, C153 |
| MLCC 1210-630V-154K-X7T | CGA6M1X7T2J154K200AC | TDK | 1 | C67 |
| MLCC 1210-630V-154K-X7T | GC355DD72J154KX01 | Murata | 1 | C67 |
| MLCC 2220-630V-105M-X7T | CAA572X7T2J105M | TDK | 6 | C68, C99, C128, C129, C148, C229 |
| MLCC 2220-630V-105M-X7T | KC355TD7LQ105MV01 | Murata | 6 | C68, C99, C128, C129, C148, C229 |
| MLCC 2220-35V-157M-X7T | CAA573X7R1E157M | TDK | 1 | C76 |

TND6378/D

Table 5. BOM OF THE MAIN BOARD (continued)

| Description | Manufacturer Part Number | Manufacturer | Qty. | Designator |
|--|--------------------------|--------------|------|--|
| THT Film Capacitor 1 μ F, 1100 V | ECWFG1B105J | Panasonic | 2 | C1, C10 |
| THT Film Capacitor X2 470 nF, 1000 V | 890493427007CS | WURTH | 2 | C1, C10 |
| Film Cap 800 V 30 μ F PP | EZPV80306MTB | Panasonic | 1 | C6 |
| E-Cap 450 V-680 μ F-105 (35 X 57 mm) | 861141486026 | WURTH | 2 | C2, C3, |
| E-Cap 450 V-680 μ F-105 (35 X 57 mm) | B43508A5687M062 | TDK | 2 | C2, C3, |
| Current Transformer EE13/7/4 | 750316796 | WURTH | 1 | CT10 |
| Current Transformer EE13/6/6 | 750344930 | WURTH | 1 | CT20 |
| Auxiliary Power Transformer B to G PQ2620/14p | 750344929 | WURTH | 1 | T60 |
| Auxiliary Power Transformer G to B PQ2620/14p | 750344928 | WURTH | 1 | T70 |
| Pulse Transformer EE13/6/6/ 1:1 10-Terminal, THT | 750344931 | WURTH | 2 | T71, T72 |
| Pulse Transformer EE8 56:1 4-Terminal, THT | 750345072 | WURTH | 1 | T41 |
| SMD Inductor 3225-100 μ H-0.12 A | NLCV32T-101K-EFD | TDK | 1 | L190 |
| SMD Inductor 3225-100 μ H-0.26 A | LQH3NPH101MMEL | Murata | 1 | L190 |
| SMD Inductor 3225-100 μ H-0.3 A | 74403042101 | WURTH | 1 | L190 |
| Radial Leaded Inductor 1014, 2200 μ H, 0.48 A | 7447480222 | WURTH | 1 | L90 |
| SMD Inductor 7 X 7 X 3.5 mm-22 μ H-1.6 A | 784778220 | WURTH | 1 | L110 |
| SMD Inductor 7 X 7 X 4.5 mm-22 μ H-1.7 A | SPM7045VT-220M-D | TDK | 1 | L110 |
| SMD Inductor 7 X 7 X 4.5 mm-22 μ H-2.9 A | ETQP4M220KFM | Panasonic | 1 | L110 |
| SMD Inductor 7 X 6 X 2.8 mm-22 μ H-2.5 A | AMP0603H220MT | Sunlord | 1 | L110 |
| Main transformer | ATWPPQ655462B202T | Sunlord | 1 | Outside of the board |
| Main transformer | PTX6R6K-17025-r | Magsonder | 1 | Outside of the board |
| Male Box Header WR-BHD, THT, Vertical, 2.54 mm, 26 pins | 61202621621 | WURTH | 1 | Control_Interface |
| Connector 5 mm Screw type. 200 X 300 mil | 74760050 | WURTH | 8 | VBUS+, VBUS-, VBAT+, VBAT-, TransUA, TransUB, TransAA, TransAB |
| Connector 2.54 mm 2 Pin | Header 4 | Any | 2 | FAN1, FAN2 |
| Heat Sink | 80 x 60 x 20 | Any | 2 | HS1, HS2 |
| FAN 60 X 60 X 25 mm 12 V 0.27 A | AFB0612SH | DELTA | 2 | HS1, HS2 |

*The adjacent items in same shadow are optional from different manufacturer.

Table 6. BOM OF THE 3 ROWS RESONATE CAPACITOR BOARD

| Description | Manufacturer Part Number | Manufacturer | Qty. | Designator |
|--------------------------|--------------------------|--------------|------|--|
| MLCC 1210-1000V-223J-C0G | CGA6P1C0G3A223JT0Y0N | TDK | 30 | C1, C2, C3, C4, C5, C6, C7, C9, C10, C11, C21, C22, C23, C24, C25, C26, C28, C29, C30, C31, C41, C42, C43, C44, C45, C46, C48, C49, C50, C51 |
| MLCC 1210-630V-223J-C0G | GCM32E5C2J223JX03L | Murata | 30 | C1, C2, C3, C4, C5, C6, C7, C9, C10, C11, C21, C22, C23, C24, C25, C26, C28, C29, C30, C31, C41, C42, C43, C44, C45, C46, C48, C49, C50, C51 |

*The adjacent items in same shadow are optional in different manufacturer.

TND6378/D

Table 7. BOM OF THE 1 ROW RESONATE CAPACITOR BOARD

| Description | Manufacturer Part Number | Manufacturer | Qty. | Designator |
|--------------------------|--------------------------|--------------|------|---|
| MLCC 1210-1000V-223J-C0G | CGA6P1C0G3A223JT0Y0N | TDK | 12 | C1, C2, C3, C4, C5, C6, C7, C8, C9, C10, C11, C12 |
| MLCC 1210-630V-223J-C0G | GCM32E5C2J223JX03L | Murata | 12 | C1, C2, C3, C4, C5, C6, C7, C8, C9, C10, C11, C12 |

*The adjacent items in same shadow are optional from different manufacturers.

onsemi is licensed by the Philips Corporation to carry the I²C bus protocol.

onsemi, onsemi, and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "onsemi" or its affiliates and/or subsidiaries in the United States and/or other countries. onsemi owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of onsemi's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. onsemi reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and onsemi makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does onsemi assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using onsemi products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by onsemi. "Typical" parameters which may be provided in onsemi data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. onsemi does not convey any license under any of its intellectual property rights nor the rights of others. onsemi products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use onsemi products for any such unintended or unauthorized application, Buyer shall indemnify and hold onsemi and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that onsemi was negligent regarding the design or manufacture of the part. onsemi is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:
Email Requests to: orderlit@onsemi.com

onsemi Website: www.onsemi.com

TECHNICAL SUPPORT
North American Technical Support:
Voice Mail: 1 800-282-9855 Toll Free USA/Canada
Phone: 011 421 33 790 2910

Europe, Middle East and Africa Technical Support:
Phone: 00421 33 790 2910
For additional information, please contact your local Sales Representative