



SiC Simulations with Physical & Scalable Models

Tips and Applications

Didier Balocco

EMEA Business Marketing Engineer



Content

- Introduction : Why Physical & Scalable models are the Best ?
- Physical & Scalable Simulation Model Capabilities : Tips and Interesting Results
 - Die Nodes Access Inside the Package : What is happening internally ?
 - Corner Models : Nothing is Perfect...
 - Electro-Thermal Simulations : Using Cauer Networks.
 - Switching Losses vs V_{GS} , Package and Structure : Using Double Pulse Measurement
- Topologies Simulations with Physical & Scalable Models (Virtual Prototyping)
 - Flying Capacitor Boost : DC-DC deep analysis
 - I-NPC vs T-NPC : Which is the best cell ?
 - 6-Pack Boost Active Front End or 3-Phase Grid Power Factor Corrector
- Conclusion and References

Why Physical & Scalable models are the Best ?

Physically Based SPICE Models for SiC MOSFETs

 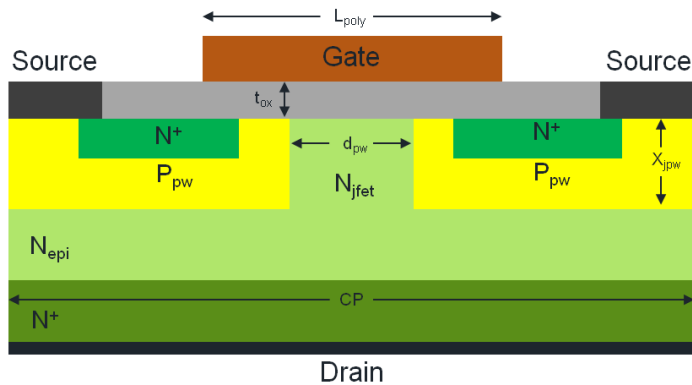Each zone inside the physical structure is modeled by a device.
Each device equation considers dimensions and physics quantities
- Current density, Electrical field, Temperature, ...




Physical Structure \longrightarrow Physical & Scalable Model

- Contains
 - SiC Physics Equations
 - One model per Technology
 - Electro-Thermal
 - Can predict performances of not available parts...
- Benefits
 - Accurate, consistent, and correlated with process variation modeling
 - Best IC industry standard practice


SuperJunction Output Capacitor (Coss) Simulation

- With Behavioral Model

 

✗ It is clear the behavioral model cannot capture the nearly 3-decade drop in output capacitance inherent to all Super-Junctions


- With Physical & Scalable Model

 


✓ Physical & Scalable well predicts the 3-decade drop in C_{oss} .

Resonant Transition Simulation under Constant Current

Coss comparison

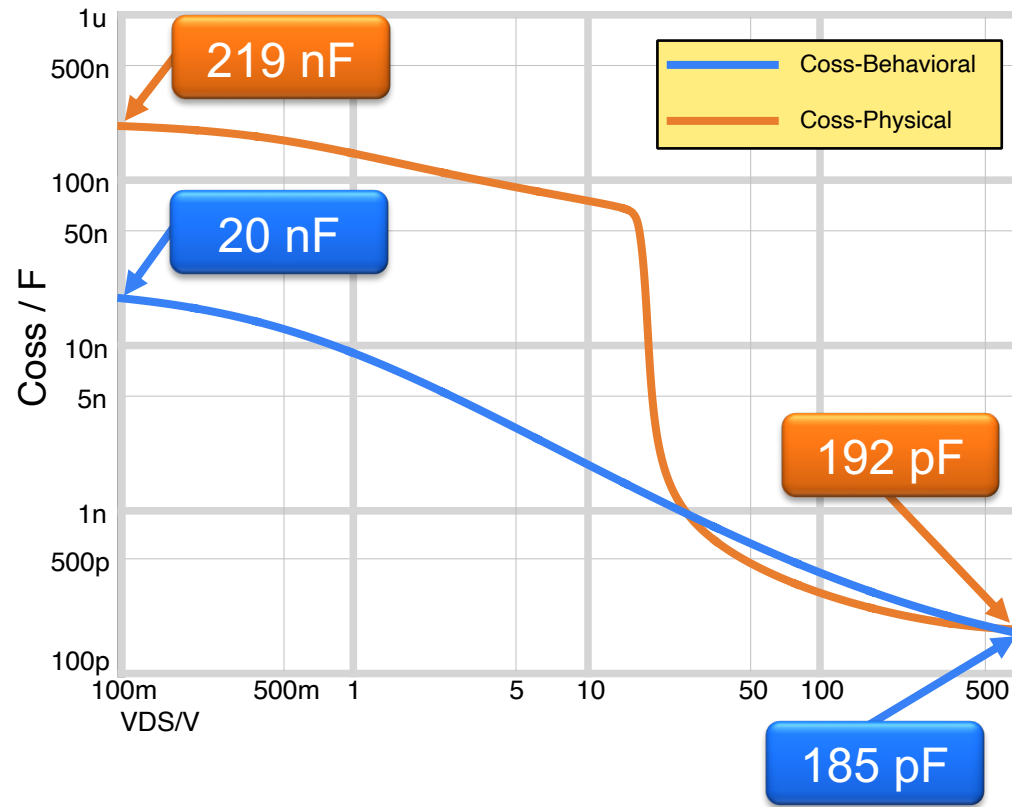

Resonant Transition

 

Physical & Scalable Simulation Model Capabilities


Tips and Interesting Results

Die Nodes Access Inside the Package

What is happening internally ?

Access Die Nodes

- Schematic

 


- Internal node names :
 - Ends with a 'i'
 - In SIMetrix : like '**Qn:xy:di**'
- Useful to study package parasitic impedances effects on waveforms...


Drain-to-Source voltage differences

Light-colored = Die nodes
Dark-colored = Pin nodes

- Turn-ON

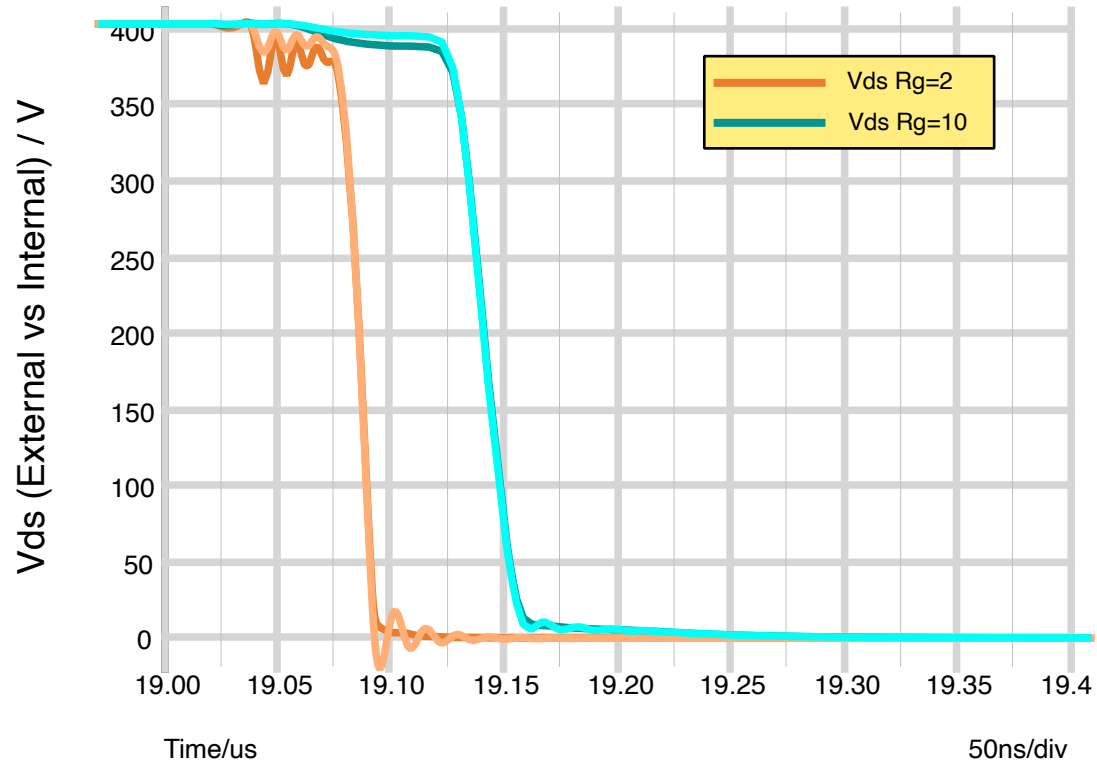

- Turn-OFF

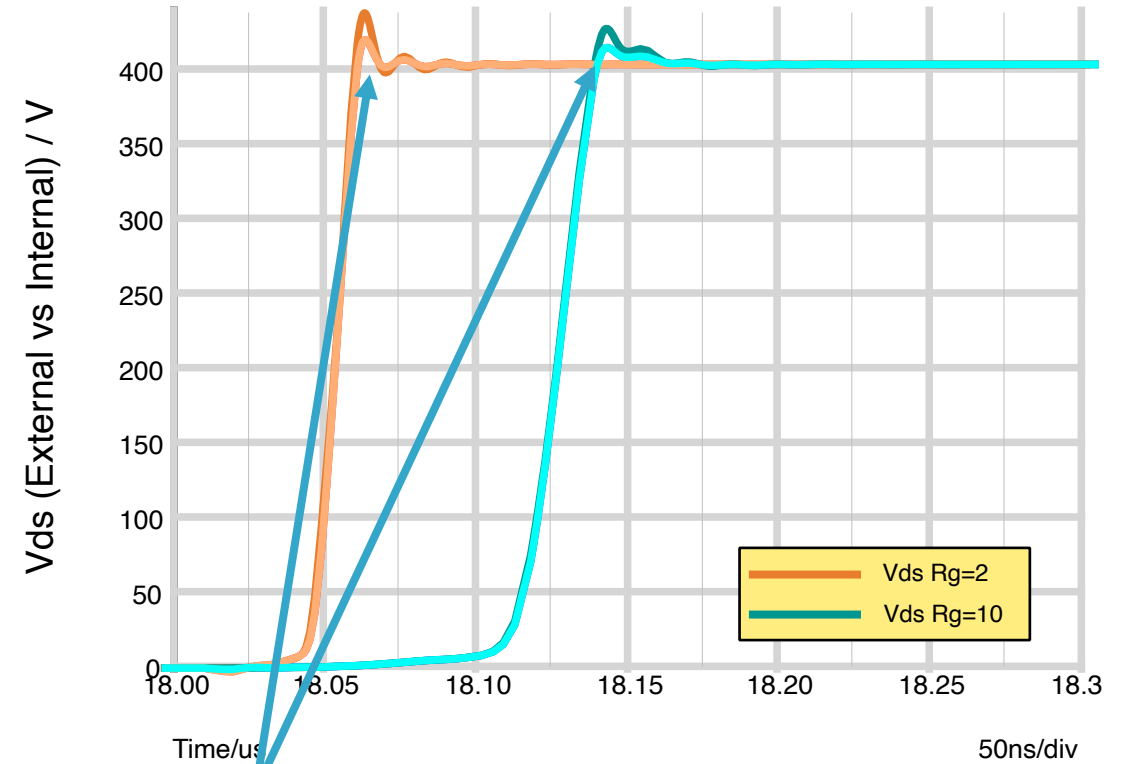


Less overvoltage stress on the die than seen on the pins

Gate-to-Source voltage differences vs External Gate Resistor


MOSFET with LOW internal Rg

MOSFET with HIGH internal Rg

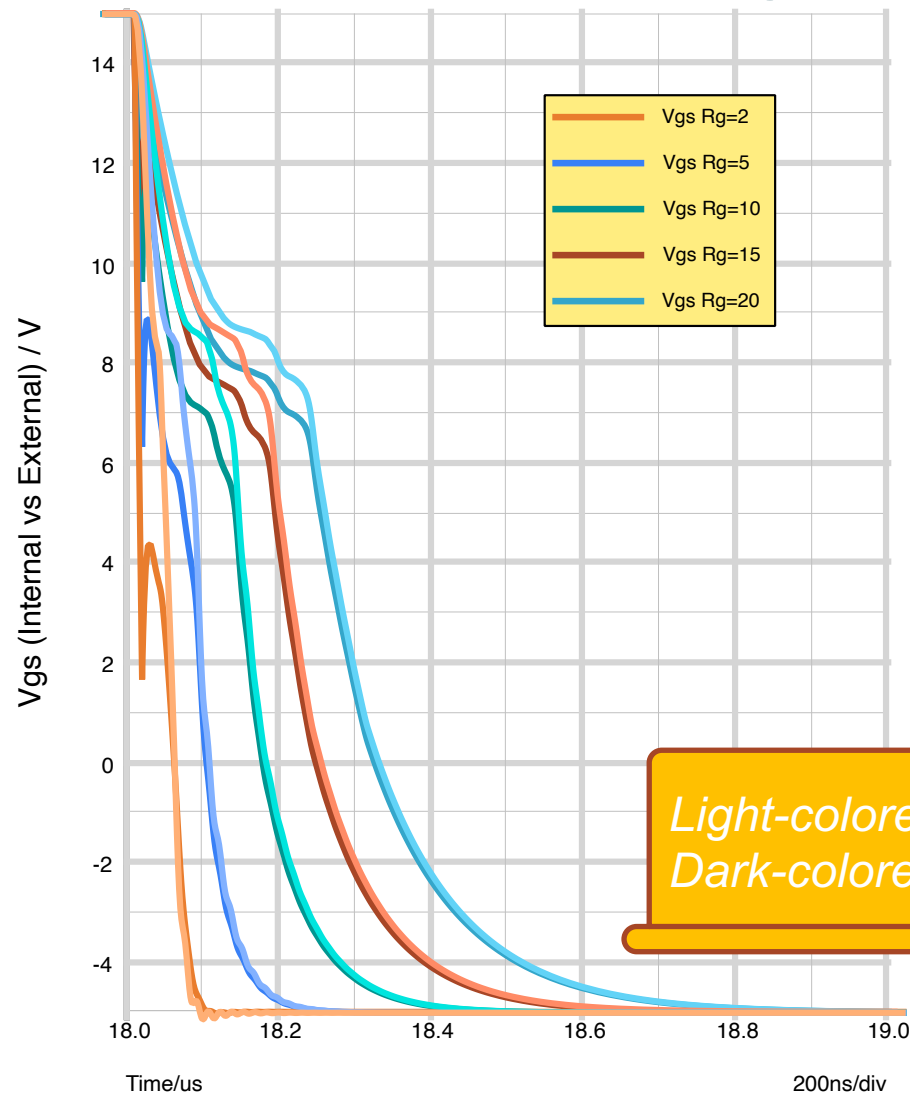

More delay

Less Ringings

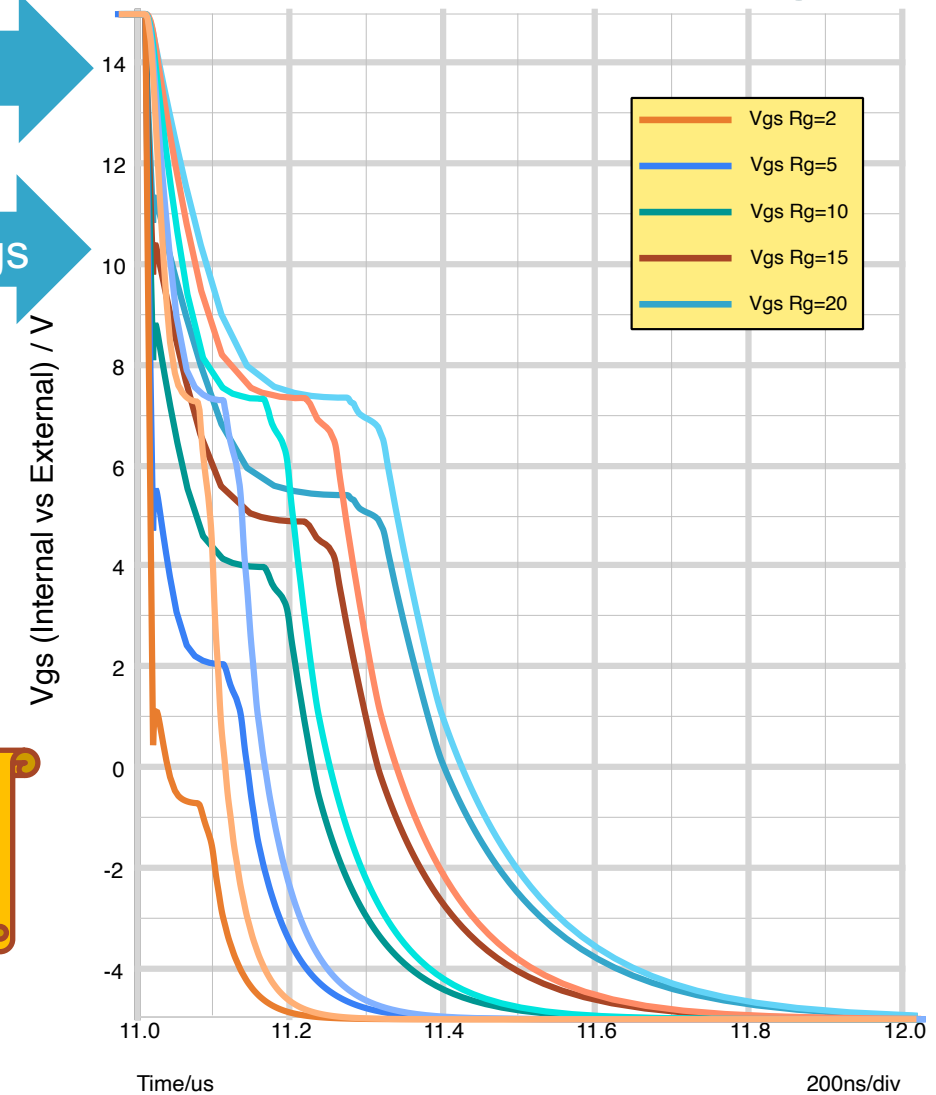


Light-colored = Die nodes
Dark-colored = Pin nodes

Gate-to-Source voltage differences vs External Gate Resistor

Impact...

- The delays between external gate signal and internal gate signal when crossing the Threshold are :
 - For $R_g = 5 \Omega$ → Delay = 30 ns
 - For $R_g = 2 \Omega$ → Delay = 70 ns...
- It is a large difference !
- With High Internal Gate Resistance, In Half- or Full-Bridge, Wrong delays can lead malfunction...
 - Due to the bad information available when looking to external gate signal only.

MOSFET with HIGH internal R_g (Details)

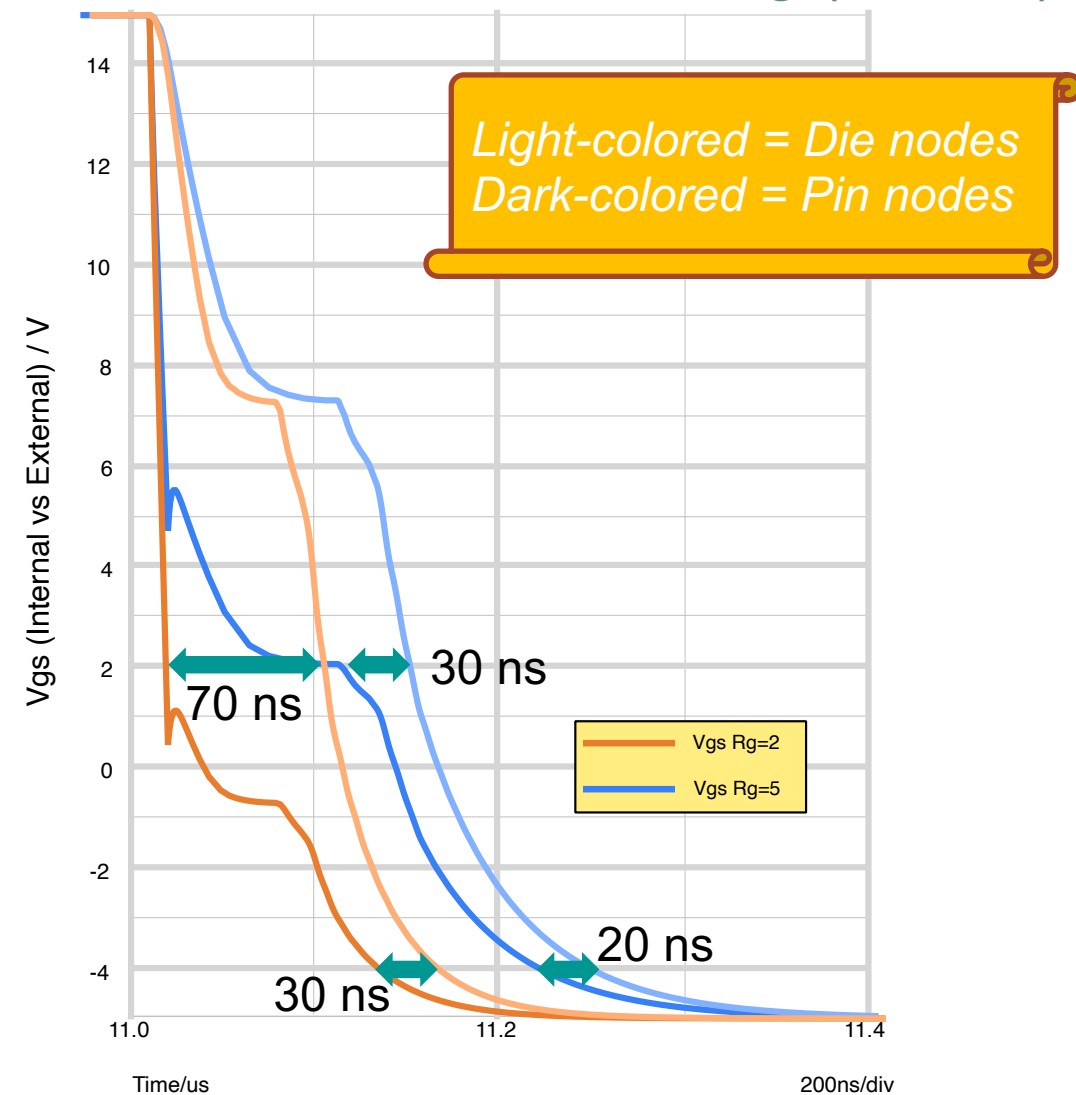


Corner Models


Nothing is Perfect...

Corner Models

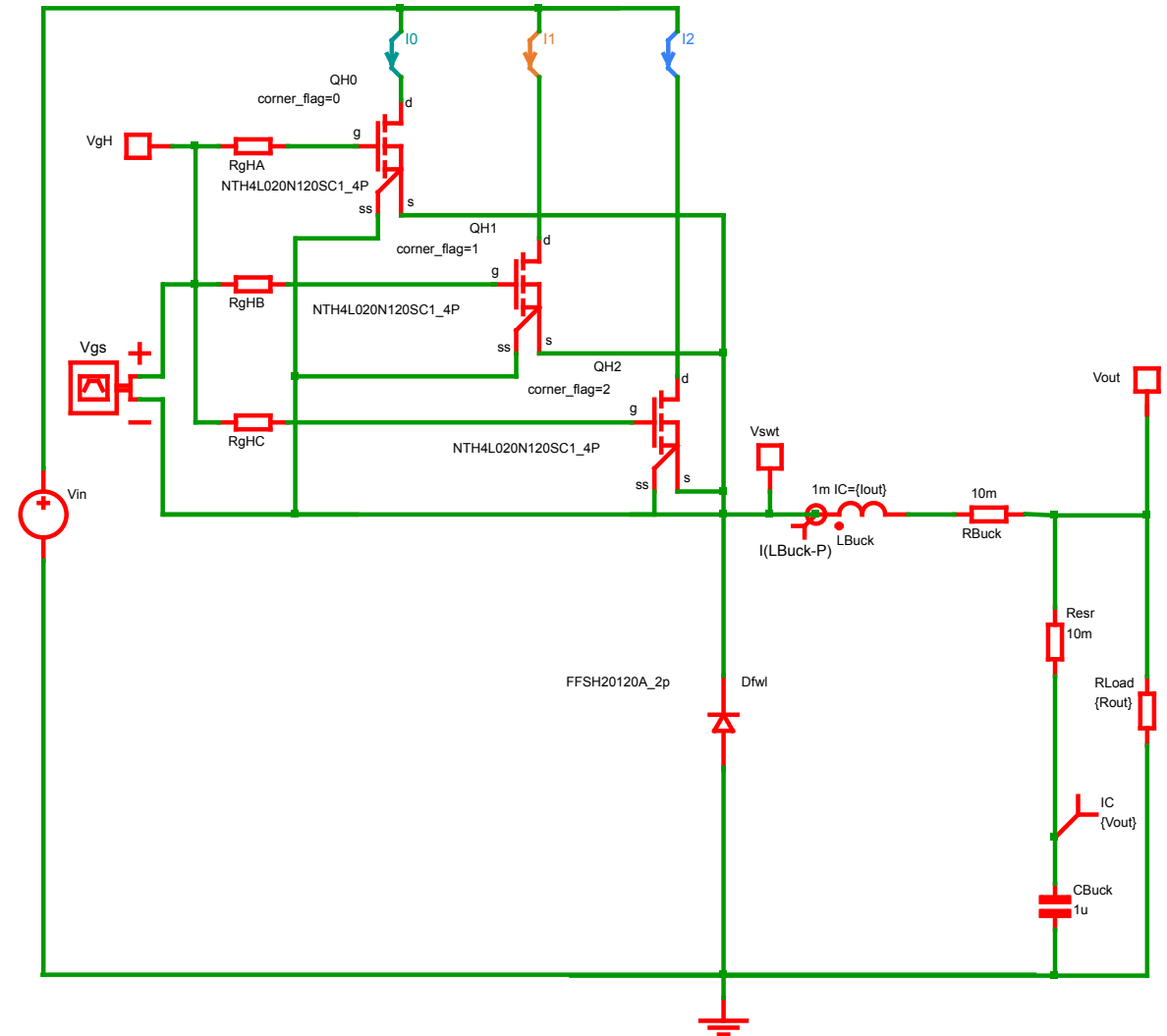- Models online are made and calibrated to give nominal or typical values
- Parameters have Gaussian distribution
- Corner models are the :
 - Maximum threshold device &
 - Minimum threshold device.
- What happens if we parallel them ?




Buck stage waveforms with Corner Models

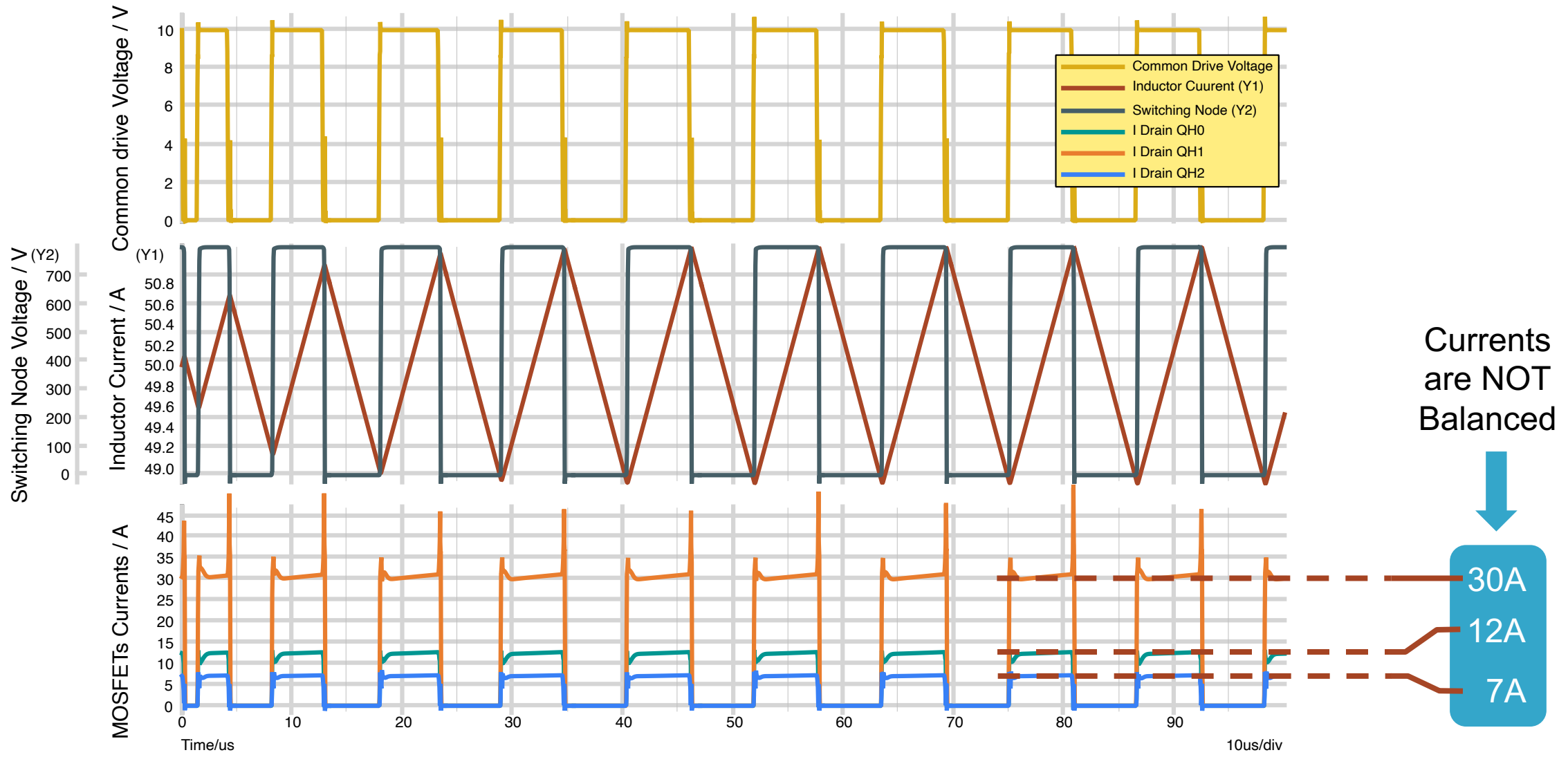


Buck stage waveforms with Corner Models

Light-colored = Die nodes
Dark-colored = Pin nodes

• Turn-ON

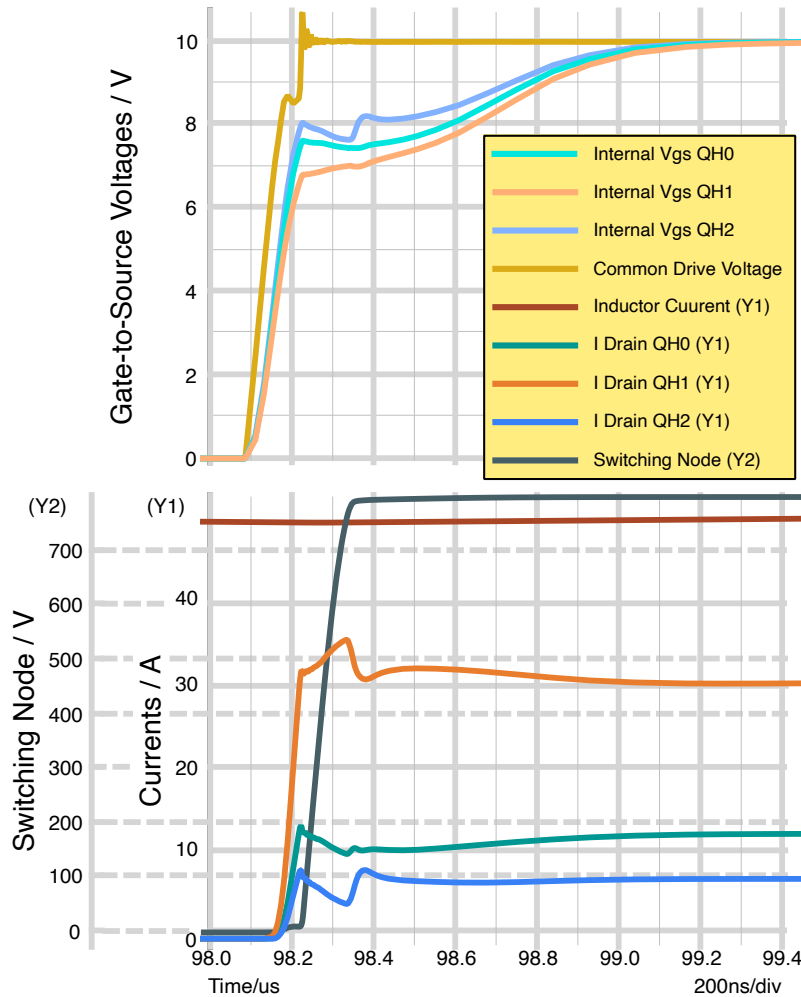


• Turn-OFF

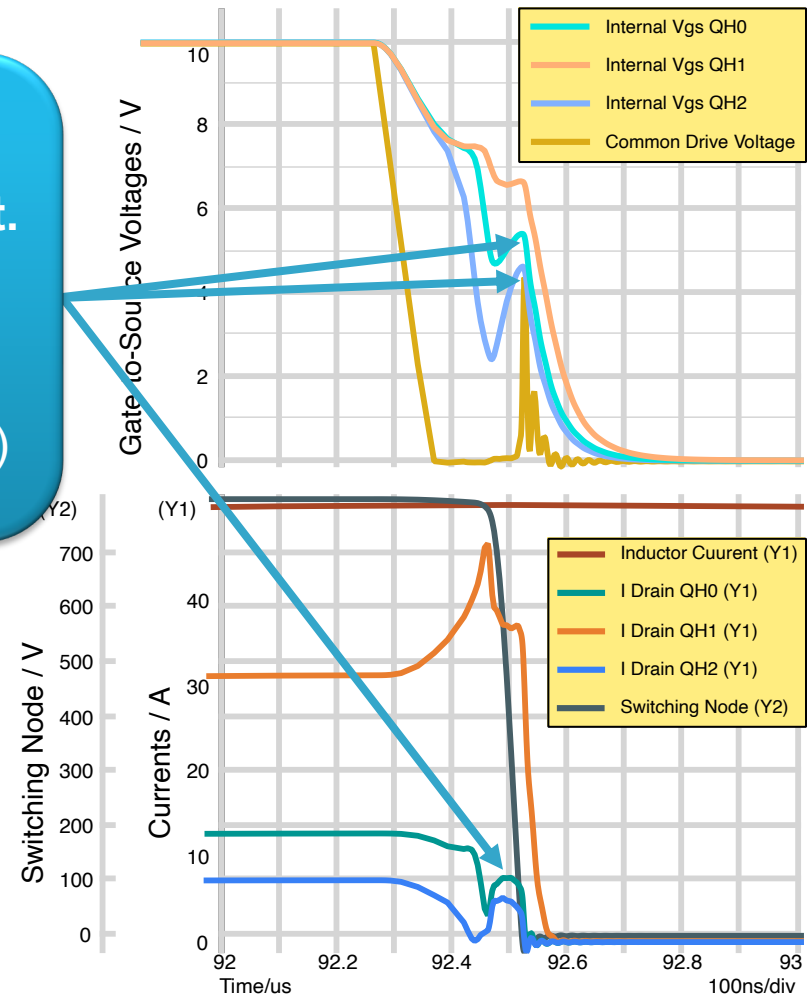

During Turn-OFF, QH0 and QH2 restart to conduct. It may be link to Gate-to-Source network (Internal+External) coupling

Buck stage waveforms with Corner Models

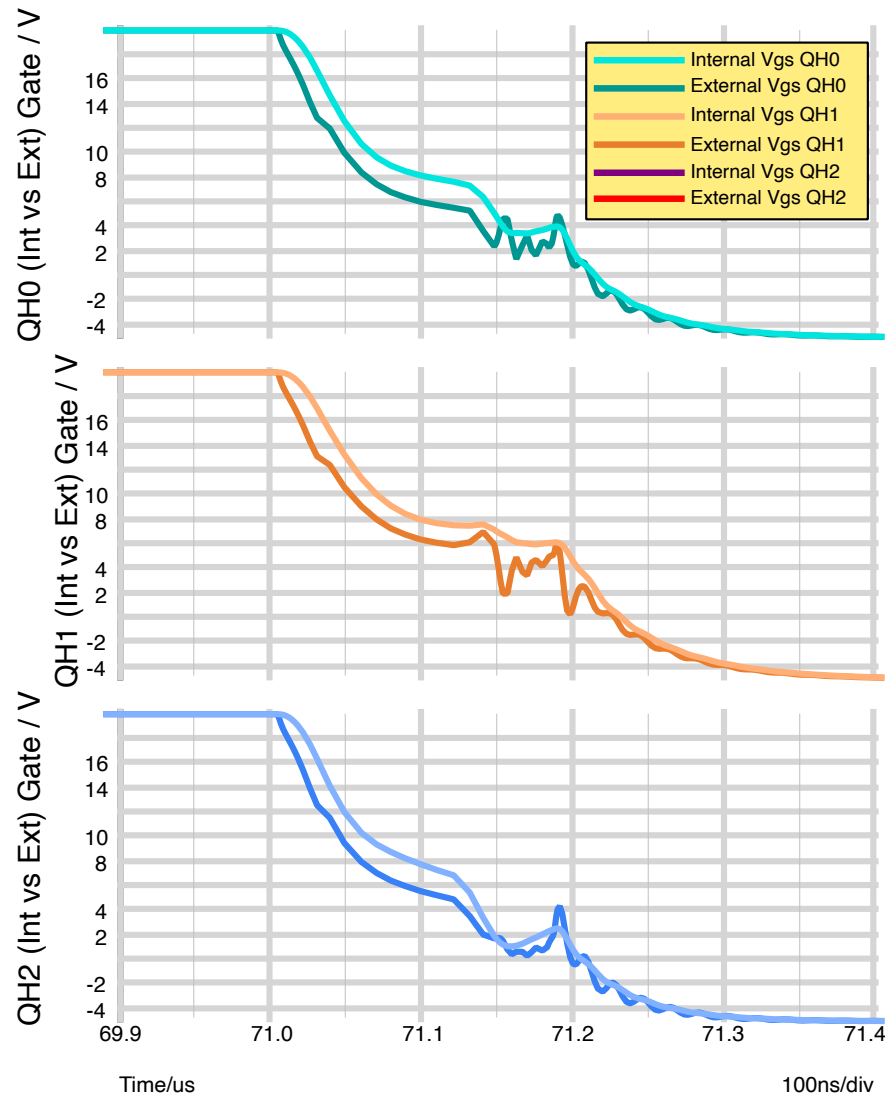


- We can see a lot of ringing on all external Gate-to-Kelvin Source waveforms...
- When QH0 and QH2 re-start to conduct, we have a peak of voltage above 2V (the threshold) on the internal Gate-to-Source waveforms.


Light-colored = Die nodes
Dark-colored = Pin nodes

Buck stage waveforms with Corner Models

- Losses (W)

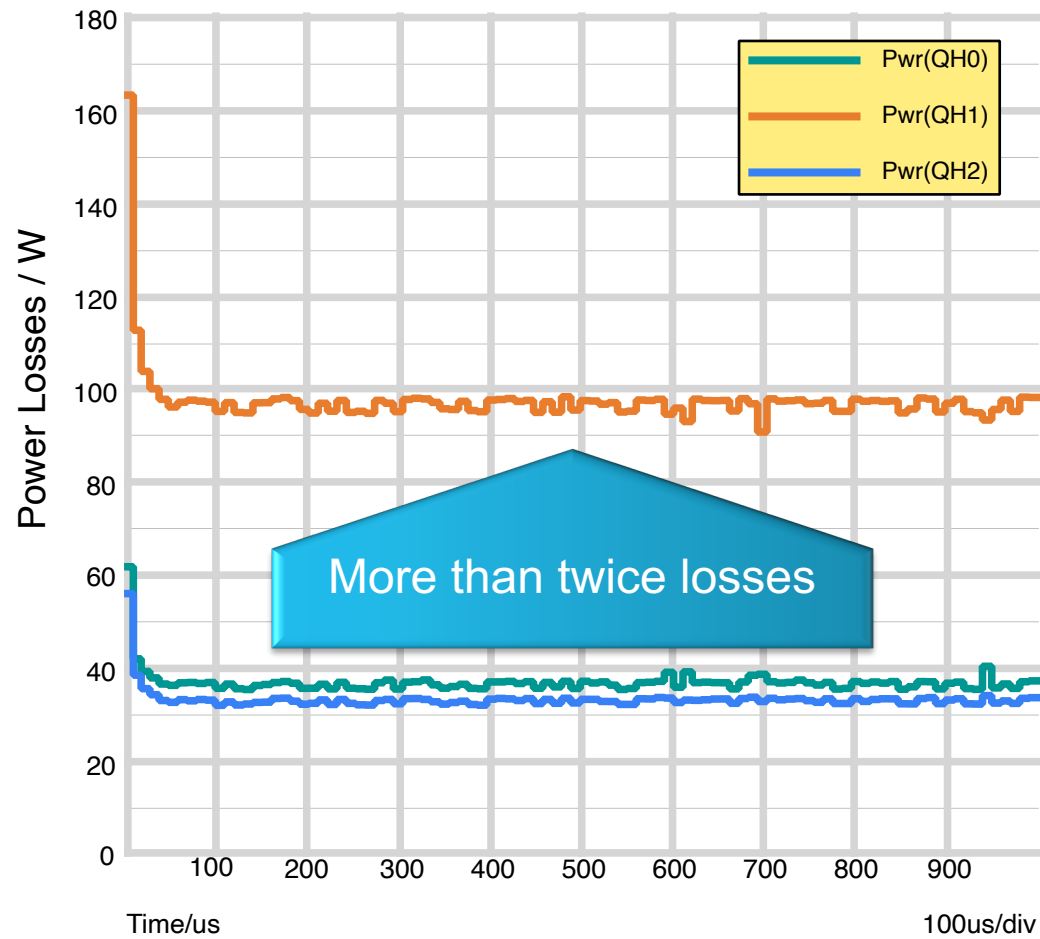

- Energies (μJ)

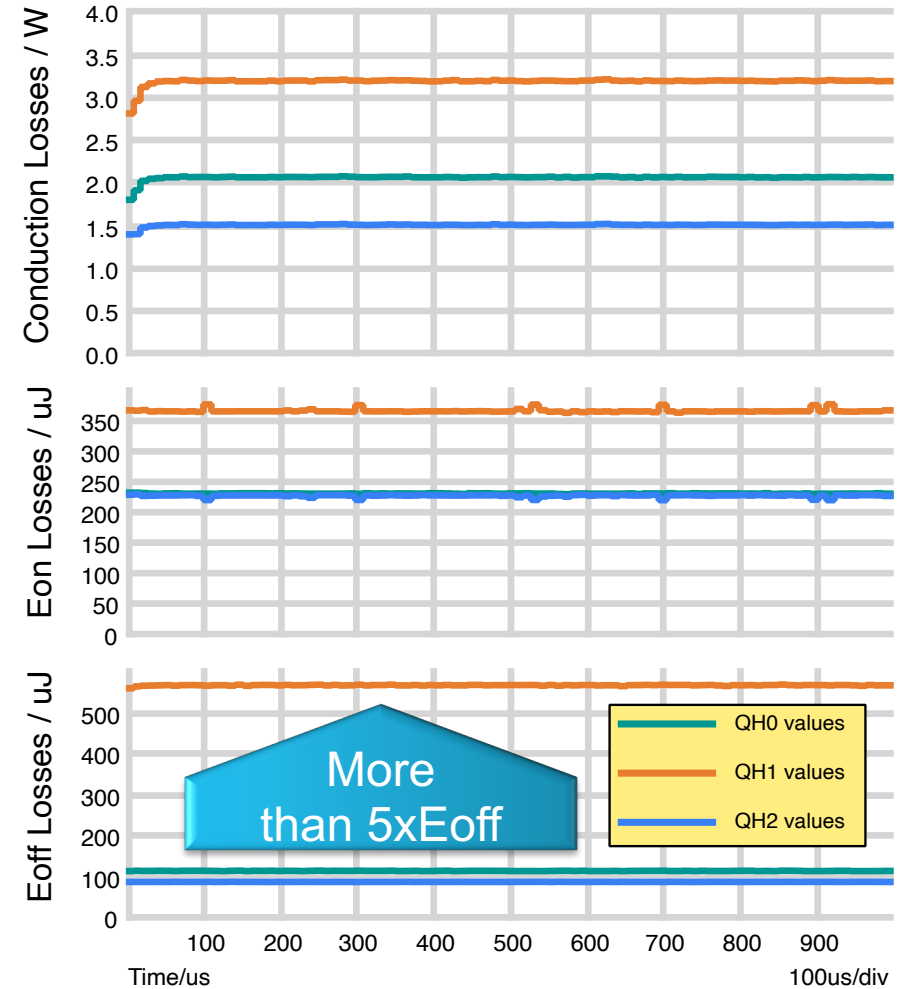


Electro-Thermal Simulations

Using Cauer Networks.

Electro-Thermal simulations


- We can simulate thermal behaviors using the following equivalences :
 - Power flow => Current
 - Temperature => Voltage
- Thermo-Electrical models have 2 extra pins :
 - Tcase = Case temperature
 - Tj = Junction temperature

- Thermo-Electrical models internal :

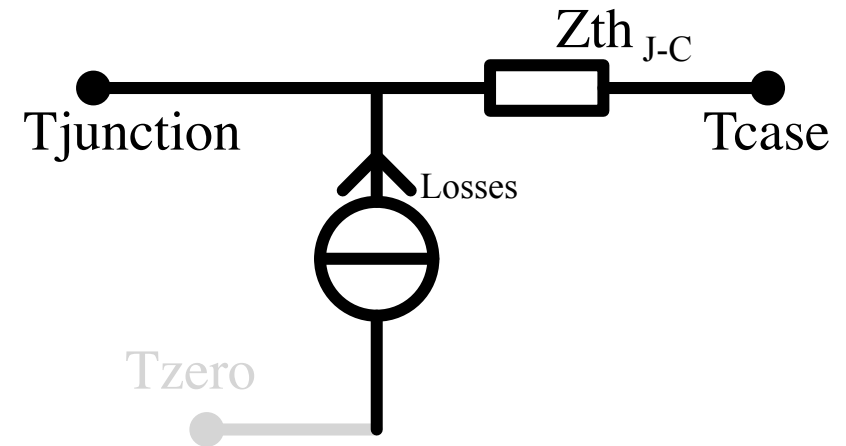


Electro-Thermal simulations : ΔT_{J-C}

Simulation Schematic

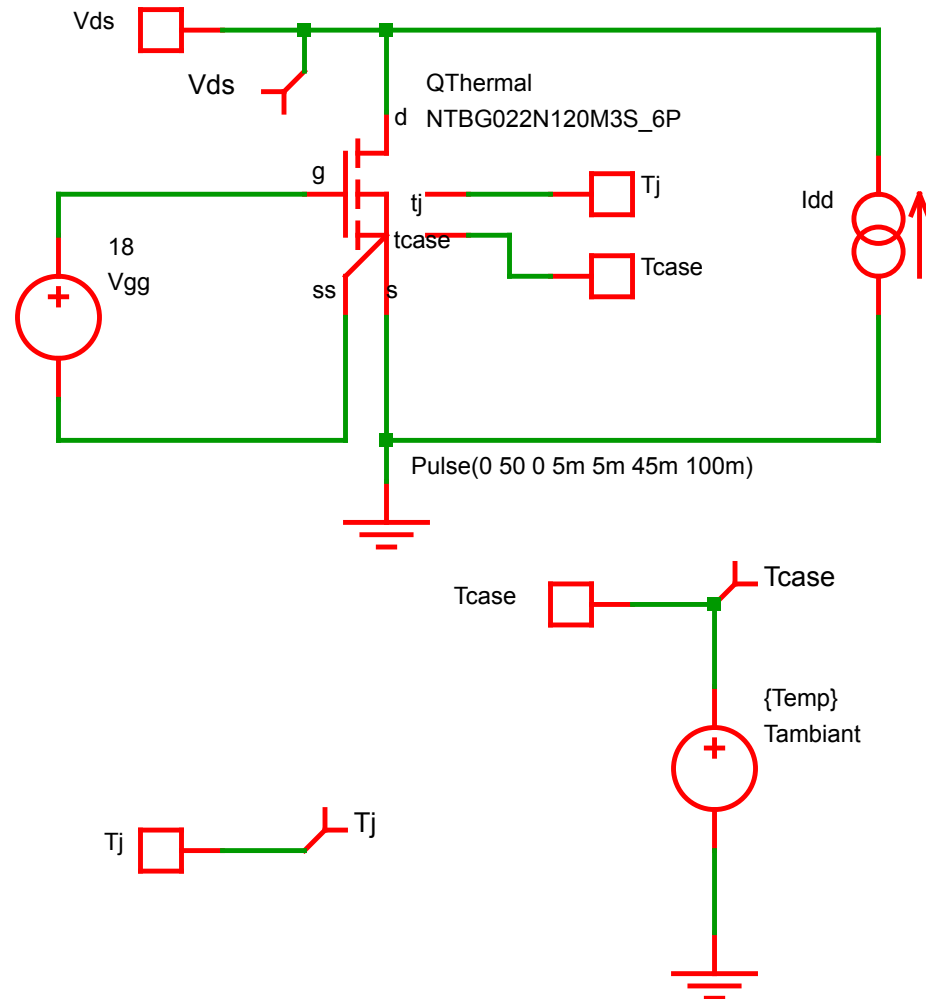


Results

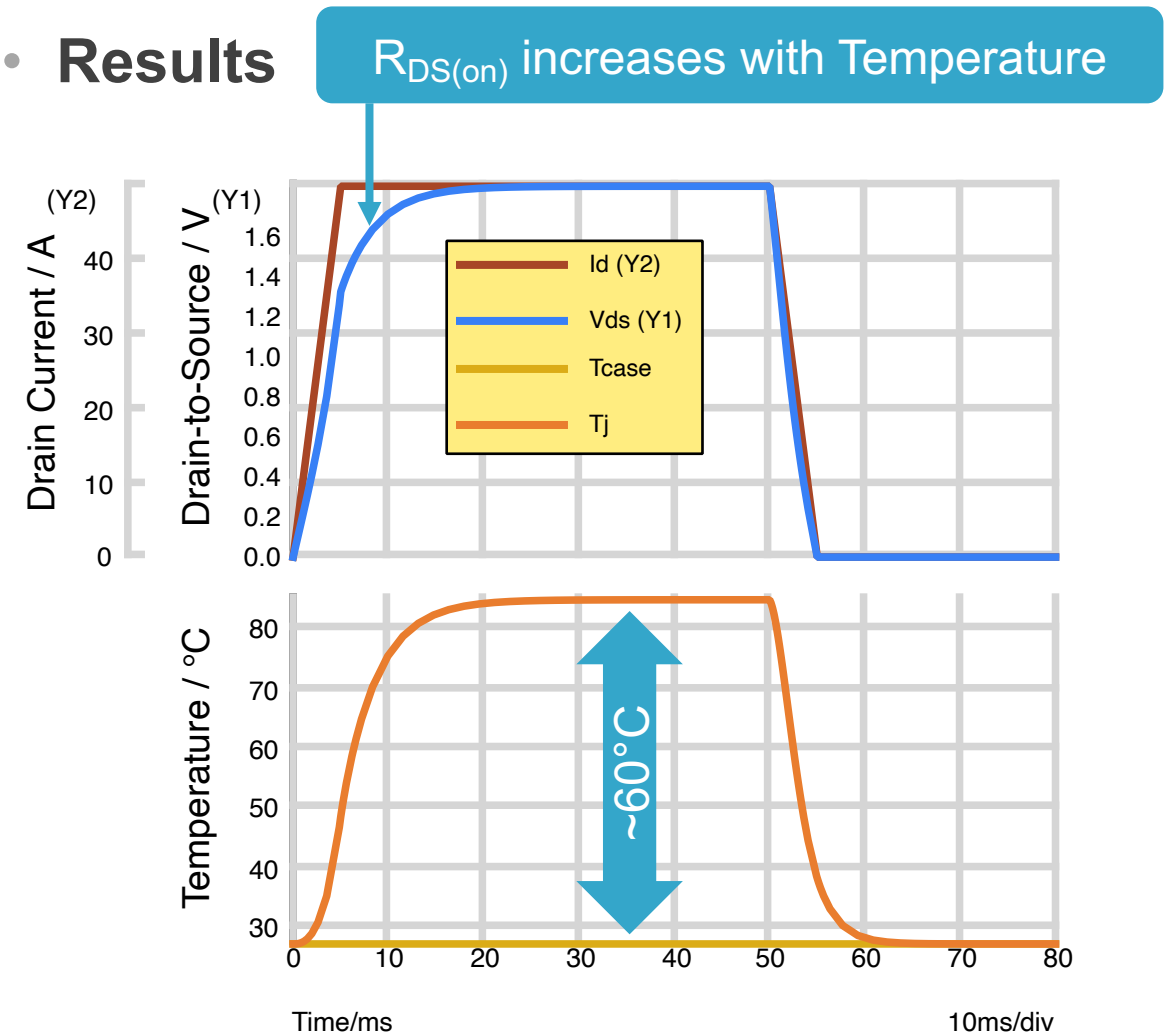


Electro-Thermal simulations : Heat Sink with Cauer network

- Cauer network for 1-ich PCB

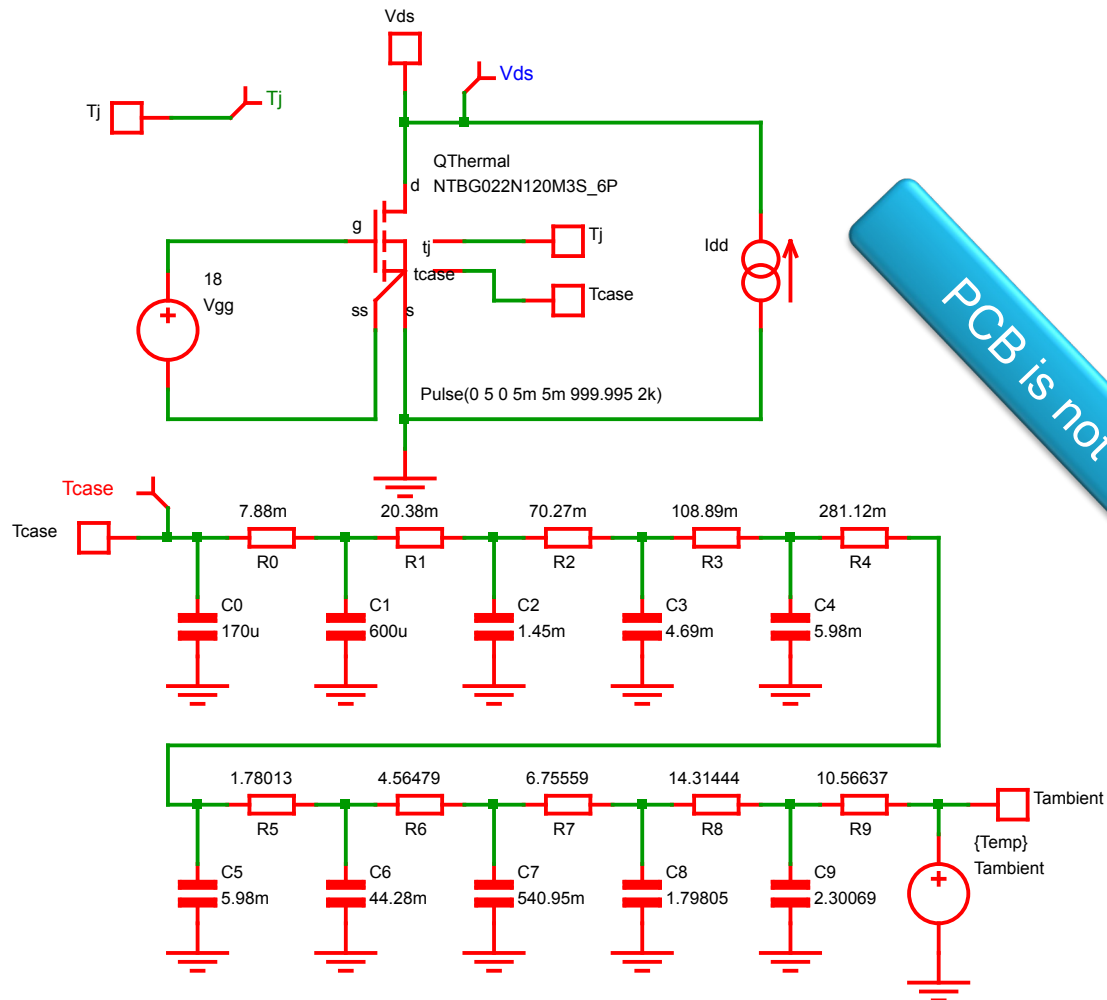

PCB is not the best HeatSink

- Results

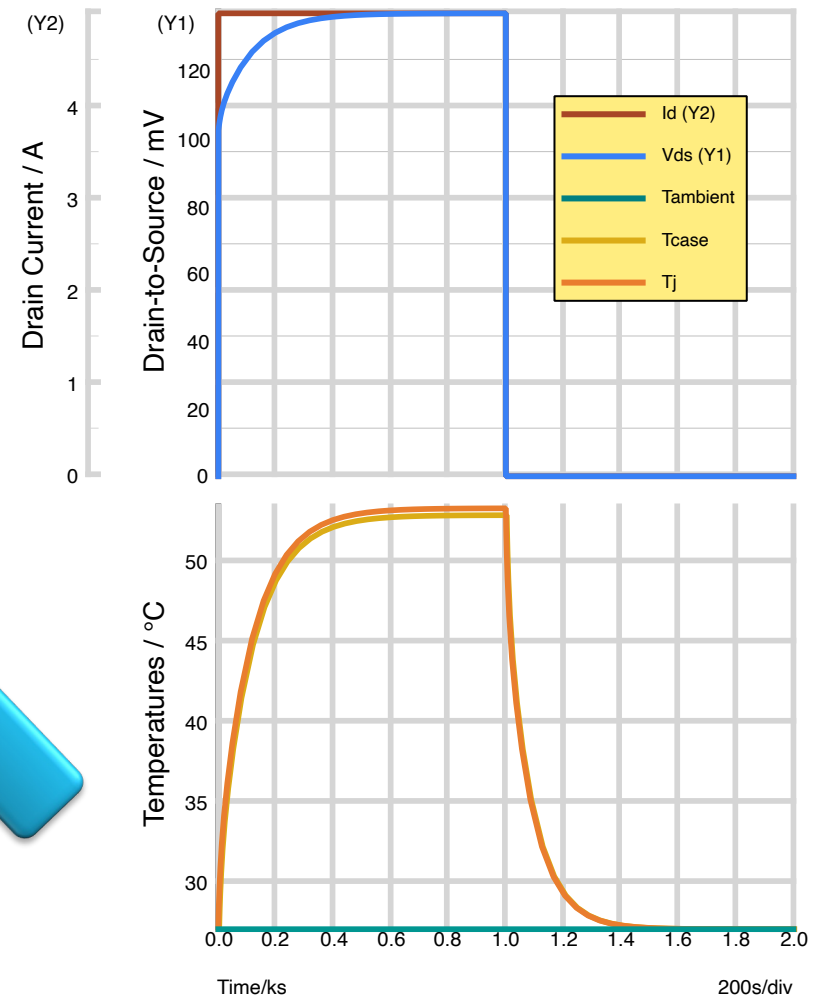

Switching Losses vs V_{GS} , Package and Structure

Using Double Pulse Measurement

Double Pulse Measurement Setup

• Schematic

* Current and Voltage for Eon and Eoff measurement

.Param Im=40
.Param Vbus=800


* Driver parameters Rise & Fall time

.Param tRise=10n
.Param tFall=10n

* Driver output voltage


.Param vOn=18
.Param vOff=-3

* Gate series resistance
.Param Rg=5

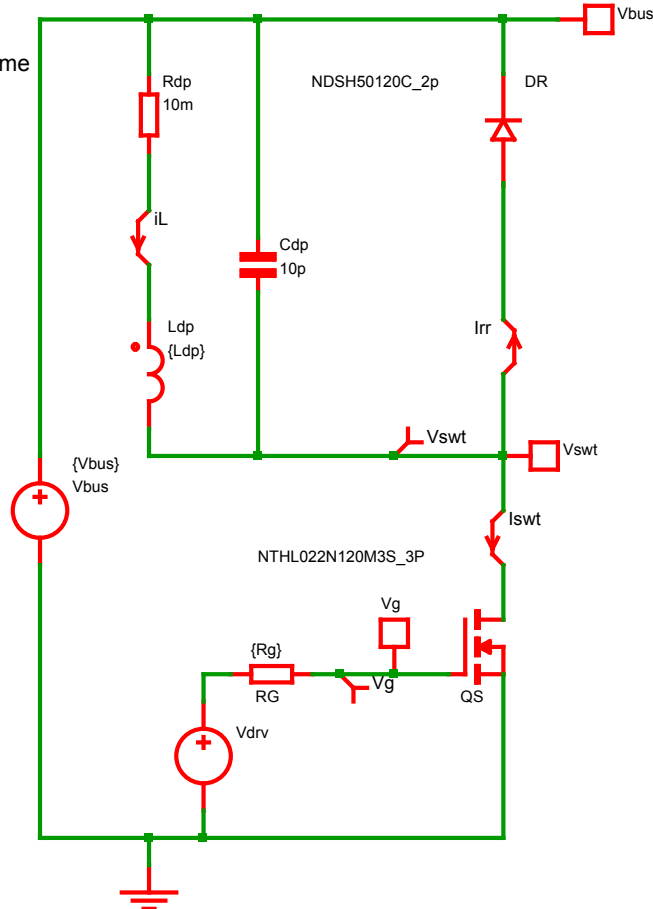


PWL(0 {vOff} {t1} {vOff} {t2} {vOn} {t3} {vOn} {t4} {vOff} {t5} {vOff} {t6} {vOn} {t7} {vOn} {t8} {vOff})

• Waveforms

 

Double Pulse Measurement Setup

- **Conventions**

 

- **Script**

- You can also use the waveform viewer math functions :
 - Multiply Voltage and Current = Losses
 - Integrate Losses
 - Measure using cursors the difference in between the two triggering points
- In our case, a script doing the previous steps has been created to measure E_{on} , E_{off} , and many other parameters... at once.


V_{GS} values' Influence

Setup : NDSH50120C (50 A, 1200 V, D3) freewheeling diode
NTH4L022N120M3S (22 mΩ, 1200 V, M3S) Switching MOSFET
Test point : 800 V / 40 A / 5Ω External Gate Resistor

V _{GS} Low/Off	V _{GS} High/On	Turn-on	Turn-off
0 V	12V	686.73 μJ	168.08 μJ
-3 V	12 V	685.52 μJ	109.03 μJ
0 V	15 V	467.44 μJ	168.75 μJ
-3 V	15V	461.23 μJ	108.92 μJ
0 V	18 V	376.66 μJ	168.56 μJ
-3 V	18 V	369.35 μJ	109.18 μJ

Structure Influence

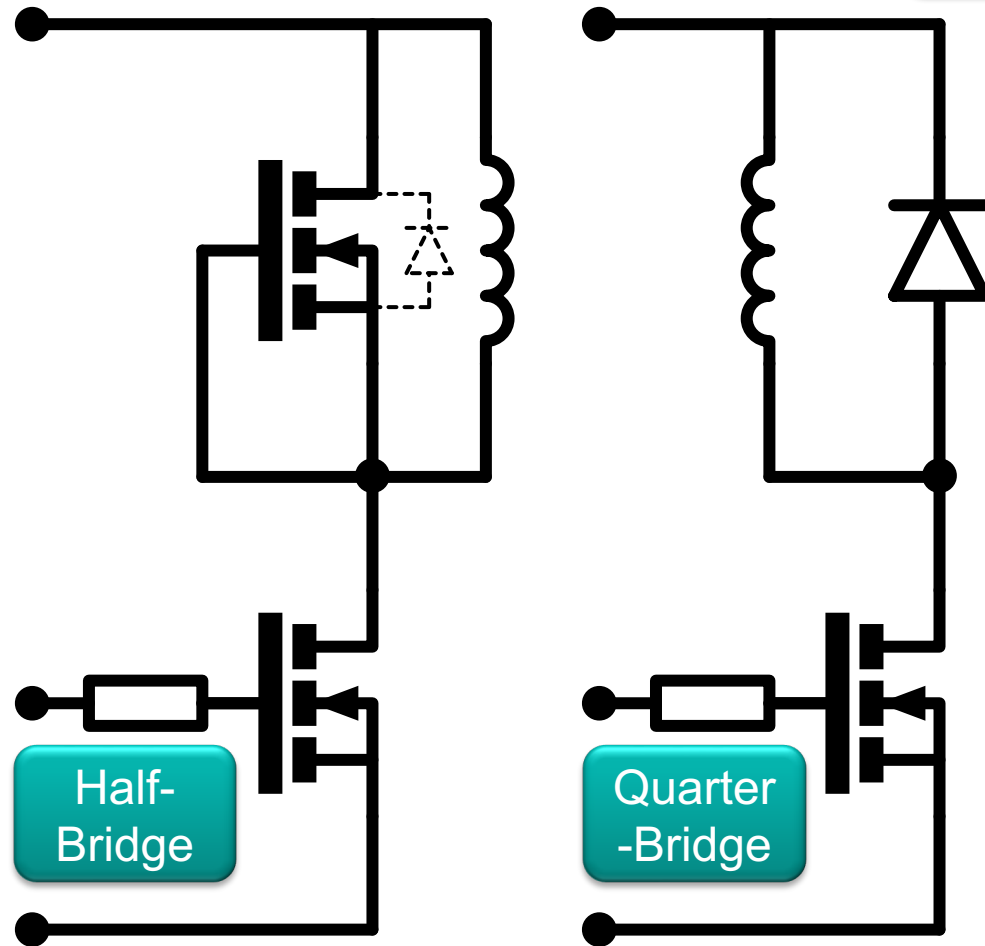Setup : NDSH50120C (50 A, 1200 V, D3) Quarter-brick only
NTH4L022N120M3S (22 mΩ, 1200 V, M3S) MOSFET
Test point : 800 V / 40 A / 5Ω External Gate Resistor



Structure	Quarter-Bridge	Half-Bridge
Turn-on	369 μJ	421 μJ
Turn-off	109 μJ	117 μJ

As SiC Schottky diode has less reverse current than SiC P-N Junction Body diode, Quarter-Bridge shows better results because there is less losses due to less reverse current flow.

Package Influence

Setup : NDSH50120C (50 A, 1200 V, D3) freewheeling diode
NTH4L022N120M3S (22 mΩ, 1200 V, M3S) Switching MOSFET
Test point : 800 V / 40 A / 5Ω External Gate Resistor

Package	TO247-3L	TO247-4L	D2Pak-7L
Turn-on	1115 μJ	421 μJ	483 μJ
Turn-off	257 μJ	117 μJ	111 μJ
Total	1372 μJ	538 μJ	594 μJ

Kelvin Packages show more than Half switching losses.

Topologies Simulations with Physical & Scalable Models

**Flying Capacitor Boost, I-NPC vs T-NPC,
6-Pack Boost Active front End**


Flying Capacitor Boost

DC-DC deep analysis



Flying Capacitor Boost

- Single Input — Single output
- Stacked Switches and Diodes
- Operates like an interleaved topology





 
- Example :
- 700 V in, 1100 V out
- 30 kW
- 30 kHz switching frequency
- Using M3S 1200V MOSFETs
- Using D1 30A 1200V Diodes



Flying Capacitor Boost waveforms

  

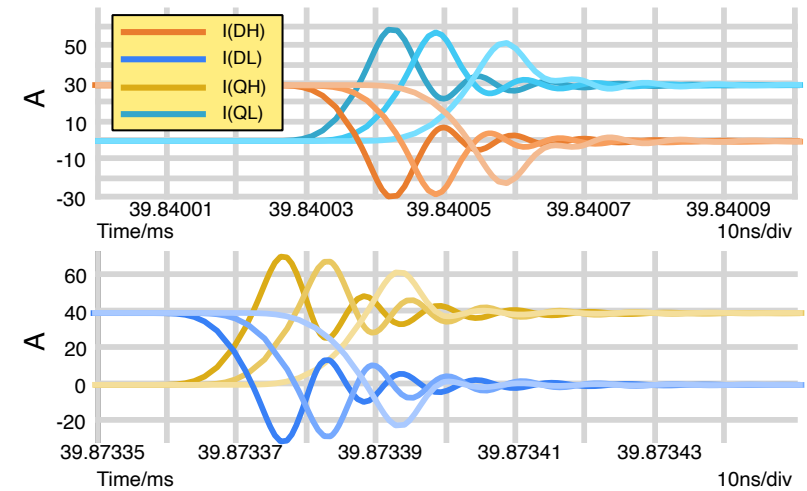    Flying Capacitor Boost Turn-ON and Turn-OFF zoom




External Gate Resistor	Negative peak I(DH)	Negative peak I(DL)
$R_g = 2.5 \Omega$	-29.3 A	-30.6 A
$R_g = 5 \Omega$	-27.8 A	-28.4 A
$R_g = 10 \Omega$	-22.3 A	-22.3 A

Flying Capacitor Boost performances

Losses using Current flowing out of Tcase


• $R_G = 2 \Omega$

 

Only MOSFETs losses increase by 2 or 3 W

Only MOSFETs ΔT_{J-C} increase around 1°C


• $R_G = 10 \Omega$

 

I-NPC vs T-NPC

Which is the best cell ?

I-NPC vs T-NPC : Quick comparison

 

- Comparison setup : Buck stage
 - 400 V in, 200 V / 20 A out
 - Switching frequency around 100 kHz (Self oscillating PWM)
 - D1 or D2 diodes = 50A / 650V
 - M2 MOSFET = 15 mΩ / 650V
 - M3S MOSFET = 22 mΩ / 1200V


Topology	I-NPC	I-NPC	I-NPC	A-NPC	A-NPC	T-NPC	SR T-NPC	SR T-NPC
QsH	M2 32.6 W	M2 18.7 W	M3S 7.8 W	M2 36.3 W	M3S 7.7 W	M3S 8.6 W	M3S 6.5 W	M3S 8.6 W
QdH/DH	D1 11.5 W	D2 10.9 W	D2 10.9 W	M2 18.1 W	M3S 18.8 W	M3S 50.4 W	M2 61.4 W	M3S 26.2 W
QmH	M2 4.4 W	M2 4.3 W	M2 4.3 W	M2 4.4 W	M3S 6.2 W	M3S 3.0 W	M2 2.2 W	M3S 3.1 W
Total	48.5 W	33.9 W	23.0 W	58.8 W	32.7 W	62 W	70.1 W	37.9 W

6-Pack Boost Active Front End

Or 3-Phase Grid Power Factor Corrector


6-Pack Boost Active Front End

 - 230 Vrms 3-Phase 50 Hz Grid input
- 950 V 50 kW output
- 72 kHz Switching frequency
- 80 μ H inductor, 10 m Ω ESR, 70 pF //
- 60 μ F capacitor, 2.5m Ω ESR
- D-Q control with Sine PWM
- FeedForward Duty cycle prediction
- 3rd Harmony Injection




6-Pack Boost Active Front End : Waveforms

- Without 3rd Harmonic Injection

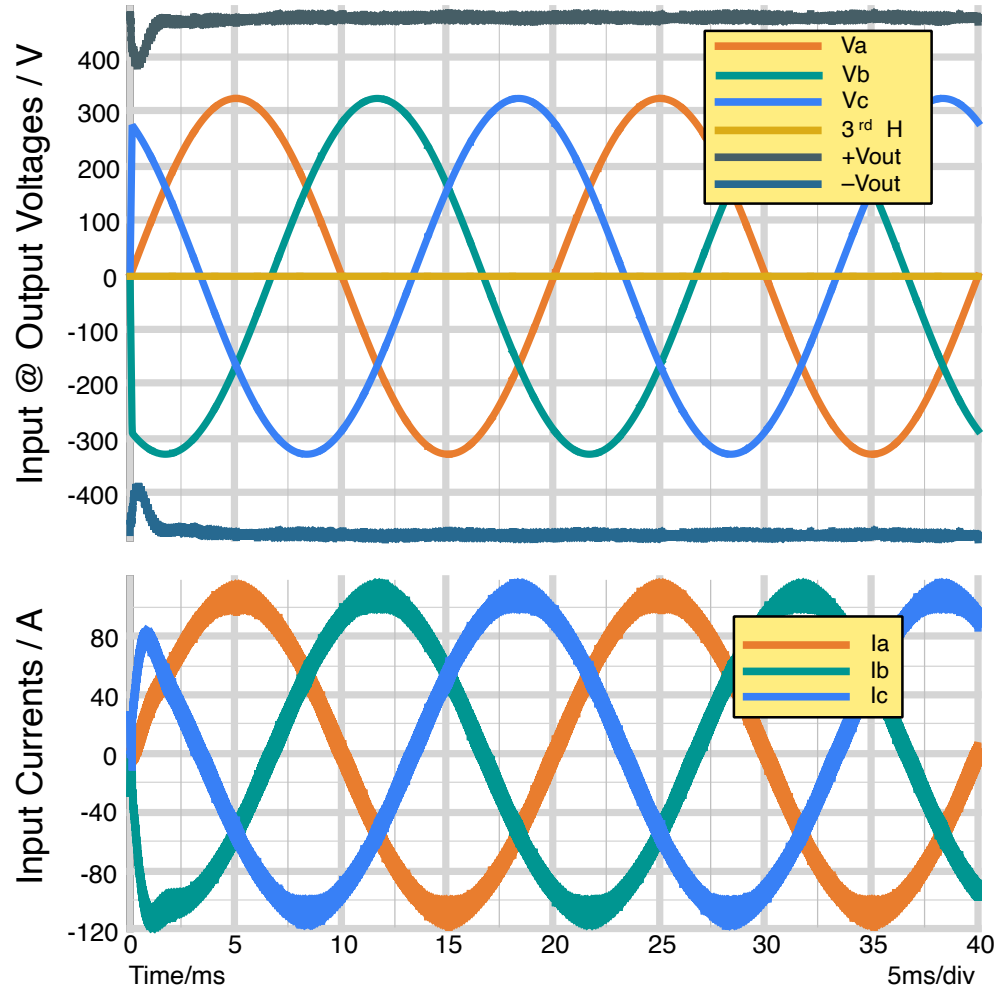


- With 3rd Harmonic Injection

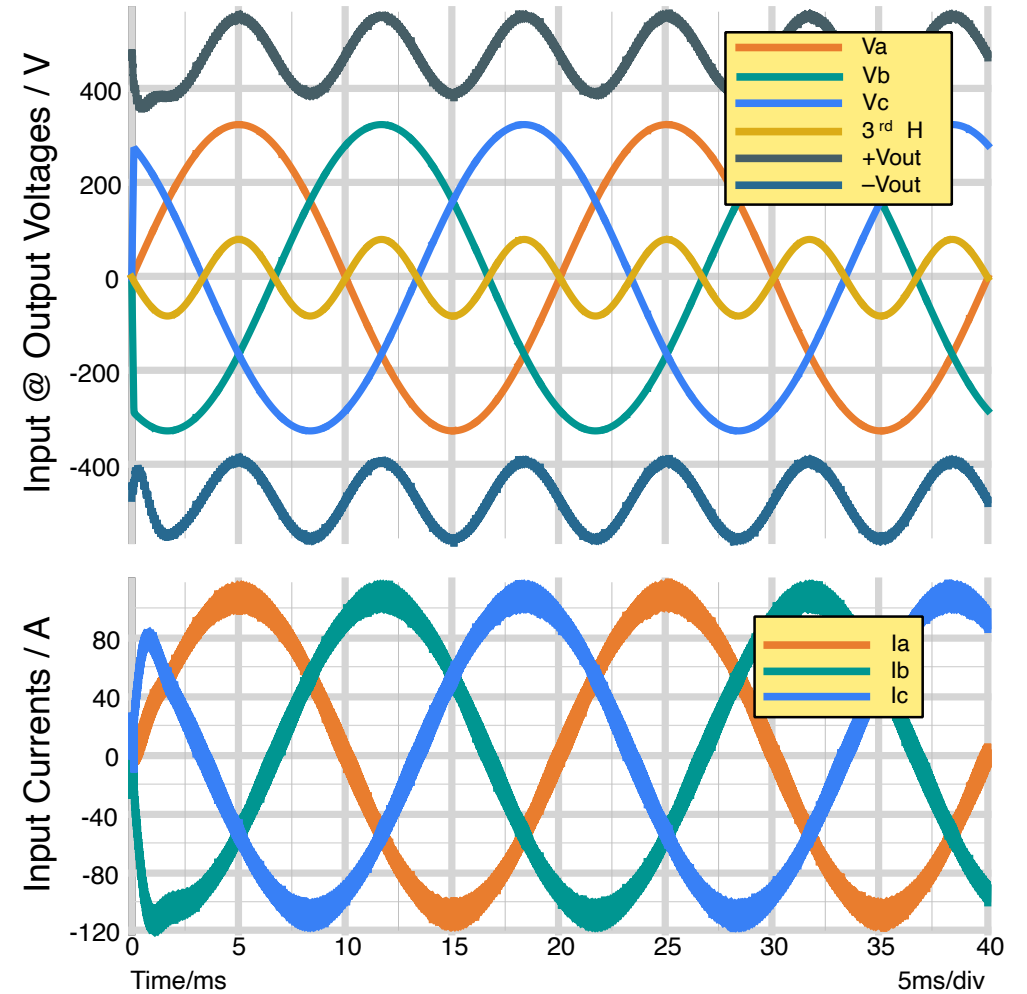


6-Pack Boost Active Front End : Losses Cycle by Cycle

Without 3rd Harmonic Injection

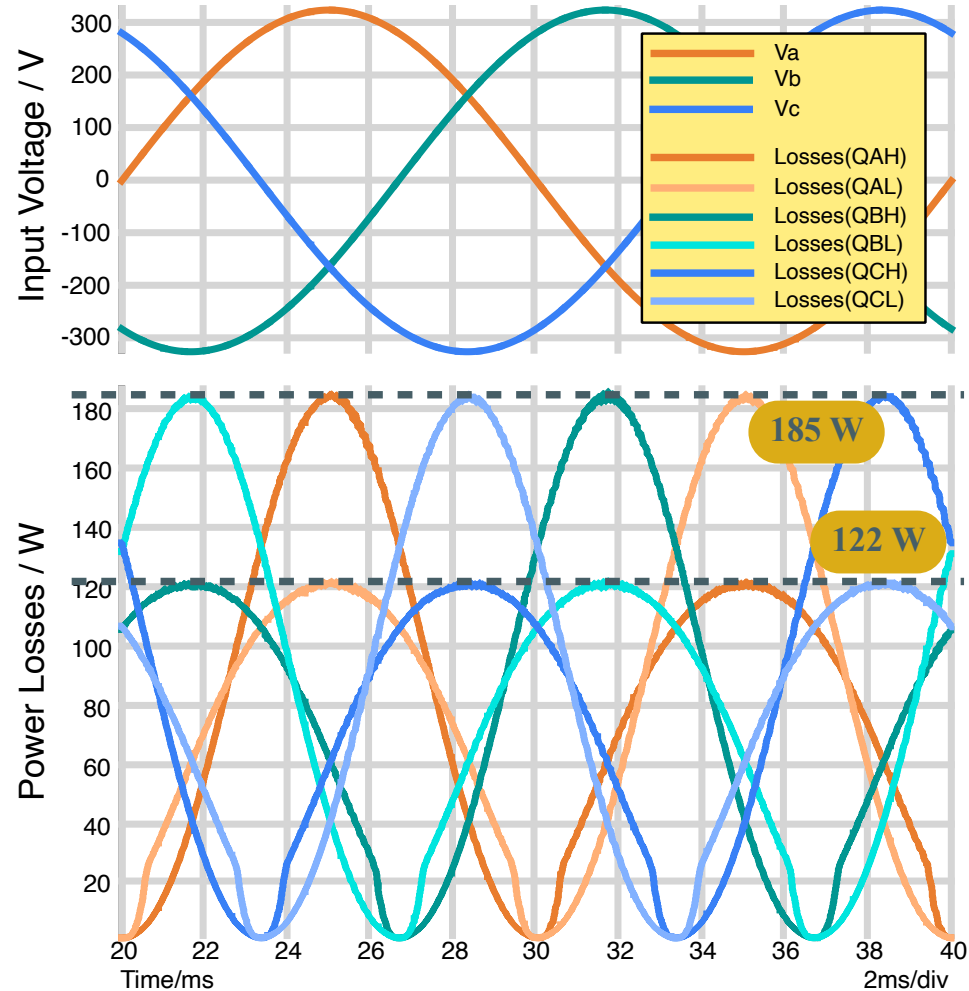

With 3rd Harmonic Injection

 

6-Pack Boost Active Front End : Average Losses over Grid Cycle

- Without 3rd Harmonic Injection

QAH Power Losses : 83.5584W

QAL Power Losses : 83.5516W

QBH Power Losses : 83.55W

QBL Power Losses : 83.5384W

QCH Power Losses : 83.5505W

QCL Power Losses : 83.5402W

- Total

Power Losses : 501.289W

- With 3rd Harmonic Injection

QAH Power Losses : 83.6955W

QAL Power Losses : 83.6902W

QBH Power Losses : 83.6783W

QBL Power Losses : 83.6803W

QCH Power Losses : 83.6782W

QCL Power Losses : 83.6865W

- Total

Power Losses : 502.109W



Same
Losses

Conclusion

Conclusion

- **onsemi** simulation models offer unique features like :
 - Access to internal nodes
 - Accurate results for device have large non-linearities over several decades
- We have seen how to set Electro-Thermal simulations and get more out of them :
 - Junction temperature rise,
 - Heat propagation and Average Losses using power flow.
- Topologies simulations and analysis can bring very useful information like :
 - Junction temperature rise,
 - Losses analysis (switching energy, reverse current effect, $R_{DS(on)}$ variations, ...)
 - Impact of parasitic components on **Silicon Carbide** devices performances
- Physical & Scalable models make virtual prototyping much more real.

onsemiTM

Intelligent Technology. Better Future.

Follow Us @onsemi



www.onsemi.com

Bibliography or References

- [1] An Introduction to Physical Scalable Models for Wide Bandgap Power Semiconductor – Part One (Blog article)
<https://www.onsemi.com/blog/industrial-cloud-power/wide-band-gap-ecosystem-part-i>
- [2] Wide Bandgap Power Semiconductor: Silicon Carbide MOSFET Models – Part Two – (Blog Article)
<https://www.onsemi.com/blog/industrial-cloud-power/wide-band-gap-ecosystem-switches-disruptive-environments>
- [3] Wide Bandgap Semiconductor Simulation Model Verification – Part Three – (Blog Article)
<https://www.onsemi.com/blog/industrial-cloud-power/wide-bandgap-semiconductor-simulation-model-verification>
- [4] Physically Based, Scalable SPICE Modeling Methodologies for Modern Power Electronic Devices – (White paper)
<https://www.onsemi.com/pub/Collateral/TND6260-D.PDF>
- [5] SPICE Modeling Tutorial – (Tutorial)
<https://www.onsemi.com/pub/collateral/tnd6248-d.pptx>
- [6] Physically Based, Scalable SPICE Modeling Methodologies for Modern Power Electronic Devices – (Video)
<https://www.onsemi.com/video/physically-based-scalable-spice-modeling-methodologies-for-modern-power-electronic-devices>
- [7] How to use Physical and Scalable Models with SIMetrix, OrCAD and LTSpice – (Application note)
<https://www.onsemi.com/pub/collateral/and9783-d.pdf>
- [8] Using Physical and Scalable Simulation Models to Evaluate Parameters and Application Results – (White paper)
<https://www.onsemi.com/pub/collateral/tnd6330-d.pdf>
- [9] Simulate with Physical and Scalable Discrete Models...What could we get ? – (Tutorial)
<https://www.onsemi.com/pub/Collateral/TND6329-D.PDF>
- [10] Using Physical and Scalable Simulation Models to Evaluate Parameters and Application Results – (Video)
<https://www.onsemi.com/video/using-physical-and-scalable-simulation-models-to-evaluate-parameters-and-application-results>
- [11] Usage of SIMetrix to Study MOSFETs Thermal Behaviors on Heatsink – (Application note)
<https://www.onsemi.com/pub/collateral/and90096-d.pdf>